

**LROBRUYA**

**LONTEN Super Starter  
Kit for Arduino Uno**



## Content

Preface .....	4
Kit Introduction .....	6
Kit List .....	7
Install Arduino IDE .....	8
Add Libraries and Open Serial Monitor .....	16
Blink Test .....	26
Lesson 1 LED .....	36
Lesson 2 RGB LED .....	45
Lesson 3 Digital Inputs .....	54
Lesson 4 Active Buzzer .....	59
Lesson 5 Passive Buzzer .....	62
Lesson 6 Tilt Ball Switch .....	66
Lesson 7 Analog Value Reading .....	69
Lesson 8 Servo .....	73
Lesson 9 Analog Joystick Module .....	77
Lesson 10 Water Level Detection Sensor Module .....	81
Lesson 11 Sound Sensor Module .....	85
Lesson 12 DHT11 Temperature and Humidity Sensor .....	91
Lesson 13 Ultrasonic Sensor Module .....	95



---

Lesson 14 HC-SR501 PIR Sensor .....	100
Lesson 15 IR Receiver Module .....	110
Lesson 16 Membrane Switch Module .....	117
Lesson 17 Eight LED with 74HC595 .....	121
Lesson 18 Photocell .....	130
Lesson 19 74HC595 And Segment Display .....	136
Lesson 20 Four Digital Seven Segment Display .....	142
Lesson 21 GY-521 Module .....	146
Lesson 22 MAX7219 LED Dot Matrix Module .....	154
Lesson 23 RC522 RFID Module .....	158
Lesson 24 Real Time Clock Module .....	164
Lesson 25 The Serial Monitor .....	169
Lesson 26 LCD1602 I2C Module .....	178
Lesson 27 Thermometer .....	183
Lesson 28 DC Motors .....	189
Lesson 29 Relay .....	200
Lesson 30 Stepper Motor .....	204
Lesson 31 Controlling Stepper Motor With Remote .....	212
Lesson 32 Controlling Stepper Motor With Rotary Encoder .....	216



## Preface

### Company Profile

Founded in 2014, Shenzhen Lonten Technology Co., Ltd. focuses on the design, research production of Electronics Module for robotics related products. Consisting of professional researchers and skilled engineers, our R&D team constantly strives for creative function and excellent user experience. The company's R&D investments on arduino kits raspberry pi kits, as well as 3D printer and robots that back up STEAM education.

### Customer Service

Our self-owned factory is certificated with BSCI and SO, covering an area of 5,000 square meters, and achieving an annual production capacity of over 10,000 units. Our products are all certified to CE, FCC, and ROHS standards, have exported to more than 100 countries including, but not limited to France, the United States of America, Australia, Russia, the United Kingdom, Germany, Singapore, Egypt, and India, bringing technological innovation to all walks of life.

By the way, We also look forward to hearing from you and any of your critical comment or suggestions. Pls email us by [lonten3@qq.com](mailto:lonten3@qq.com) or [info@lontentech.com](mailto:info@lontentech.com), if you have any questions or suggestions.



---

As a continuous and fast growing company. We keep striving our best to offer you excellent products and quality service.

## **Our Store**

store: <https://www.lontentech.com/>

Brand: LONTEN

## **Product Catalog**

<https://www.aliexpress.us/item/3256805786131500.html?gatewayAdapt=glo2usa4itemAdapt>


## **Tutorial**

This tutorial include codes, libraries and detailed user documentation. It is designed for beginners. You will learn all the basic knowledge about how to use Arduino controller board, sensors and components.

# LROBRYA
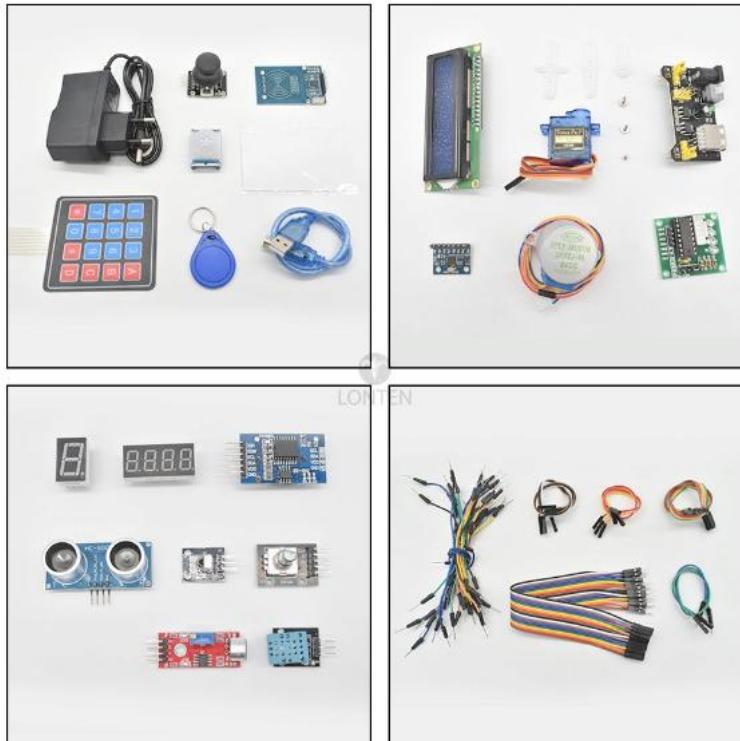
## Kit Introduction

This is a Super Starter Kit for Arduino, rolled out by LONTEN.



components.

Now, let's start from the lessons.

This tutorial include codes, libraries and lessons. It is designed for beginners. You will learn all the basic knowledge about how to use Arduino controller board, sensors and

# LROBRYA



## Kit List

### Super Starter Kit

Contact us:

<https://www.lontentech.com/pages/contact-us>




## Install Arduino IDE

### Introduction

The Arduino Integrated Development Environment (IDE) is the software side of the Arduino platform.

In this Project, you will learn how to setup your computer to use Arduino and how to set about the Projects that follow.

The Arduino software that you will use to program your Arduino is available for Windows, Mac and Linux. The installation process is different for all three platforms and unfortunately there is a certain amount of manual work to install the software.

**STEP 1: Go to <https://www.arduino.cc/en/software>.**



The screenshot shows the Arduino IDE 2.1.1 download page. On the left, there's a teal rounded square icon with a white infinity symbol and a plus sign. To its right, the text "Arduino IDE 2.1.1" is displayed. Below this, a paragraph describes the new features of version 2.1.1, mentioning faster performance, a modern editor, autocompletion, code navigation, and a live debugger. It also links to the "Arduino IDE 2.0 documentation". Further down, it mentions "Nightly builds" and provides a link to the GitHub source code, stating it's open source and hosted on GitHub. On the right side, a teal sidebar titled "DOWNLOAD OPTIONS" lists download links for various operating systems: Windows (Win 10 and newer, 64 bits), Windows (MSI installer), Windows (ZIP file), Linux (AppImage 64 bits (X86-64)), Linux (ZIP file 64 bits (X86-64)), macOS (Intel, 10.14: "Mojave" or newer, 64 bits), and macOS (Apple Silicon, 11: "Big Sur" or newer, 64 bits). At the bottom of the sidebar, there's a link to "Release Notes".

**The version available at this website is usually the latest version, and the actual version may be newer than the version in the picture.**

# LROBRYA

## STEP2: Download the development software that is compatible with the operating.

system of your computer. Take Windows as an example here.




Click Windows Win 10 and newer, 64 bits.



Click JUST DOWNLOAD.




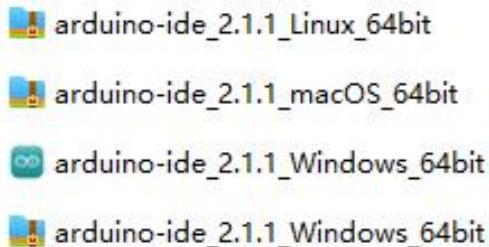Also version 2.1.1 is available in the material we provided, and the versions of our materials are the latest versions when this course was made.



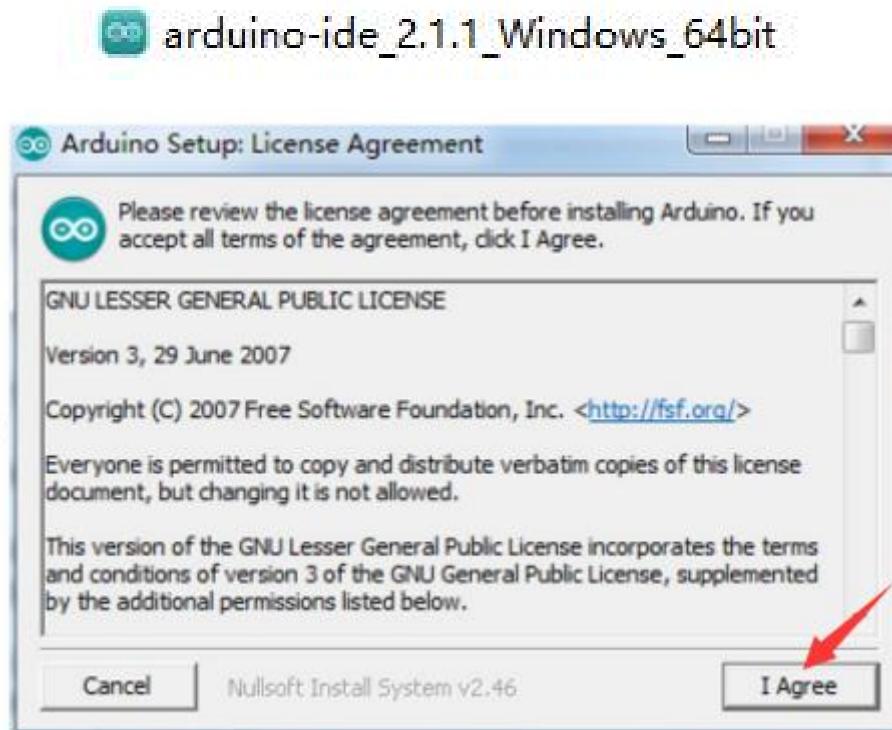
## Installing Arduino (Windows)

Install Arduino with the exe. Installation package.




Click I Agree to see the following interface.

# LROBRUYA

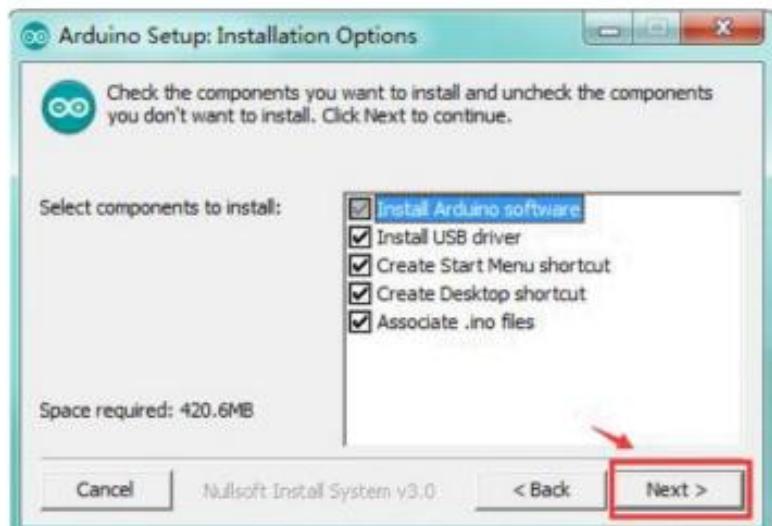

Click Next

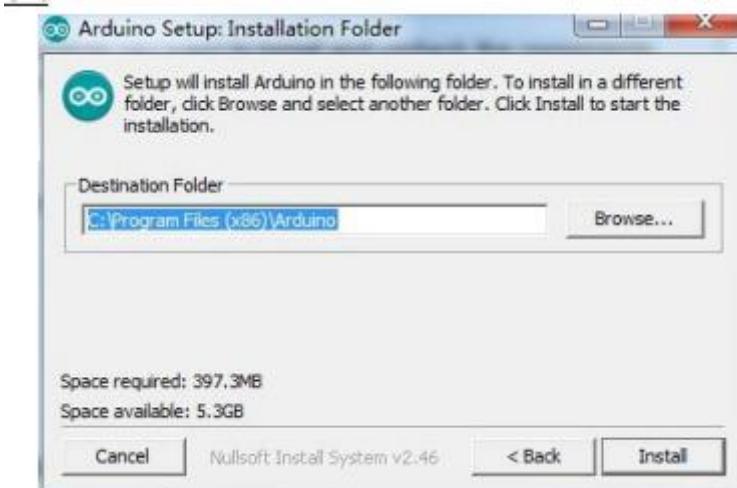


You can press **Browse...** to choose an installation path or directly type in the directory you want.

# LROBRUYA




Click Install to initiate installation

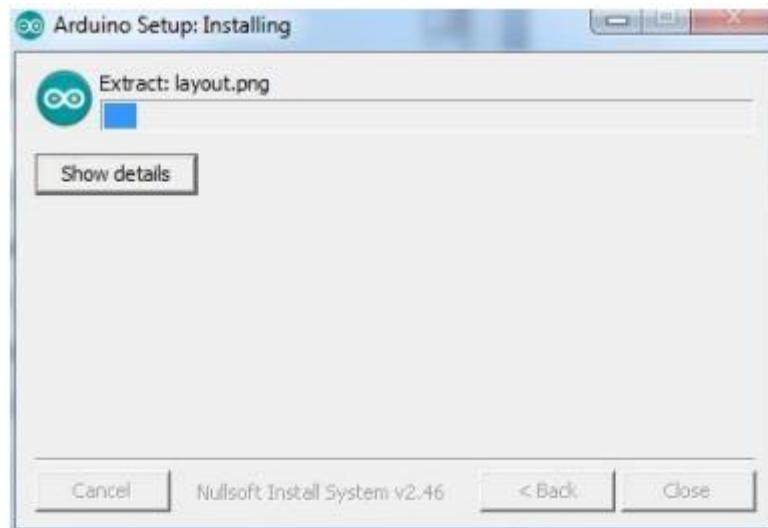

Finally, the following interface appears, click Install to finish the installation.


# LROBRUYA

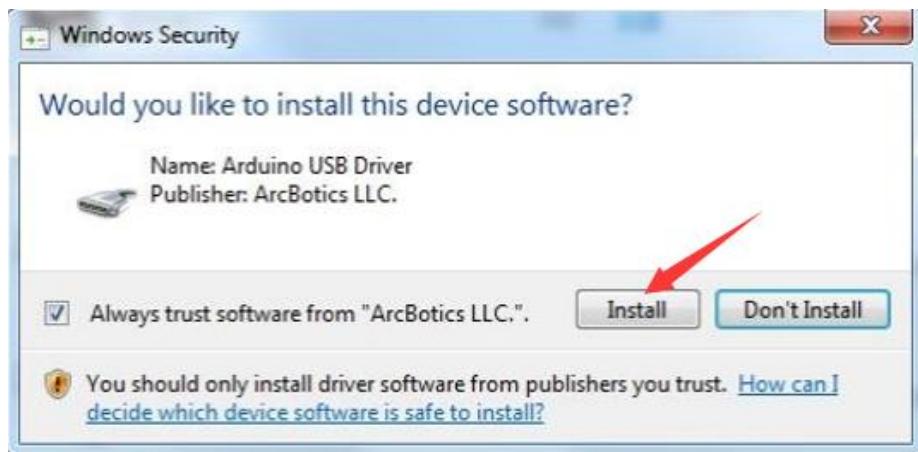

Next, the following icon appears on the desktop



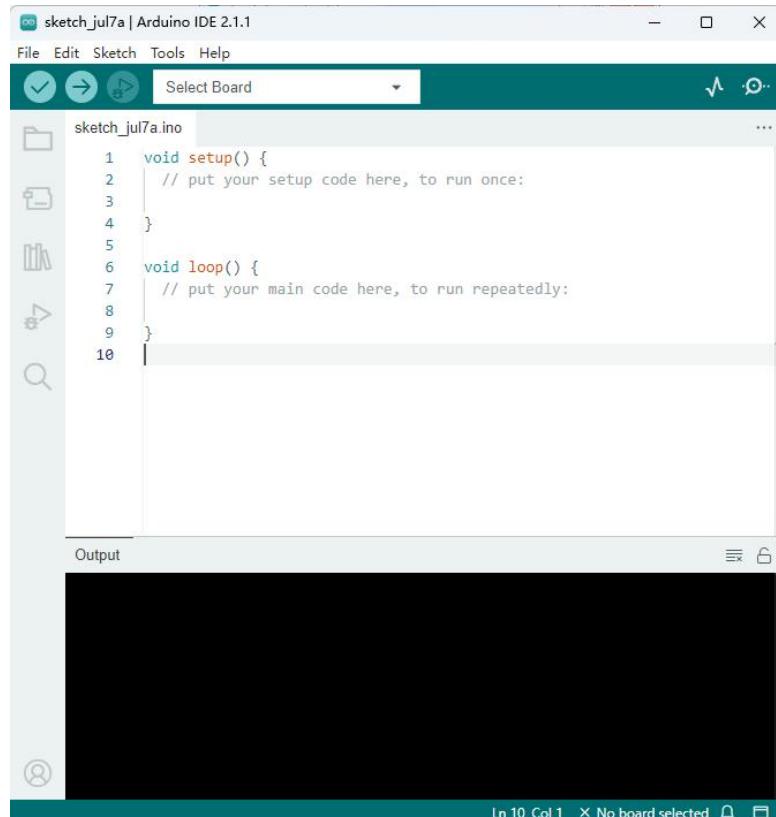Double-click to enter the desired development environment



You may directly choose the installation package for installation and


# LROBRYA

skip the contents below and jump to the next section. But if you want to learn some methods other than the installation package, please continue to read the section.

Unzip the zip file downloaded, Double-click to open the program and enter the desired development environment.


arduino-ide_2.1.1_Windows_64bit				
名称	修改日期	类型	大小	
drivers	2023/7/5 21:45	文件夹		
examples	2023/7/5 21:45	文件夹		
hardware	2023/7/5 21:45	文件夹		
java	2023/7/5 21:45	文件夹		
lib	2023/7/5 21:45	文件夹		
libraries	2023/7/5 21:45	文件夹		
reference	2023/7/5 21:45	文件夹		
tools	2023/7/5 21:45	文件夹		
tools-builder	2023/7/5 21:45	文件夹		
arduino	2017/6/1 0:58	应用程序	395 KB	
arduino.l4j	2017/6/1 0:58	配置设置	1 KB	
arduino_debug	2017/6/1 0:58	应用程序	393 KB	
arduino_debug.l4j	2017/6/1 0:58	配置设置	1 KB	
arduino-builder	2017/6/1 0:58	应用程序	3,214 KB	
libusb0.dll	2017/6/1 0:58	应用程序扩展	43 KB	
msvcp100.dll	2017/6/1 0:58	应用程序扩展	412 KB	
msvcr100.dll	2017/6/1 0:58	应用程序扩展	753 KB	
revisions	2017/6/1 0:58	文本文档	83 KB	
uninstall	2023/7/5 21:45	应用程序	404 KB	

# LROBRYA

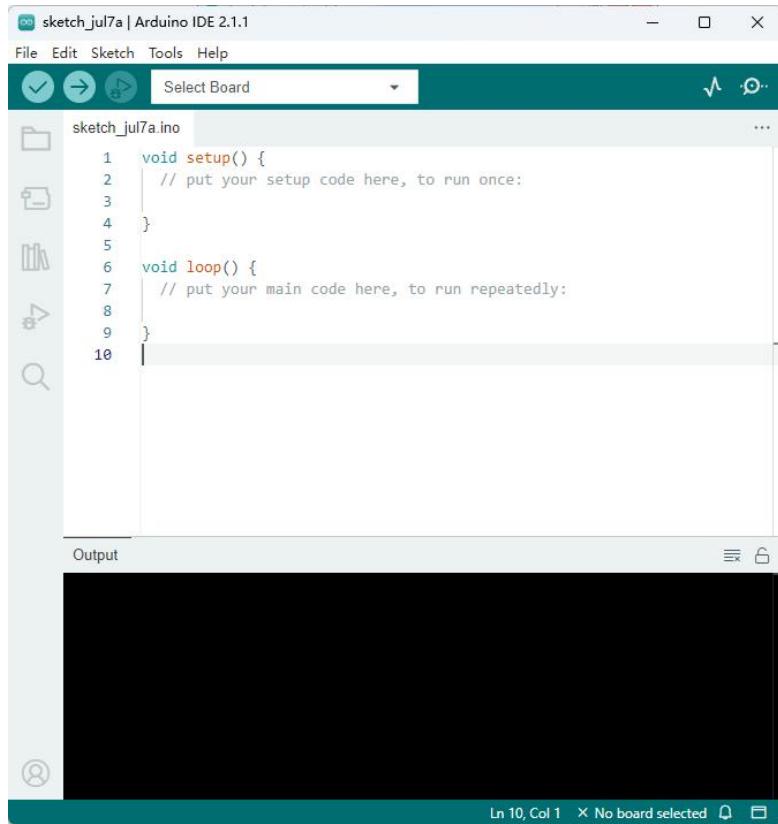
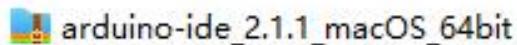
## Installing Arduino (Mac OS X)

Download and Unzip the zip file, double click the Arduino.app to enter Arduino IDE; the system will ask you to install Java runtime library if you don't have it in your computer. Once the installation is complete you can run the Arduino IDE.




## Installing Arduino (Linux)

You will have to use the make install command. If you are using the Ubuntu system, it is recommended to install Arduino IDE from the software center of Ubuntu.

# LROBRYA

---

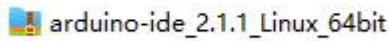

## Add Libraries and Open Serial Monitor

### Installing Additional Arduino Libraries

Once you are comfortable with the Arduino software and using the built-in functions, you may want to extend the ability of your Arduino with additional libraries.

### What are Libraries?


Libraries are a collection of code that makes it easy for you to connect to a sensor, display, module, etc. For example, the built-in Liquid Crystal library makes it easy to talk to character LCD displays. There are hundreds of additional libraries available on the Internet for download. The built-in libraries and some of these additional libraries are listed in the reference. To use the additional libraries, you will need to install them.

### How to Install a Library

#### Using the Library Manager

To install a new library into your Arduino IDE you can use the Library Manager (available from IDE version 1.8.0). Open the IDE and click to the "Sketch" menu and then Include Library > Manage Libraries.



# LROBRUYA

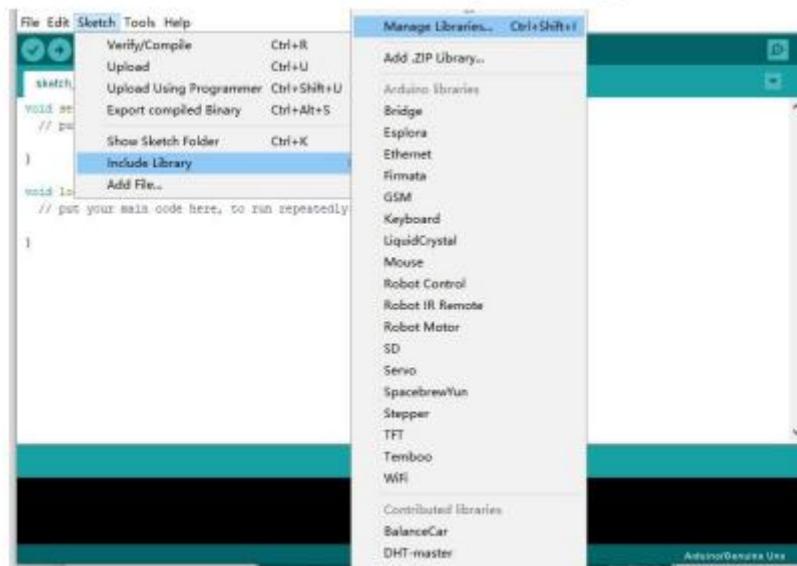

Then the library manager will open and you will find a list of libraries that are already installed or ready for installation. In this example we will install the Bridge library. Scroll the list to find it, then select the version of the library you want to install. Sometimes only one version of the library is available. If the version selection menu does not appear, don't worry: it is normal.

**There are times you have to be patient with it, just as shown in the figure. Please refresh it and wait.**

# LROBRUYA

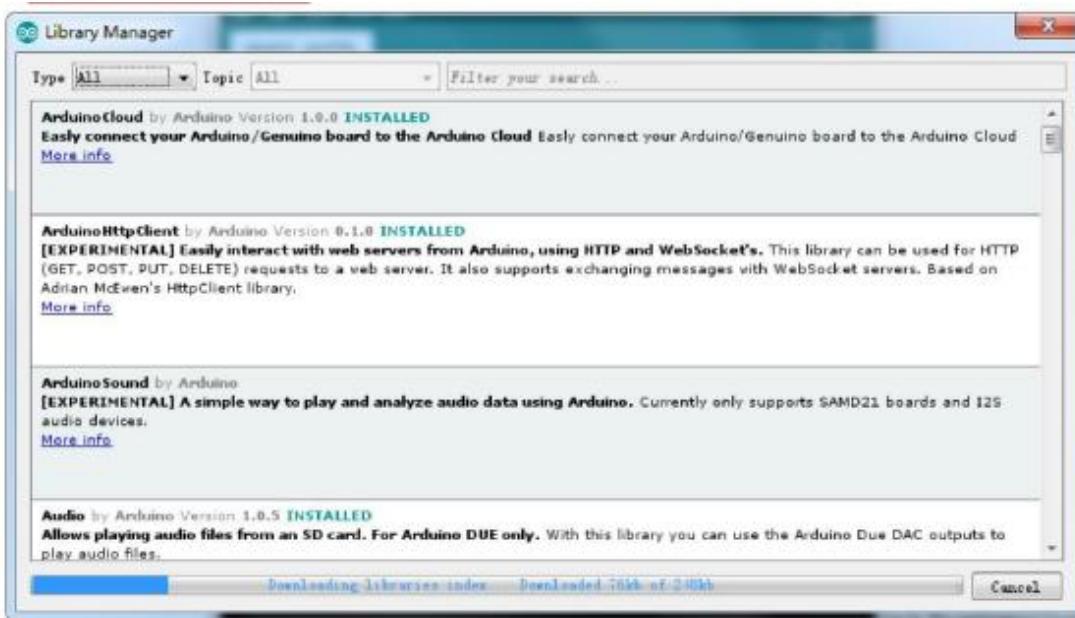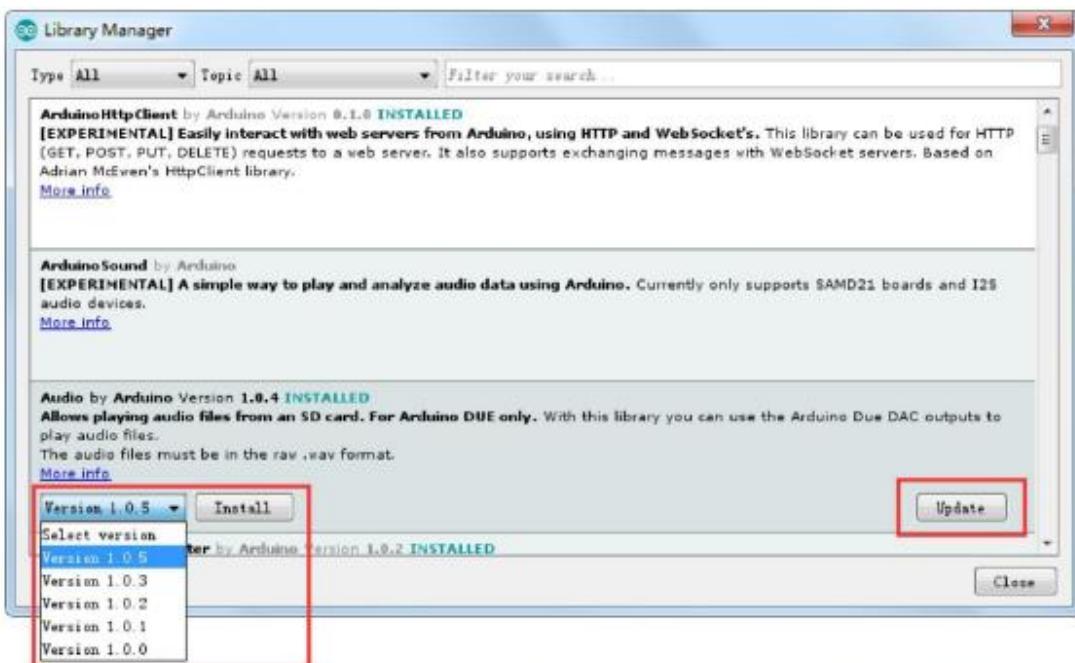

Finally click on install and wait for the IDE to install the new library.

Downloading may take time depending on your connection speed. Once it has finished, an Installed tag should appear next to the Bridge library.

You can close the library manager.

# LROBRYA



You can now find the new library available in the Include Library menu.


If you want to add your own library open a new issue on [Github](#).

## Importing a .zip Library

Libraries are often distributed as a ZIP file or folder. The name of the folder is the name of the library. Inside the folder will be a .cpp file, a .h file and often a keywords.txt file, examples folder, and other files required by the library. Starting with version 1.0.5, you can install 3rd party libraries in the IDE. Do not unzip the downloaded library, leave it as is.

In the Arduino IDE, navigate to Sketch > Include Library. At the top of the drop down list, select the option to "Add .ZIP Library".


# LROBRUYA

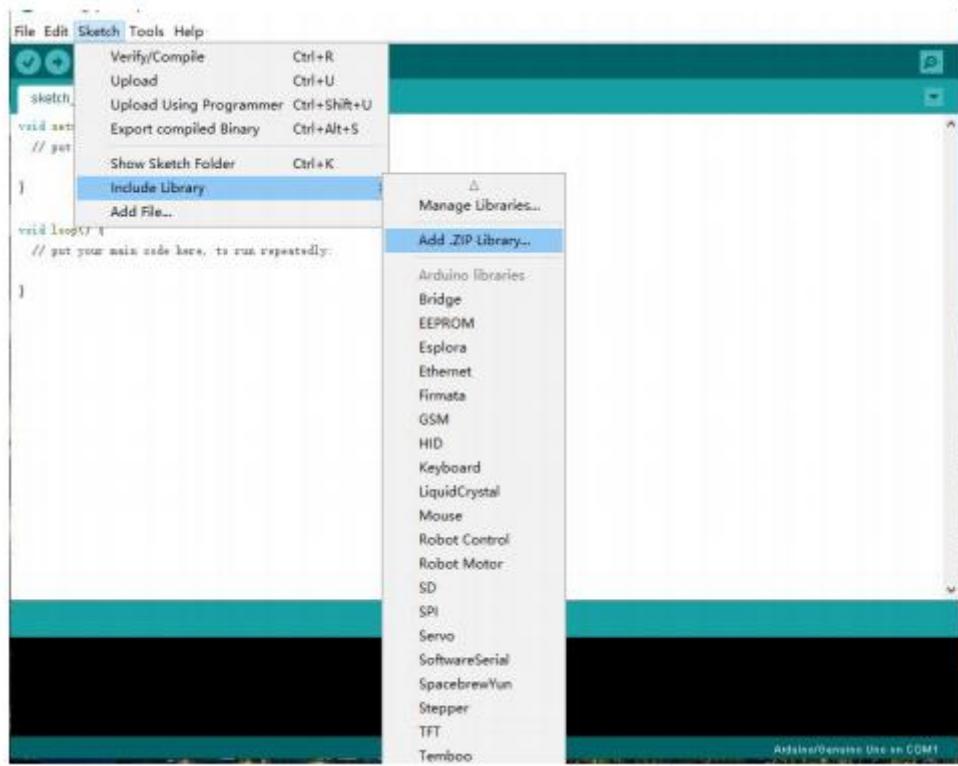

You will be prompted to select the library you would like to add.

Navigate to the .zip file's location and open it.

# LROBRUYA

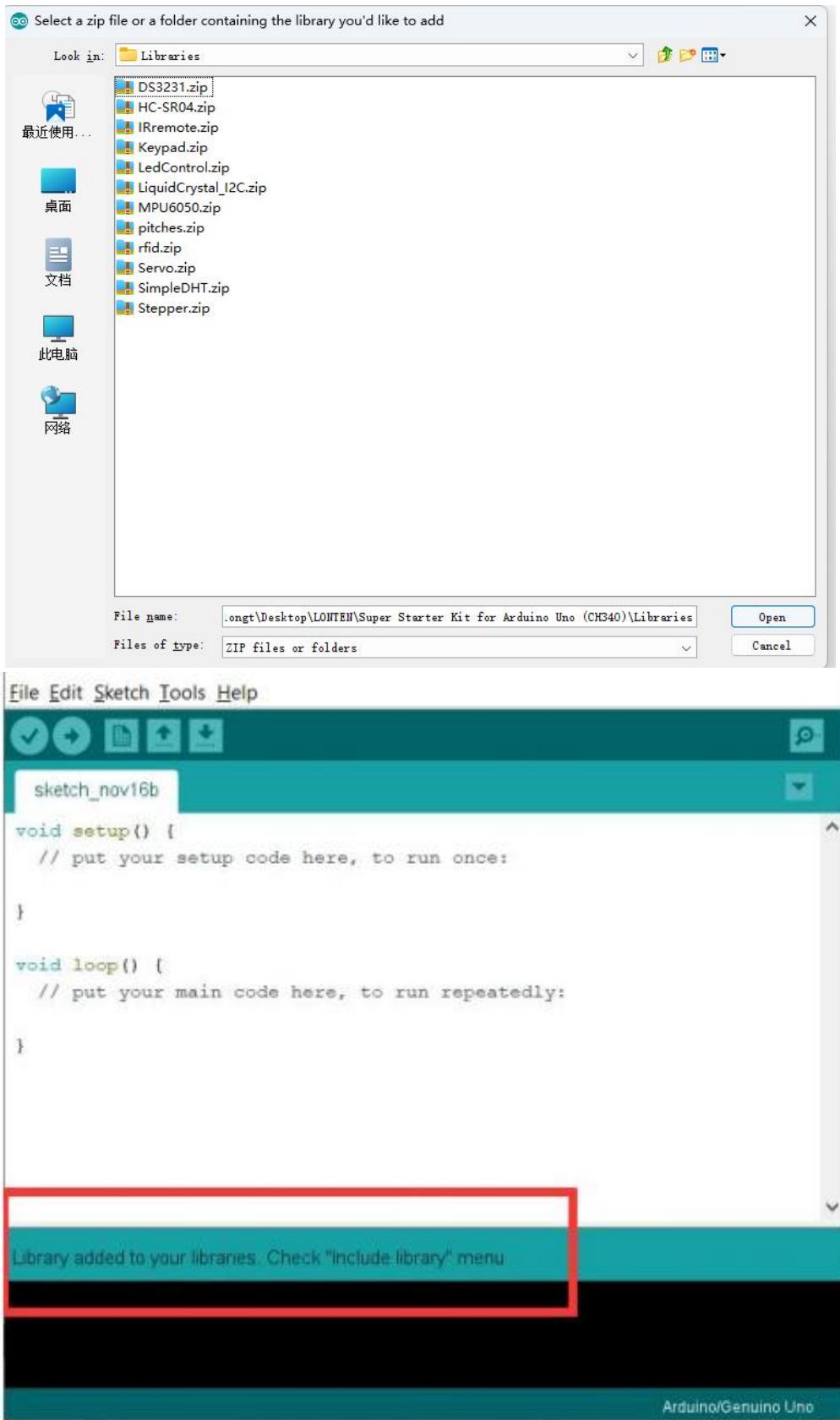



---

Return to the Sketch > Import Library menu. You should now see the library at the bottom of the drop-down menu. It is ready to be used in your sketch. The zip file will have been expanded in the libraries folder in your Arduino sketches directory. NB: the Library will be available to use in sketches, but examples for the library will not be exposed in the File > Examples until after the IDE has restarted.


### **Arduino Serial Monitor (Windows, Mac, Linux)**

The Arduino Integrated Development Environment (IDE) is the software side of the Arduino platform. And, because using a terminal is such a big part of working with Arduinos and other microcontrollers, they decided to include a serial terminal with the software. Within the Arduino environment, this is called the Serial Monitor.

### **Making a Connection**

Serial monitor comes with any and all version of the Arduino IDE. To open it, simply click the Serial Monitor icon.


# LROBRYA

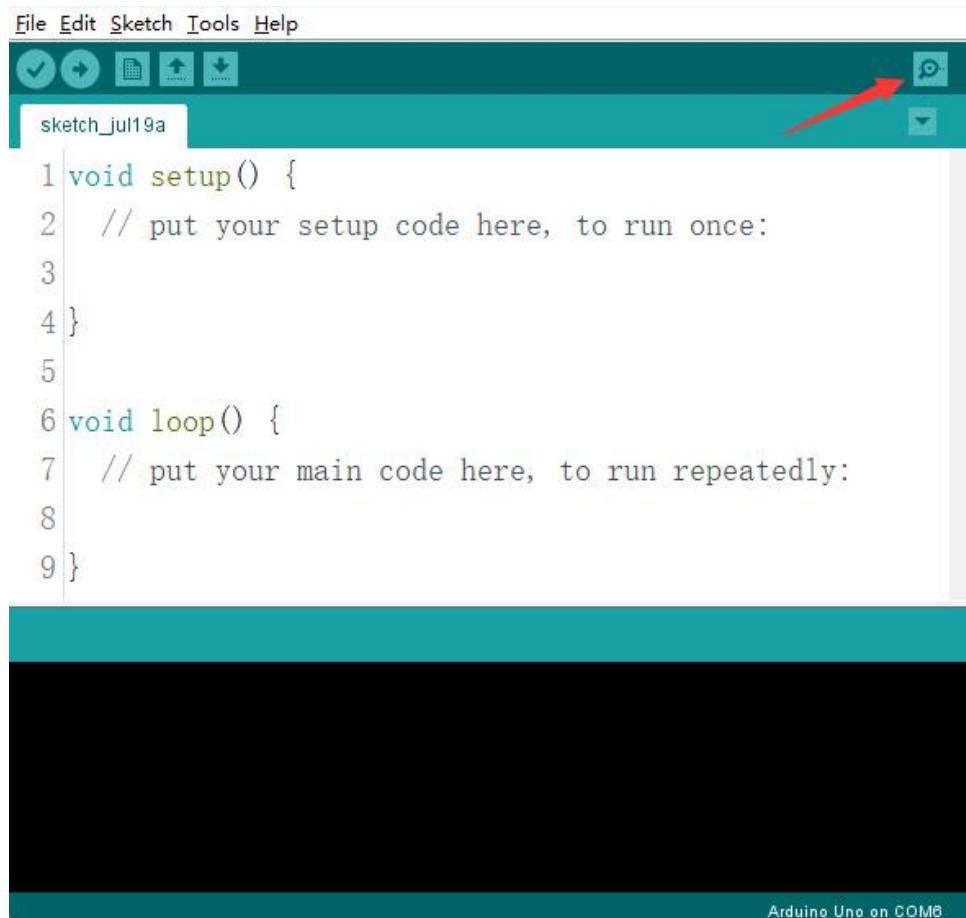


Selecting which port to open in the Serial Monitor is the same as selecting a port for uploading Arduino code. Go to Tools -> Serial Port, and select the correct port.

**Tips:** Choose the same COM port that you have in Device Manager.

# LROBRYA

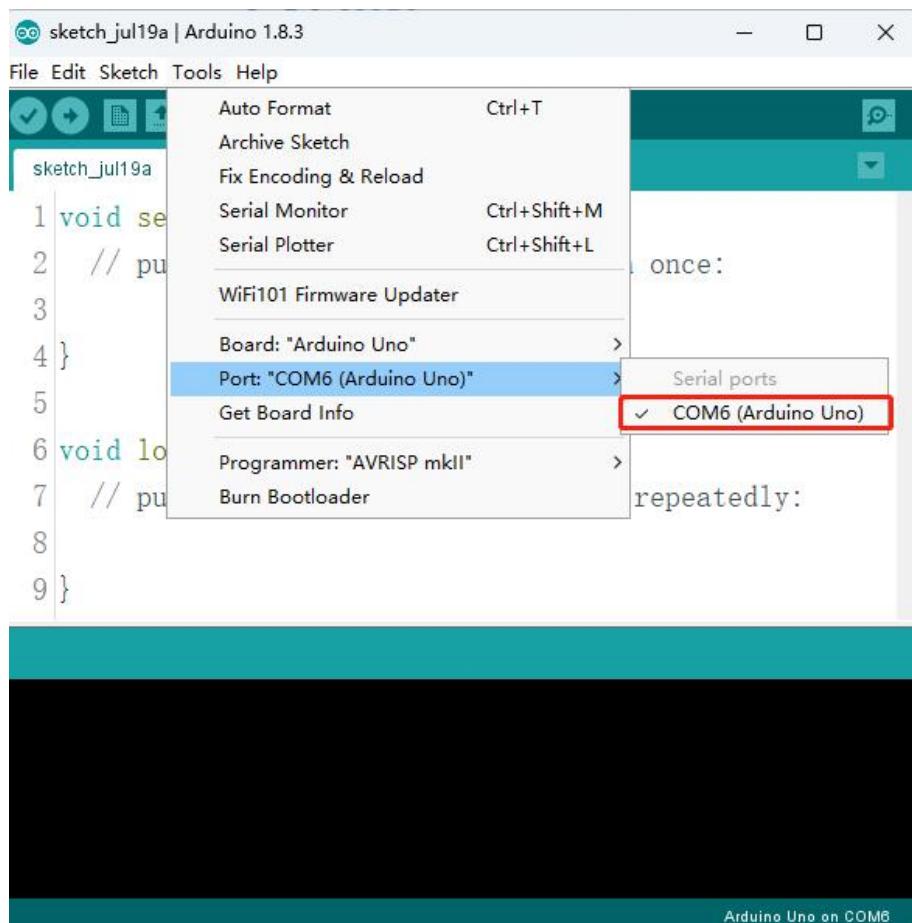

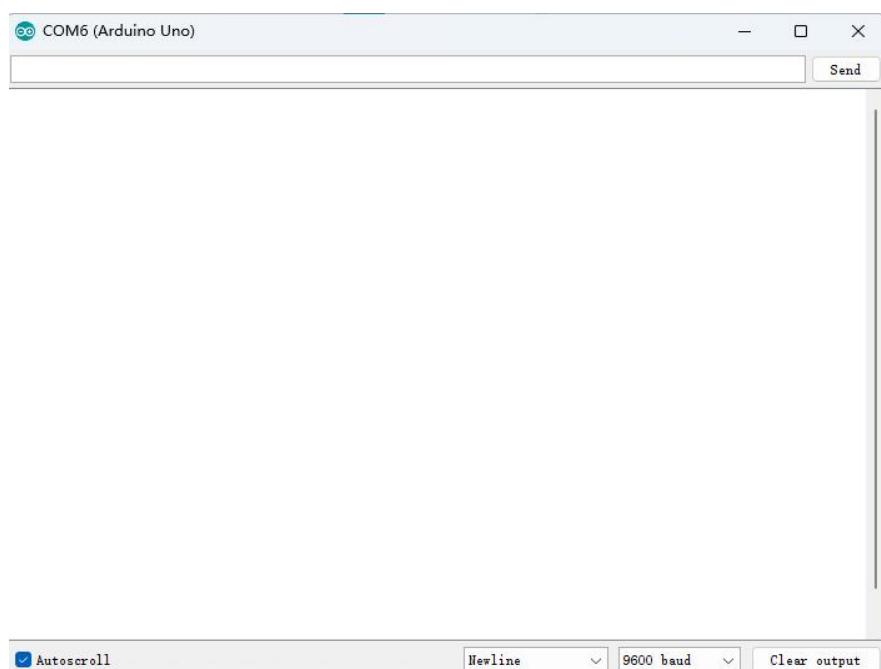Once open, you should see something like this:




# LROBRYA

---
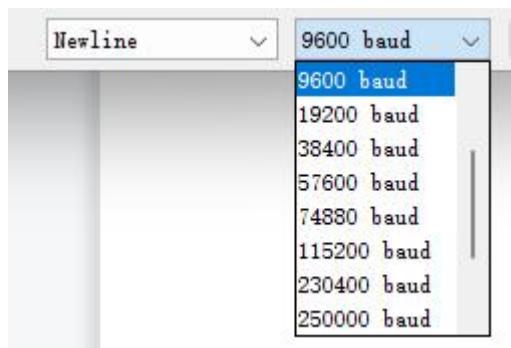
## Settings

The Serial Monitor has limited settings, but enough to handle most of your serial communication needs. The first setting you can alter is the baud rate. Click on the baud rate drop-down menu to select the correct baud rate. (9600 baud)



Last, you can set the terminal to Autoscroll or not by checking the box in the bottom left corner.



## Pros

The Serial Monitor is a great quick and easy way to establish a serial connection with your Arduino. If you're already working in the Arduino IDE, there's really no need to open up a separate terminal to display data.

## Cons

The lack of settings leaves much to be desired in the Serial Monitor, and, for advanced serial communications, it may not do the trick.



---

## Blink Test

### Overview

In this Project, you will learn how to program your UNO R3 controller board to blink the Arduino's built-in LED, and how to download programs by basic steps.

### Component Required:

LONTEN Uno R3 Board\* 1


### Principle

The UNO R3 board has rows of connectors along both sides that are used to connect to several electronic devices and plug-in 'shields' that extends its capability.

It also has a single LED that you can control from your sketches. This LED is built onto the UNO R3 board and is often referred to as the 'L' LED as this is how it is labeled on the board.

# LROBRYA

---

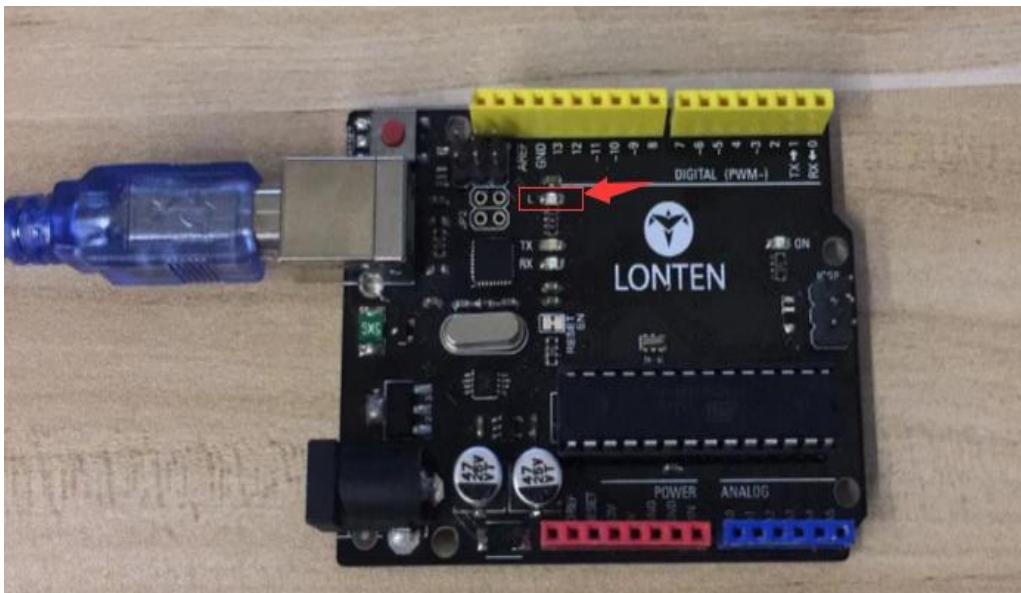


In this Project, we will reprogram the UNO board with our own Blink sketch and then change the rate at which it blinks.

In the previous chapter-How to install Arduino IDE, you set up your Arduino IDE and made sure that you could find the right serial port for it to connect to your UNO board. The time has now come to put that connection to the test and program your UNO board.

The Arduino IDE includes a large collection of example sketches that you can load up and use. This includes an example sketch for making the 'L' LED blink.


Load the 'Blink' sketch that you will find in the IDE's menu system under File > Examples > 01.Basics > Blink

# LROBRUYA

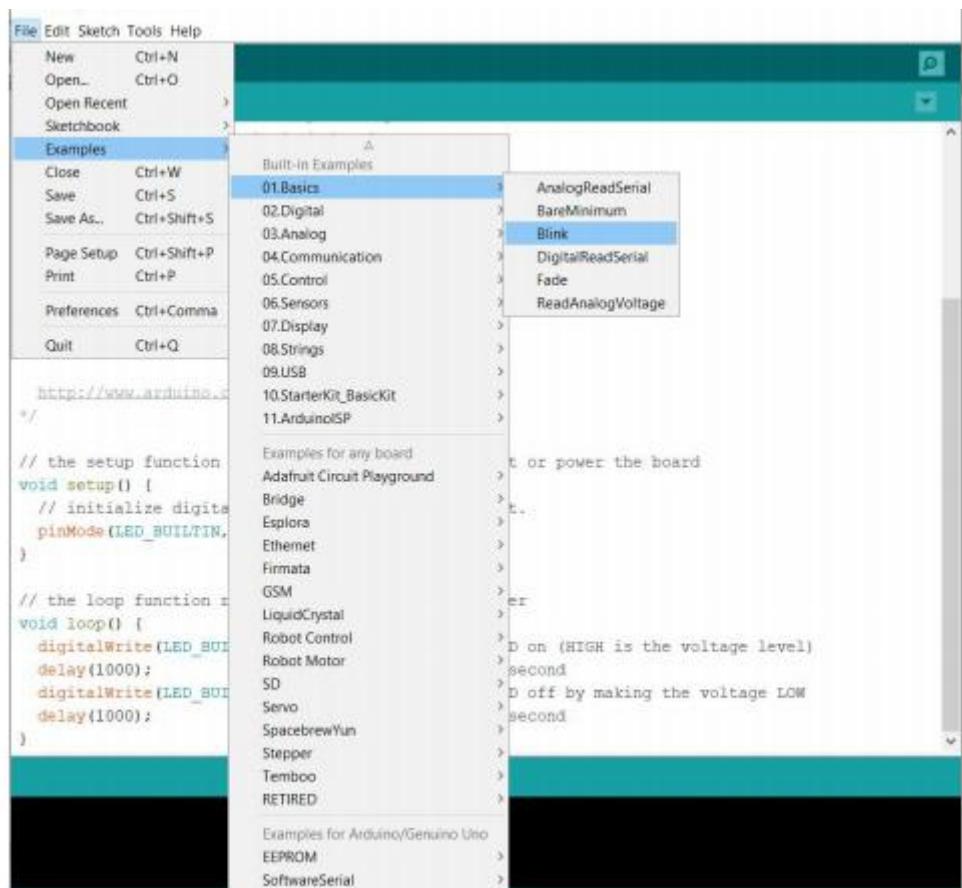

When the sketch window opens, enlarge it so that you can see the entire sketch in the window.

# LROBRUYA


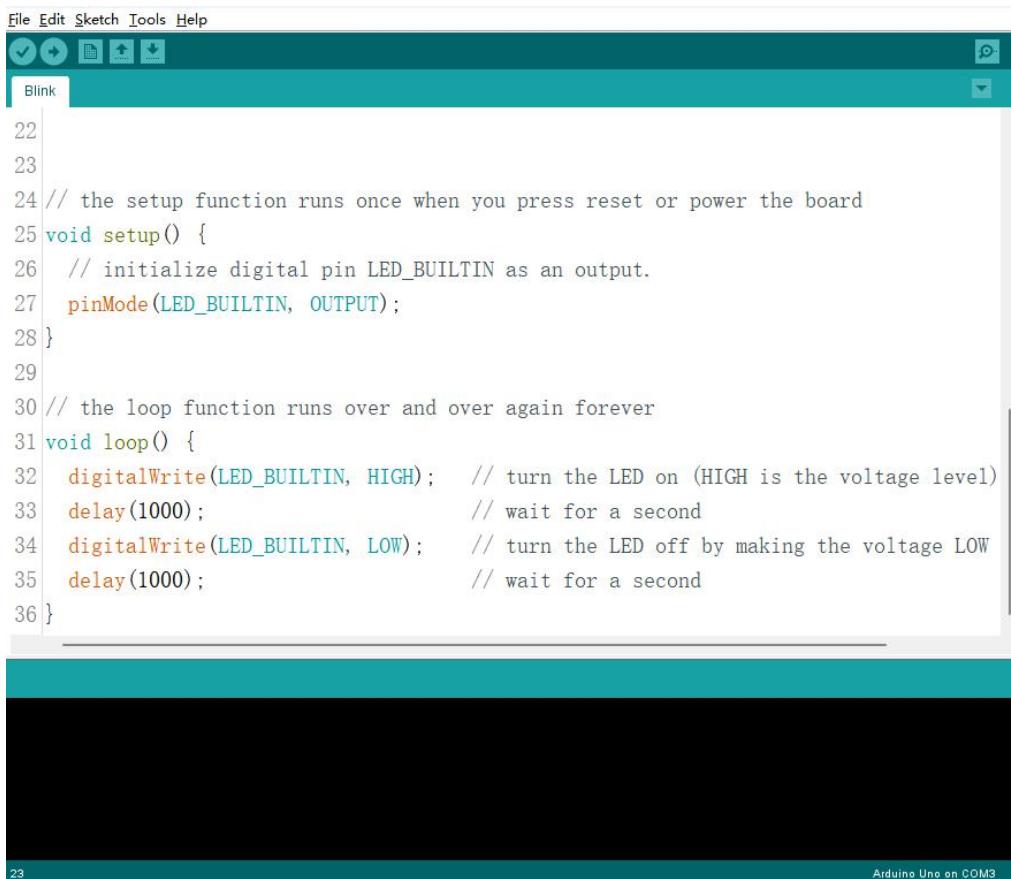


The screenshot shows the Arduino IDE interface. The menu bar includes File, Edit, Sketch, Tools, and Help. The toolbar has icons for Open, Save, Print, and Upload. A status bar at the bottom right says "Arduino Uno on COM3". The code editor contains the standard "Blink" sketch:


```
File Edit Sketch Tools Help
Blink
22
23
24 // the setup function runs once when you press reset or power the board
25 void setup() {
26   // initialize digital pin LED_BUILTIN as an output.
27   pinMode(LED_BUILTIN, OUTPUT);
28 }
29
30 // the loop function runs over and over again forever
31 void loop() {
32   digitalWrite(LED_BUILTIN, HIGH);    // turn the LED on (HIGH is the voltage level)
33   delay(1000);                      // wait for a second
34   digitalWrite(LED_BUILTIN, LOW);     // turn the LED off by making the voltage LOW
35   delay(1000);                      // wait for a second
36 }
```

Attach your Arduino board to your computer with the USB cable and check that the 'Board Type' and 'Serial Port' are set correctly.

# LROBRUYA

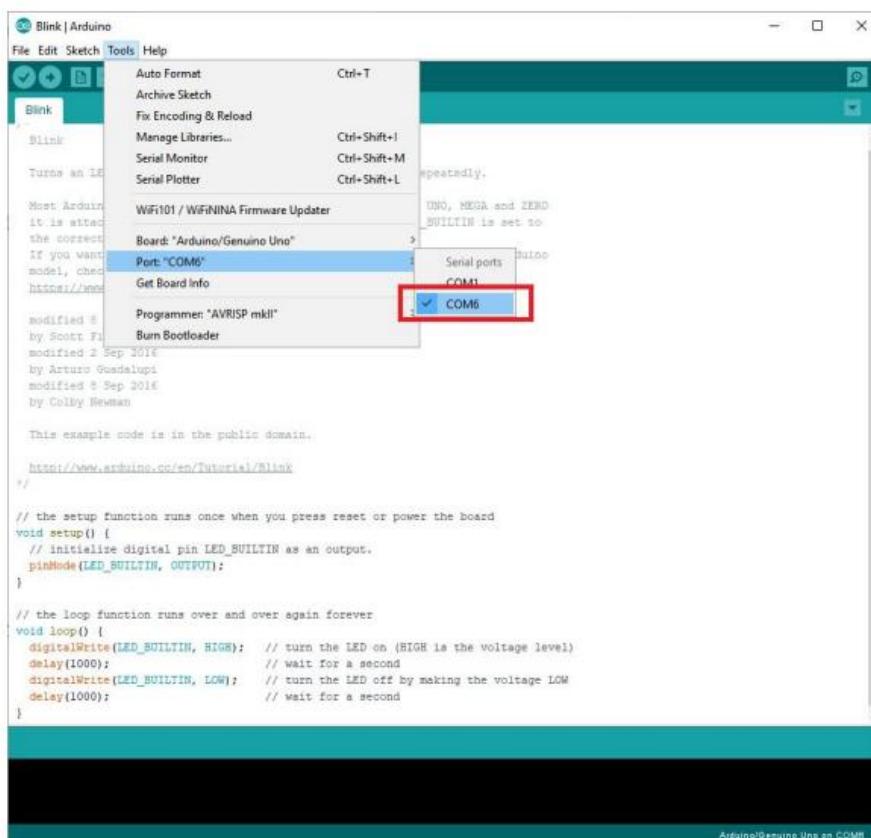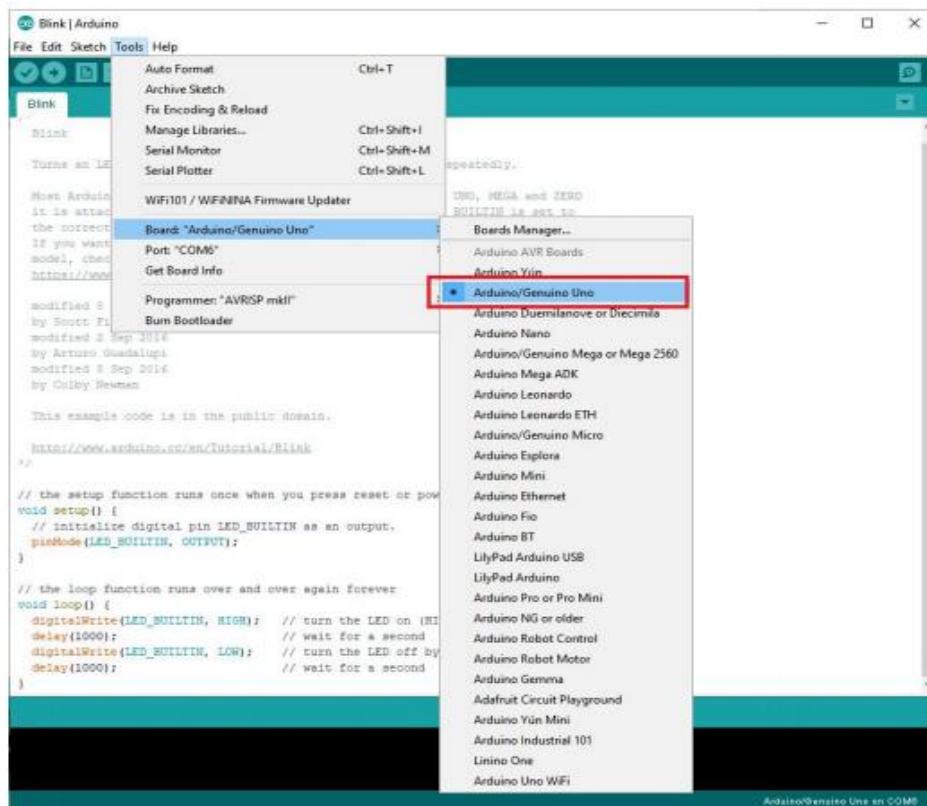

# LROBRUYA

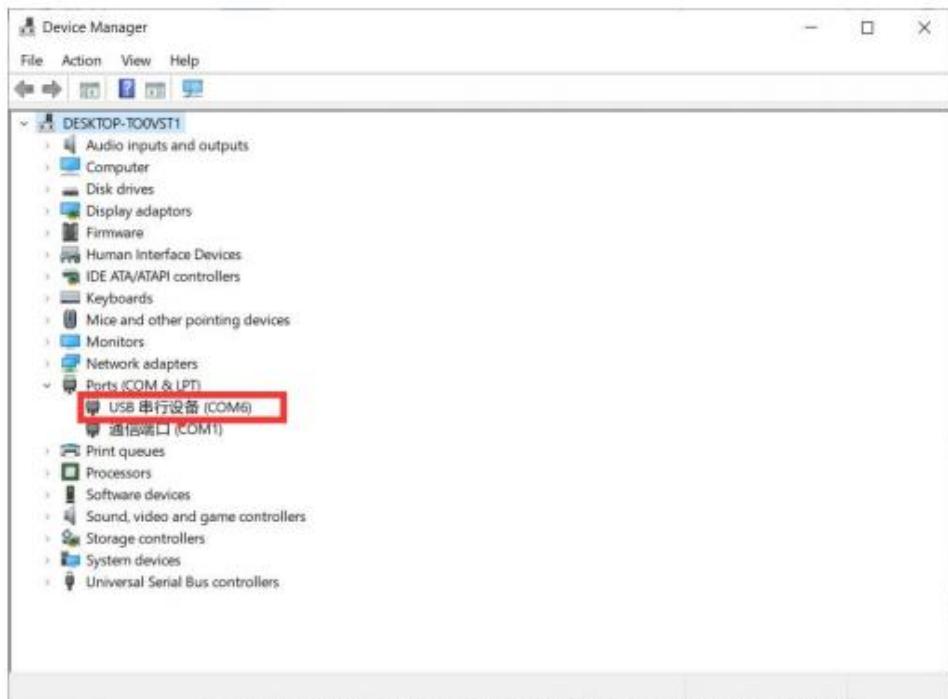

**Note: The Board Type and Serial Port here are not necessarily the same as shown in picture. If you are using UNO, then you will have to choose Arduino UNO as the Board Type, other choices can be made in the same manner. And the Serial Port displayed for everyone is different, despite COM 6 chosen here, it could be COM3 or COM4 on your computer. A right COM port is supposed to be COMX (arduino XXX), which is by the certification criteria.**


The Arduino IDE will show you the current settings for board at the bottom of the window.


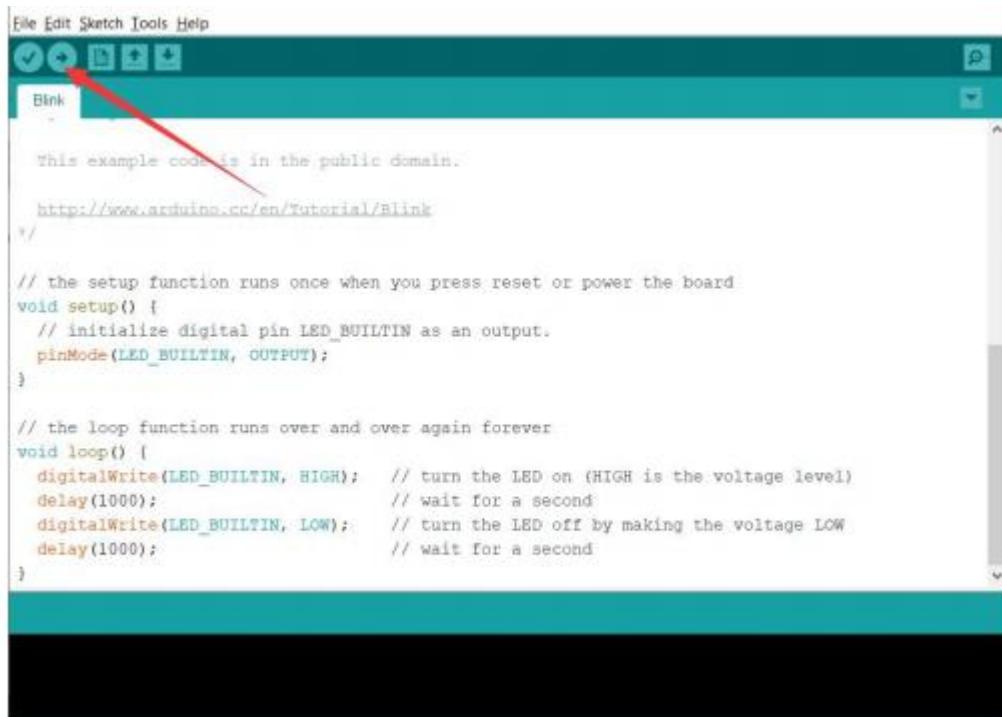
# LROBRUYA


---

Click on the 'Upload' button. The second button from the left on the toolbar.



When the status bar prompts "Done uploading", it means the code upload is successful

# LROBRUYA

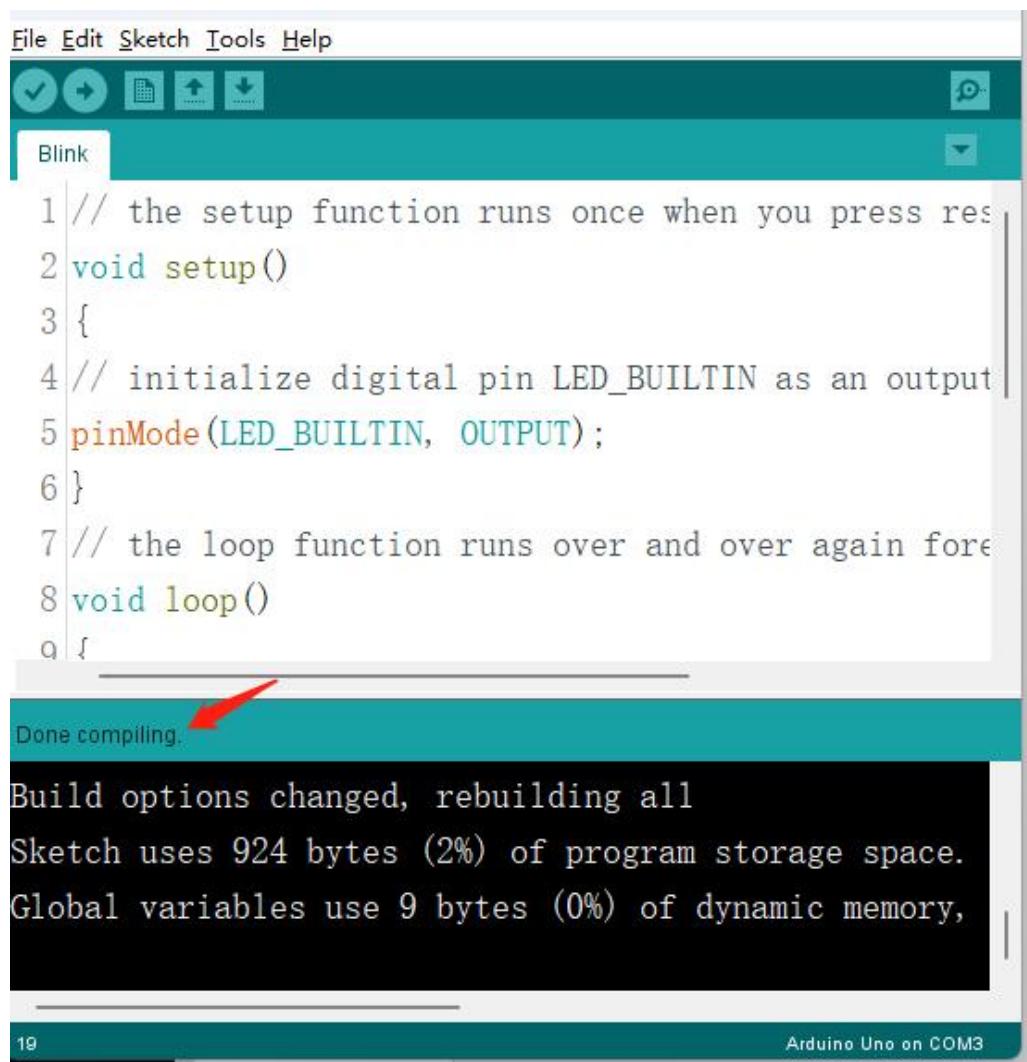

The screenshot shows the Arduino IDE interface. The top menu bar includes File, Edit, Sketch, Tools, and Help. Below the menu is a toolbar with icons for upload, download, and other functions. A dropdown menu shows "Blink". The main area contains the following sketch code:

```
1 // the setup function runs once when you press res
2 void setup()
3 {
4 // initialize digital pin LED_BUILTIN as an output
5 pinMode(LED_BUILTIN, OUTPUT);
6 }
7 // the loop function runs over and over again forever
8 void loop()
9 {
```

Below the code, a status bar displays "Done compiling." with a red arrow pointing to it. The bottom status bar also shows "Done compiling." and "Arduino Uno on COM3".

If an error message appears.



The screenshot shows the Arduino IDE interface with an error message displayed in the central window. The message reads:

```
Problem uploading to board. See http://www.arduino.cc/en/Guide/Troubleshooting#upload for suggestions.
An error occurred while uploading the sketch
avrduude: ser_open(): can't open device "\.\COM15": The system cannot find the file specified.
```

The bottom status bar shows "ArduinoGenuine Uno on COM15".


There can be several reasons:

1. The arduino uno driver software is not installed successfully, please refer to the course for the installation steps: "[How to Install Arduino](#)

# LROBRYA

Driver".

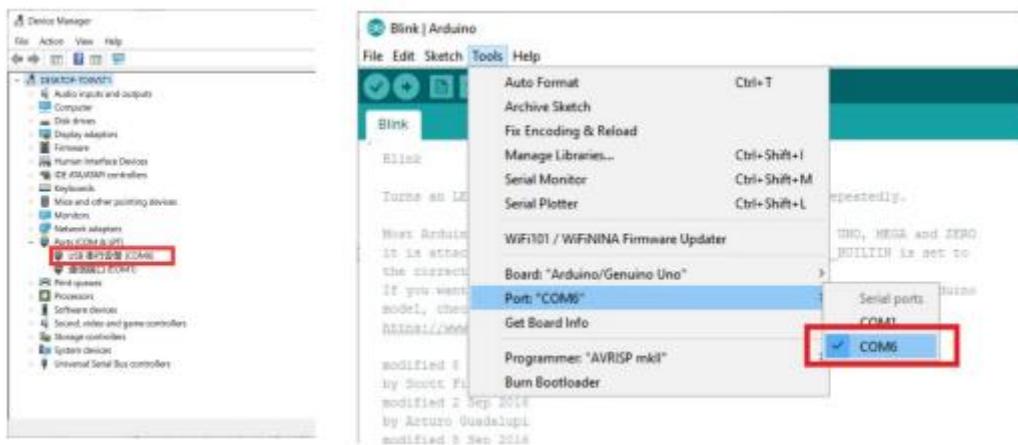2. The communication serial port selection of arduino uno is wrong; you can check the communication port COMx of your arduino uno in the computer in the device manager.



3. If your Arduino uno is connected to a Bluetooth module, it will occupy the communication serial port. You need to remove the Bluetooth module connection before uploading the code.

4. The USB data cable is not firmly connected.

Check if there are any of the above problems. After correcting, follow the previous steps to re-operate.

## Sample Program


```
// the setup function runs once when you press reset or power the board  
void setup()  
{
```



```
// initialize digital pin LED_BUILTIN as an output.  
  
pinMode(LED_BUILTIN, OUTPUT);  
  
}  
  
// the loop function runs over and over again forever  
  
void loop()  
  
{  
  
    digitalWrite(LED_BUILTIN, HIGH);  
  
    // turn the LED on (HIGH is the voltage level)  
  
    delay(1000);  
  
    // wait for a second  
  
    digitalWrite(LED_BUILTIN, LOW);  
  
    // turn the LED off by making the voltage LOW  
  
    delay(1000);  
  
    // wait for a second  
  
}
```

# LROBRYA

---

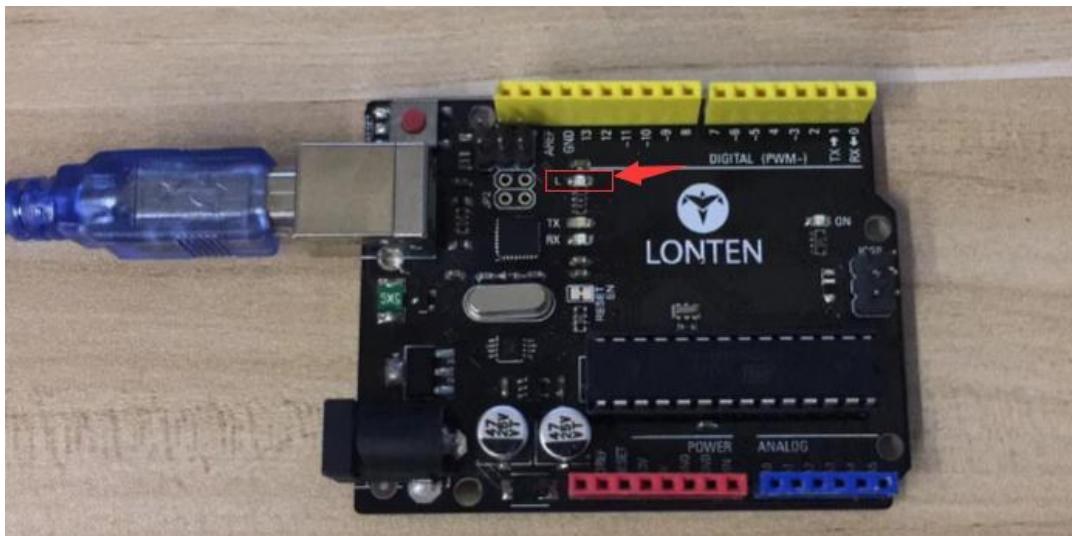

After the code is successfully uploaded, the "L" character LED will flash once per second. So far, you have completed the testing process of your first program.

## Lesson 1 LED

### Overview

In this lesson, you will learn how to change the brightness of an LED by using different values of resistor.

### Component Required:

(1) x LONTEN Uno R3 Board

(1) x 5mm red LED

(1) x 220 ohm resistor

(1) x 1k ohm resistor

(1) x 10k ohm resistor

# LROBRYA


---

(2) x M-M wires (Male to Male jumper wires)

## Component Introduction
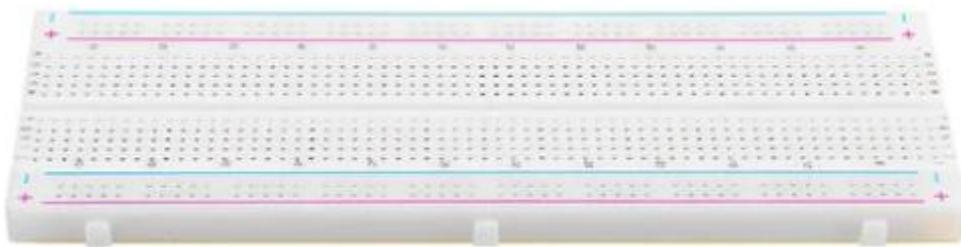
### BREADBOARD MB-102:

A breadboard enables you to prototype circuits quickly, without having to solder the connections. Below is an example.



Breadboards come in various sizes and configurations. The simplest kind is just a grid of holes in a plastic block. Inside are strips of metal that provide electrical connection between holes in the shorter rows. Pushing the legs of two different components into the same row joins them together electrically. A deep channel running down the middle indicates that there is a break in connections there, meaning, you can push a chip in with the legs at either side of the channel without connecting them together. Some breadboards have two strips of holes running along the long edges of the board that are separated from the main grid. These have strips running down the length of the board inside and provide a way to connect a common voltage. They are usually in pairs for +5 volts and

# LROBRYA

---

ground. These strips are referred to as rails and they enable you to connect power to many components or points in the board.

While breadboards are great for prototyping, they have some limitations. Because the connections are push-fit and temporary, they are not as reliable as soldered connections. If you are having intermittent problems with a circuit, it could be due to a poor connection on a breadboard.

## LED:

LEDs make great indicator lights. They use very little electricity and they pretty much last forever.

In this Lesson, you will use perhaps the most common of all LEDs: a 5mm red LED. 5mm refers to the diameter of the LED. Other common sizes are 3mm and 10mm. You cannot directly connect an LED to a battery or voltage source because 1) the LED has a positive and a negative lead and will not light if placed the wrong way and 2) an LED must be used with a resistor to limit or ‘choke’ the amount of current flowing through it; otherwise, it will burn out!



# LROBRYA

---

If you do not use a resistor with an LED, then it may well be destroyed almost immediately, as too much current will flow through, heating it and destroying the ‘junction’ where the light is produced.

There are two ways to tell which is the positive lead of the LED and which the negative.

Firstly, the positive lead is longer.

Secondly, where the negative lead enters the body of the LED, there is a flat edge to the case of the LED.

If you happen to have an LED that has a flat side next to the longer lead, you should assume that the longer lead is positive.

## RESISTORS:

As the name suggests, resistors resist the flow of electricity. The higher the value of the resistor, the more it resists and the less electrical current will flow through it. We are going to use this to control how much electricity flows through the LED and therefore, how brightly it shines.



But first, more about resistors...

The unit of resistance is called the Ohm, which is usually shortened to  $\Omega$  the Greek letter Omega. Because an Ohm is a low value of resistance (it doesn't resist much at all), we also denote the values of resistors in K $\omega$  (1,000  $\Omega$ ) and M $\Omega$  (1,000,000  $\Omega$ ).



---


These are called kilo-ohms and mega-ohms.

In this learning kit, we are going to use three different values of resistor:

**220Ω, 1KΩ and 10KΩ**. These resistors all look the same, except that they have different colored stripes on them. These stripes tell you the value of the resistor.

The resistor color code has three colored stripes and then a gold stripe at one end.

# LROBRUYA

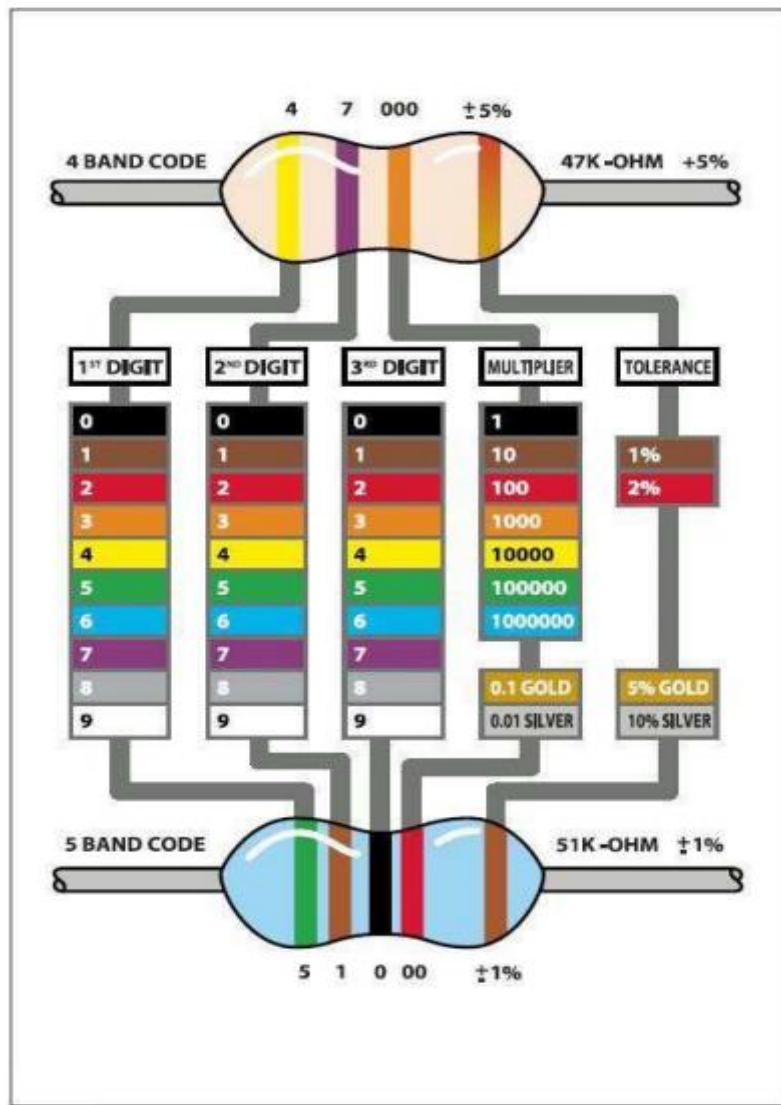

Unlike LEDs, resistors do not have a positive and negative lead. They can be connected either way around.

If you find this approach method too complicated, you can read the color ring flag on our resistors directly to determine its resistance value. Or you may use a digital multimeter instead.


We follow below diagram from the experimental schematic link. Here we

# LROBRYA

use digital pin 10. We connect LED to a 220-ohm resistor to avoid high current damaging the LED.


## Connection

### Schematic

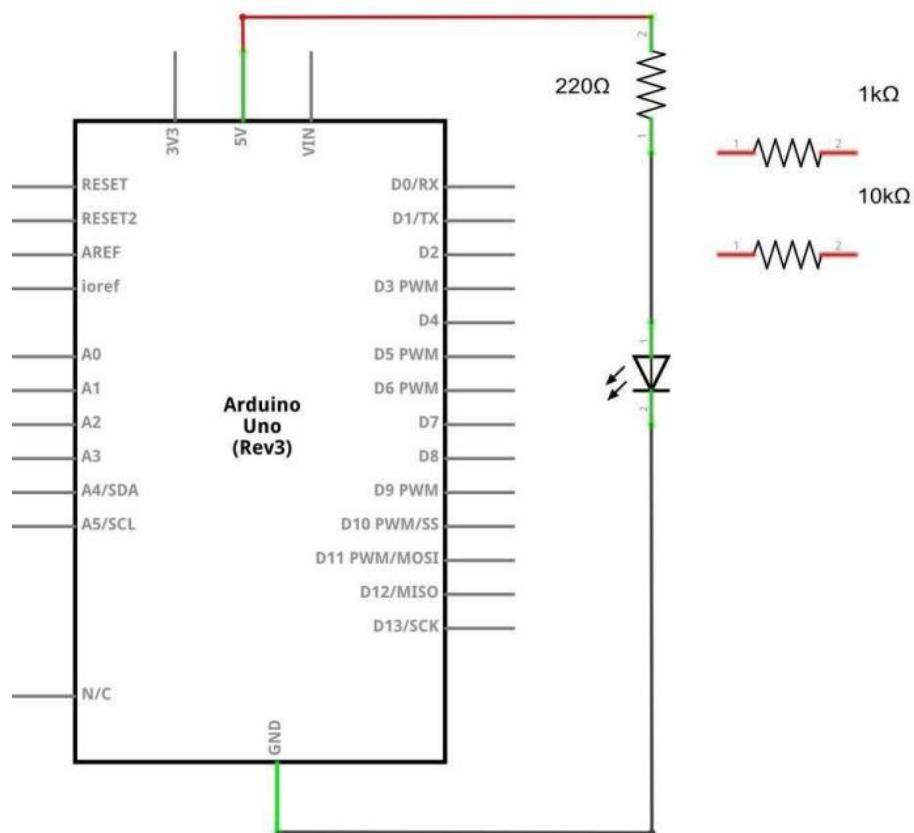

## Circuit Connection

# LROBRYA

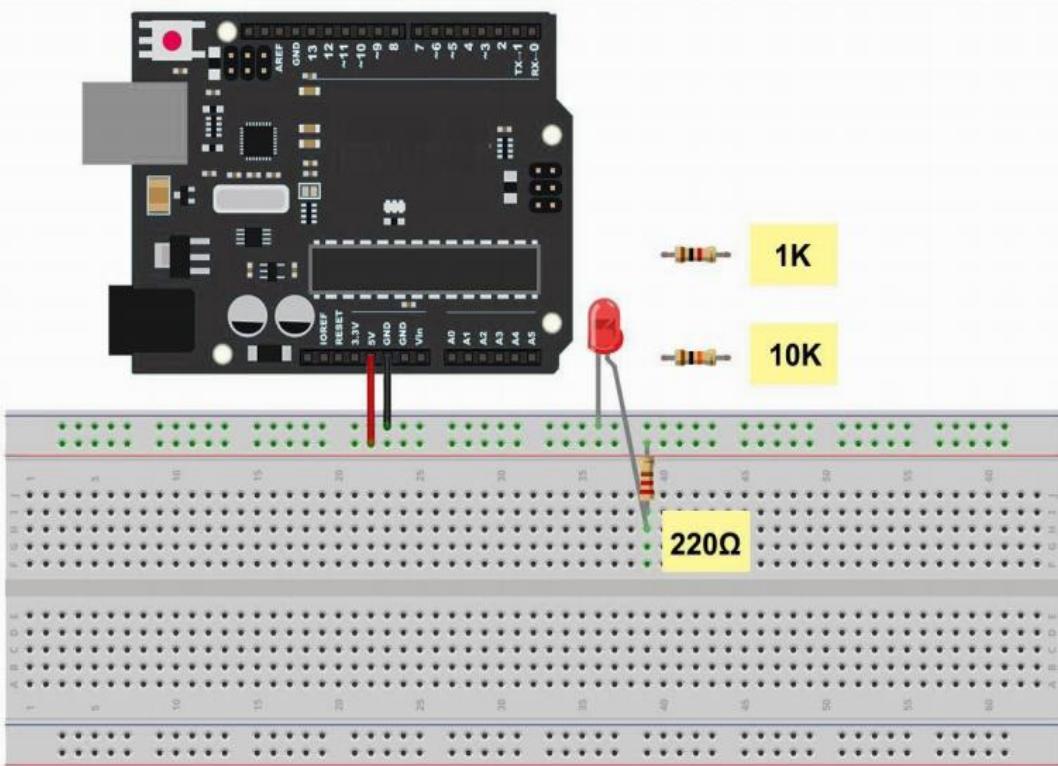

The UNO is a convenient source of 5 volts, which we will use to provide power to the LED and the resistor. You do not need to do anything with your UNO, except to plug it into a USB cable.

With the  $220\ \Omega$  resistor in place, the LED should be quite bright. If you swap out the  $220\ \Omega$  resistor for the  $1k\ \Omega$  resistor, then the LED will appear a little dimmer. Finally, with the  $10\ k\ \Omega$  resistor in place, the LED will be just about visible. Pull the red jumper lead out of the breadboard and touch it into the hole and remove it, so that it acts like a switch. You should just be able to notice the difference.


At the moment, you have 5V going to one leg of the resistor, the other leg of the resistor going to the positive side of the LED and the other side of

# LROBRYA

---

the LED going to GND. However, if we moved the resistor so that it came after the LED, as shown below, the LED will still light. You will probably want to put the  $220\ \Omega$  resistor back in place. It does not matter which side of the LED we put the resistor, as long as it is there somewhere.

## Example picture

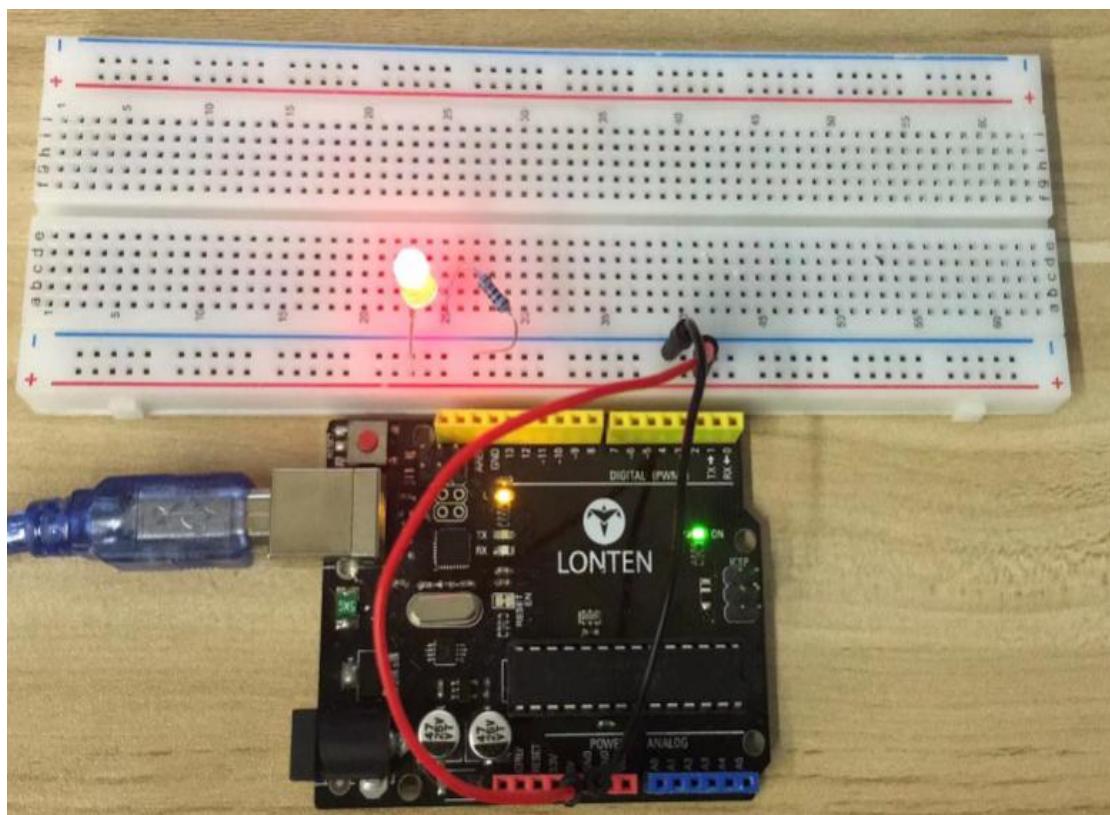



---

## Lesson 2 RGB LED

### Overview

RGB LEDs are a fun and easy way to add some color to your projects.

Since they are like 3 regular LEDs in one, how to use and connect them is not much different.

They come mostly in 2 versions: Common Anode or Common Cathode.

Common Anode uses 5V on the common pin, while Common Cathode connects to ground.

As with any LED, we need to connect some resistors inline (3 total) so we can limit the current being drawn.

In our sketch, we will start with the LED in the Red color state, then fade to Green, then fade to Blue and finally back to the Red color. By doing this we will cycle through most of the color that can be achieved.





---

## **Component Required:**

- (1) x LONTEN Uno R3
- (1) x 830 Tie Points Breadboard
- (4) x M-M wires (Male to Male jumperwires)
- (1) x RGB LED
- (3) x 220 ohm resistors

## **Component Introduction**


### **RGB LED:**

At first glance, RGB (Red, Green and Blue) LEDs look just like regular LEDs. However, inside the usual LED package, there are actually three LEDs, one red, one green and one blue. By controlling the brightness of each of the individual LEDs you can mix pretty much any color you want. We mix colors the same way you would mix paint on a palette - by adjusting the brightness of each of the three LEDs. Fortunately for us, UNO R3 board has an analogWrite function that you can use with pins marked with a ~ to output a variable amount of power to the appropriate LEDs.

The RGB LED has four leads. There is one lead going to the positive connection of each of the single LEDs within the package and a single lead that is connected to all three negative sides of the LEDs.

# LROBRYA

---

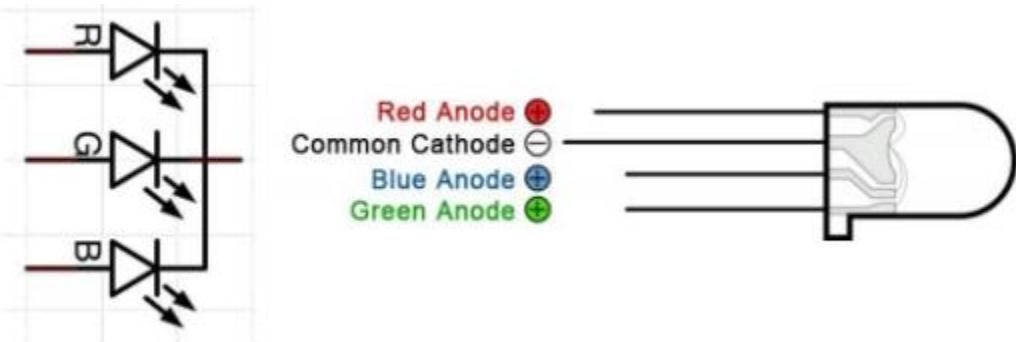

Here on the photographs you can see 4 electrode LED. Every separate pin for Green or Blue or Red color is called Anode. You will always connect “+” to it. Cathode goes to “-“(ground). If you connect it other way round the LED will not light.

The common negative connection of the LED package is the second pin from the flat side. It is also the longest of the four leads and will be connected to the ground. Each LED inside the package requires its own  $220\Omega$  resistor to prevent too much current flowing through it. The three positive leads of the LEDs (one red, one green and one blue) are connected to UNO output pins using these resistors.


## Three Primary Colors:

The reason that you can mix any color you like by varying the quantities of red, green and blue light is that your eye has three types of light receptor in it (red, green and blue). Your eye and brain process the amounts of red, green and blue and convert it into a color of the spectrum.
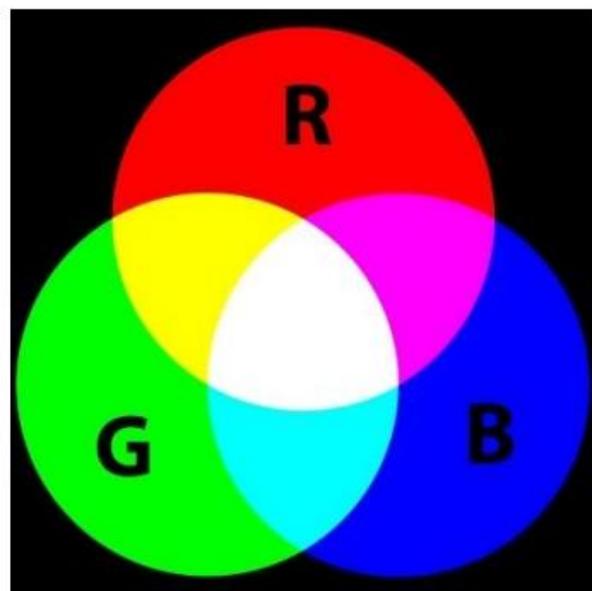
# LROBRYA

---

In a way, by using the three LEDs, we are playing a trick on the eye. This same idea is used in TVs, where the LCD has red, green and blue color dots next to each other making up each pixel.



If we set the brightness of all three LEDs to be the same, then the overall color of the light will be white. If we turn off the blue LED, so that just the red and green LEDs are the same brightness, then the light will appear yellow.

We can control the brightness of each of the red, green and blue parts of the LED separately, making it possible to mix any color we like.


Black is not so much a color as an absence of light. Therefore, the closest we can come to black with our LED is to turn off all three colors.

## Theory (PWM)
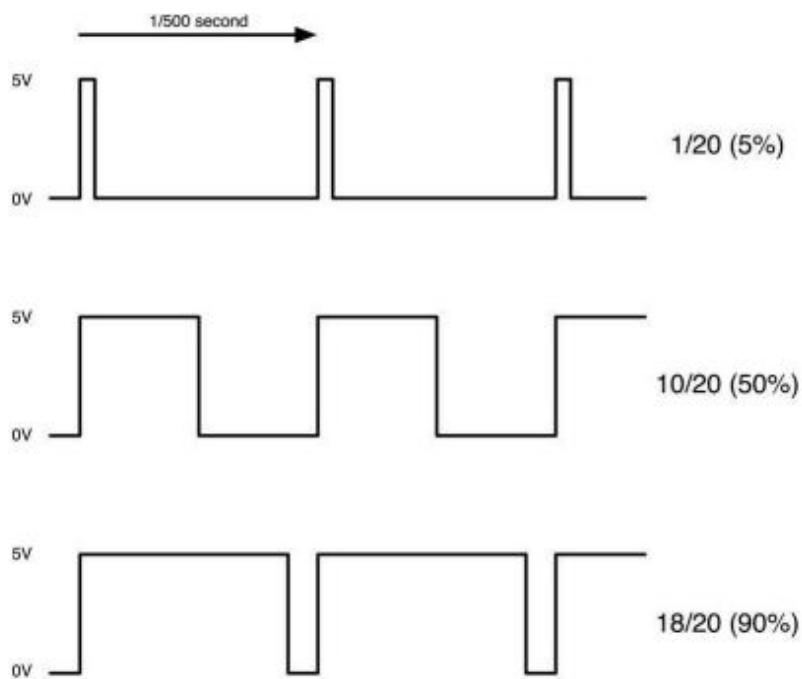
# LROBRYA

Pulse Width Modulation (PWM) is a technique for controlling power. We also use it here to control the brightness of each of the LEDs.

The diagram below shows the signal from one of the PWM pins on the UNO.



Roughly every 1/500 of a second, the PWM output will produce a pulse.

The length of this pulse is controlled by the “analogWrite” function. So “analogWrite(0)” will not produce any pulse at all and “analogWrite(255)” will produce a pulse that lasts all the way until the next pulse is due, so that the output is actually on all the time.


If we specify a value in the “analogWrite” that is somewhere in between 0 and 255, then we will produce a pulse. If the output pulse is only high for 5% of the time, then whatever we are driving will only receive 5% of

# LROBRYA

full power. If, however, the output is at 5V for 90% of the time, then the load will get 90% of the power delivered to it. We cannot see the LEDs turning on and off at that speed, so to us, it just looks like the brightness is changing.


## Connection

### Schematic

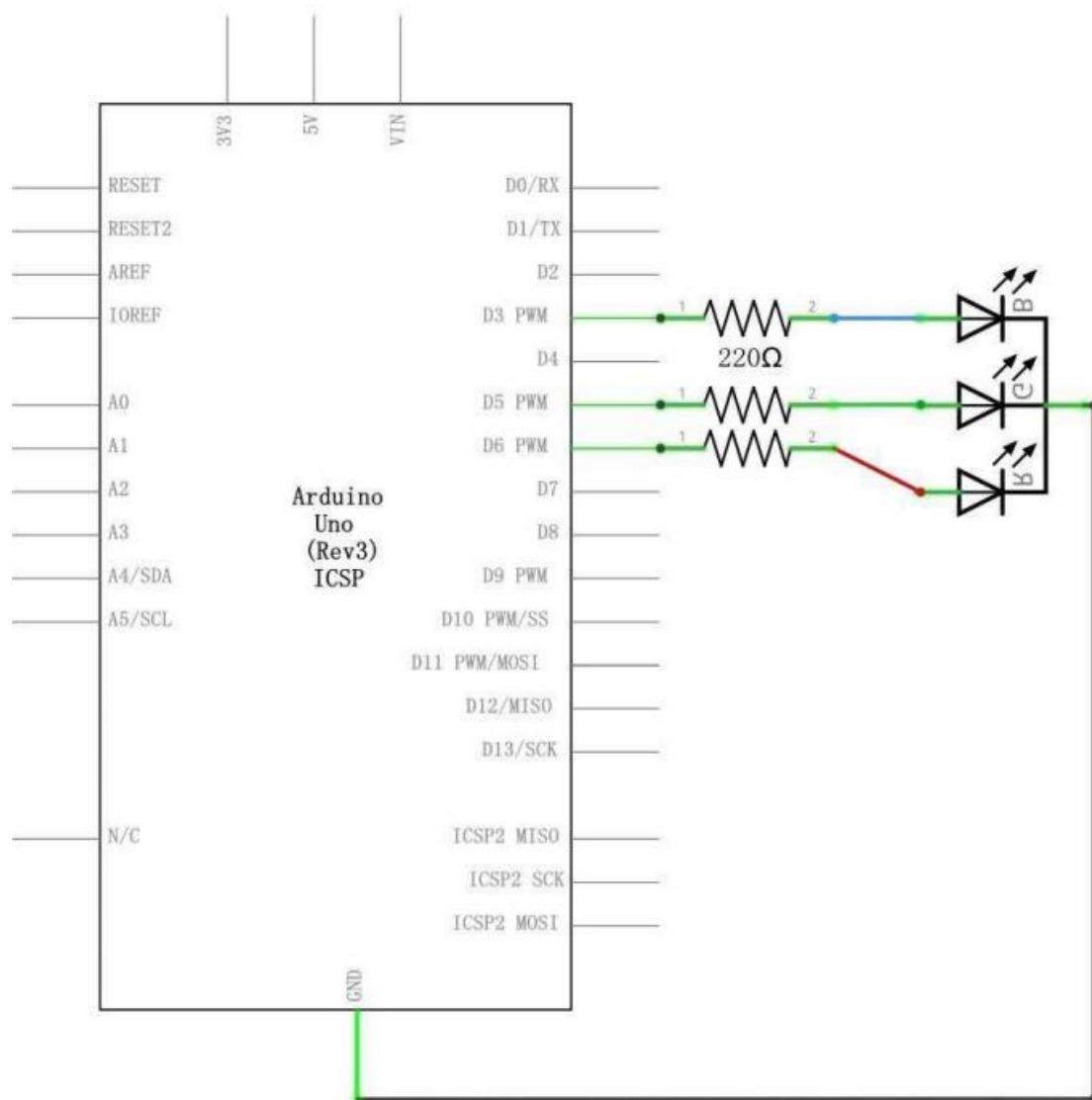


# LROBRUYA

## Circuit Connection

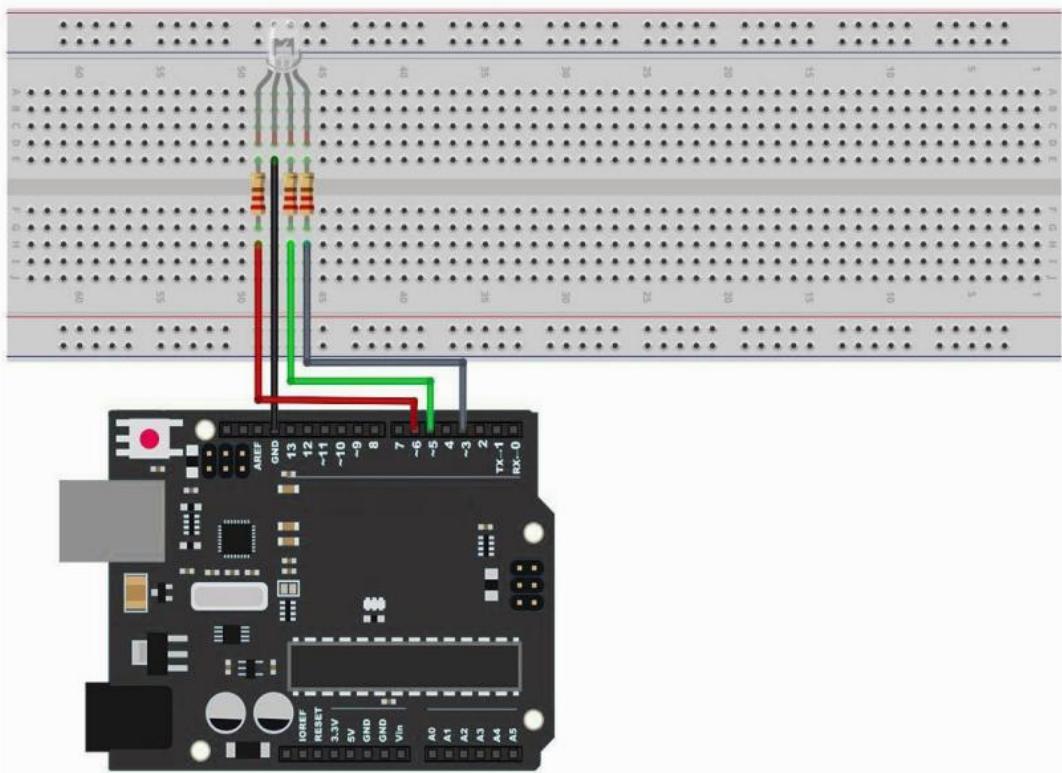


## Example picture

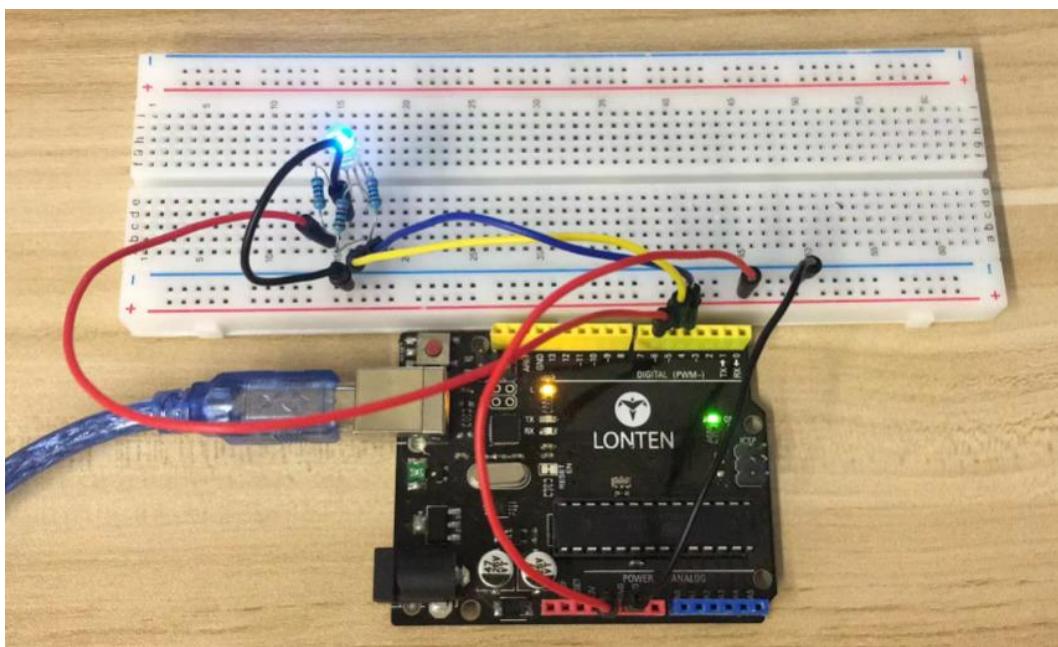

# LROBRYA
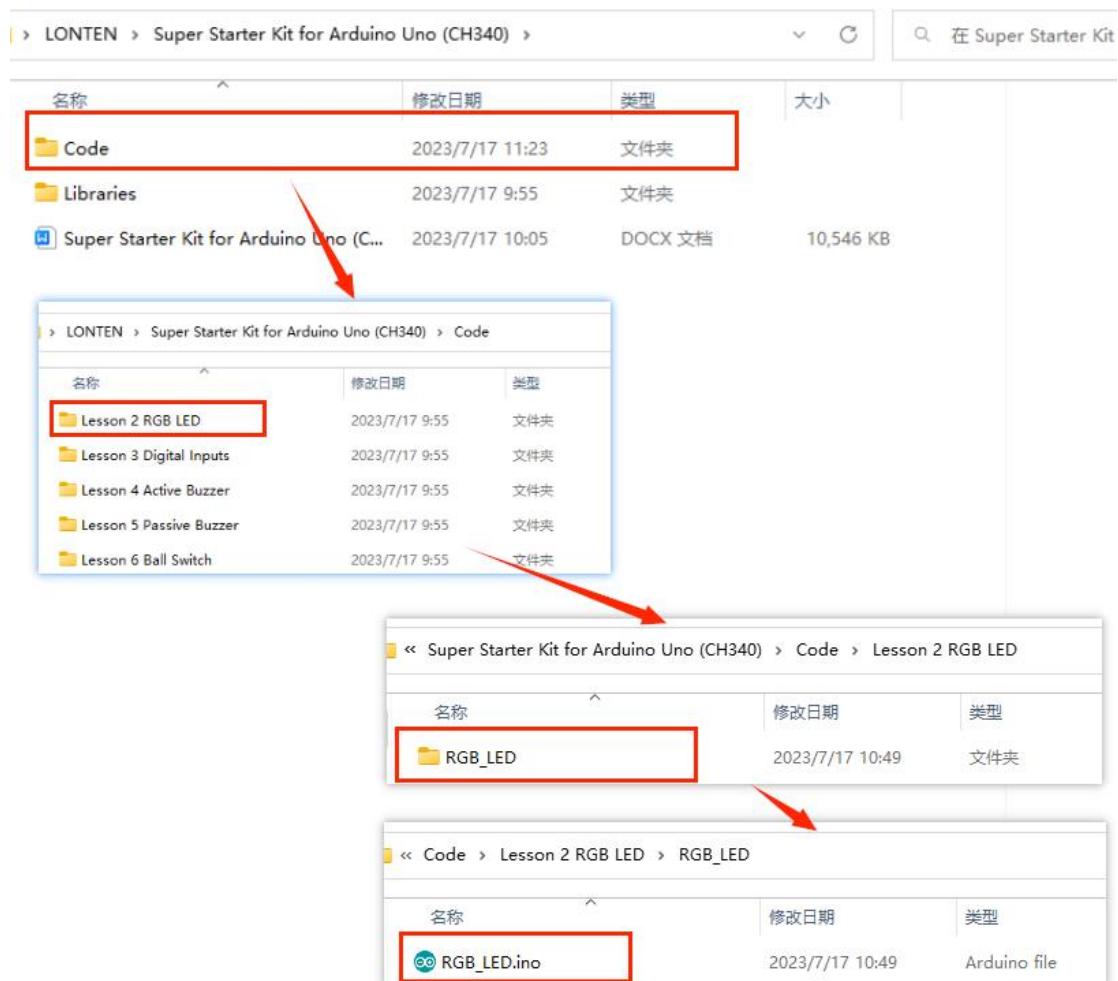
## Code

After wiring, please open the Sketch in folder path: Tutorial > code > Lesson 2 RGB LED > RGB\_LED, and click UPLOAD to upload the program.



The sketch starts by specifying which pins are going to be used for each of the colors:

```
// Define Pins
```

```
#define BLUE 3
```



```
#define GREEN 5
```

```
#define RED 6
```

The next step is to write the 'setup' function. As we have learnt in earlier lessons, the setup function runs just once after the Arduino has reset. In this case, all it has to do is define the three pins we are using as being outputs.

```
void setup()
{
    pinMode(RED, OUTPUT);
    pinMode(GREEN, OUTPUT);
    pinMode(BLUE,OUTPUT);
    digitalWrite(RED, HIGH);
    digitalWrite(GREEN, LOW);
    digitalWrite(BLUE, LOW);
}
```

Before we take a look at the 'loop' function, let's look at the last function in the sketch.

The define variables

```
redValue = 255; // choose a value between 1 and 255 to change the color.
greenValue = 0;
```



---

```
blueValue = 0;
```

This function takes three arguments, one for the brightness of the red, green and blue LEDs. In each case the number will be in the range 0 to 255, where 0 means off and 255 means maximum brightness. The function then calls 'analogWrite' to set the brightness of each LED.

Try adding a few colors of your own to the sketch and watch the effect on your LED.

### **Lesson 3 Digital Inputs**

#### **Overview**

In this lesson, you will learn to use push buttons with digital inputs to turn an LED on and off.

Pressing the button will turn the LED on; pressing the other button will turn the LED off.

#### **Component Required:**

- (1) x LONTEN Uno R3
- (1) x 830 Tie-points Breadboard
- (1) x 5mm red LED
- (1) x 220 ohm resistor
- (2) x push switches

# LROBRYA

---



(7) x M-M wires (Male to Male jumperwires)

## Component Introduction
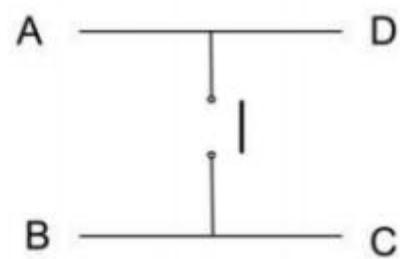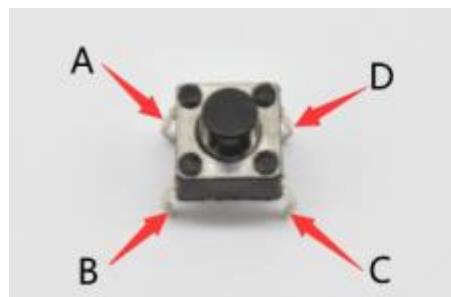
### PUSH SWITCHES:

Switches are really simple components. When you press a button or flip a lever, they connect two contacts together so that electricity can flow through them.

The little tactile switches that are used in this lesson have four connections, which can be a little confusing.




Actually, there are only really two electrical connections. Inside the switch package, pins B and C are connected together, as are A and D.


## Connection

### Schematic

# LROBRUYA

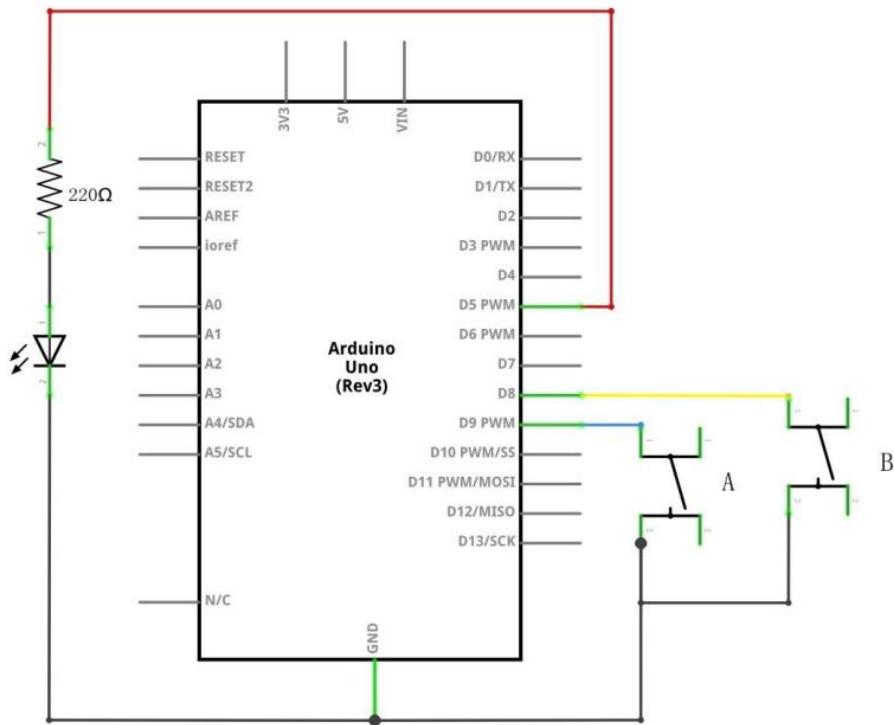

## Circuit Connection

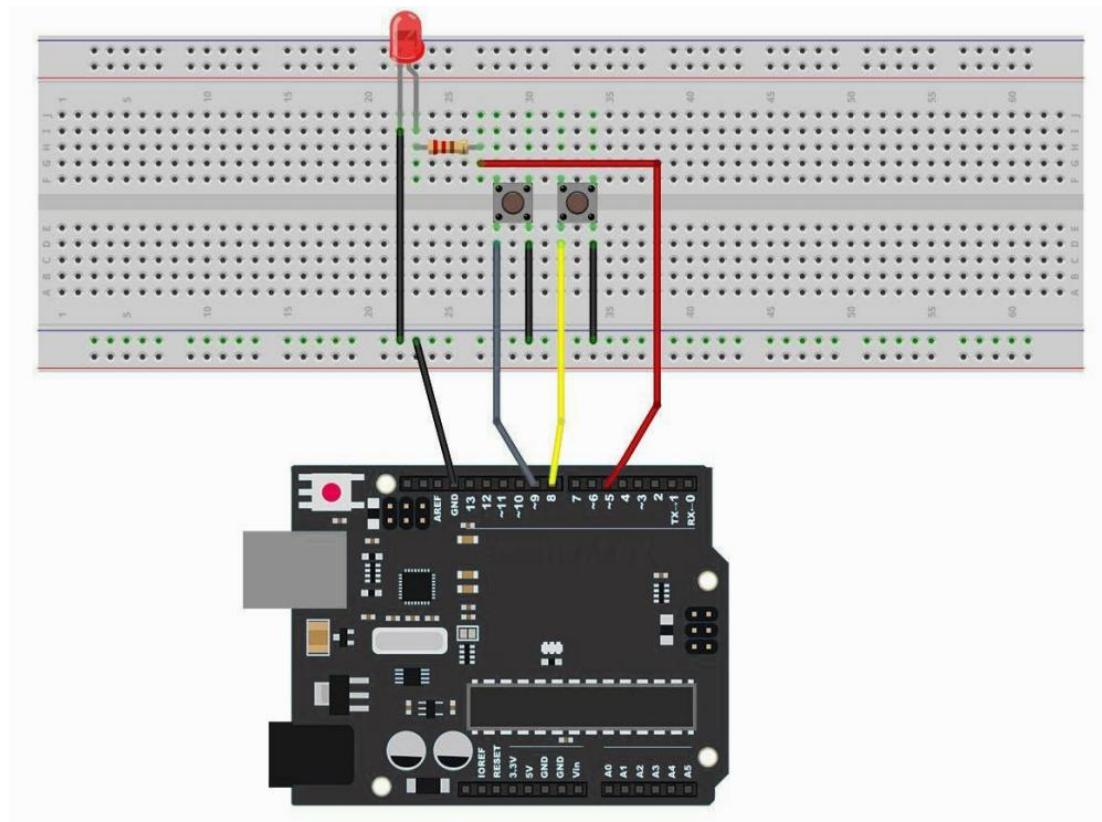


# LROBRYA

Although the bodies of the switches are square, the pins protrude from opposite sides of the switch. This means that the pins will only be far enough apart when they are placed correctly on the breadboard.

Remember that the LED has to have the shorter negative lead to the left.

## Example picture

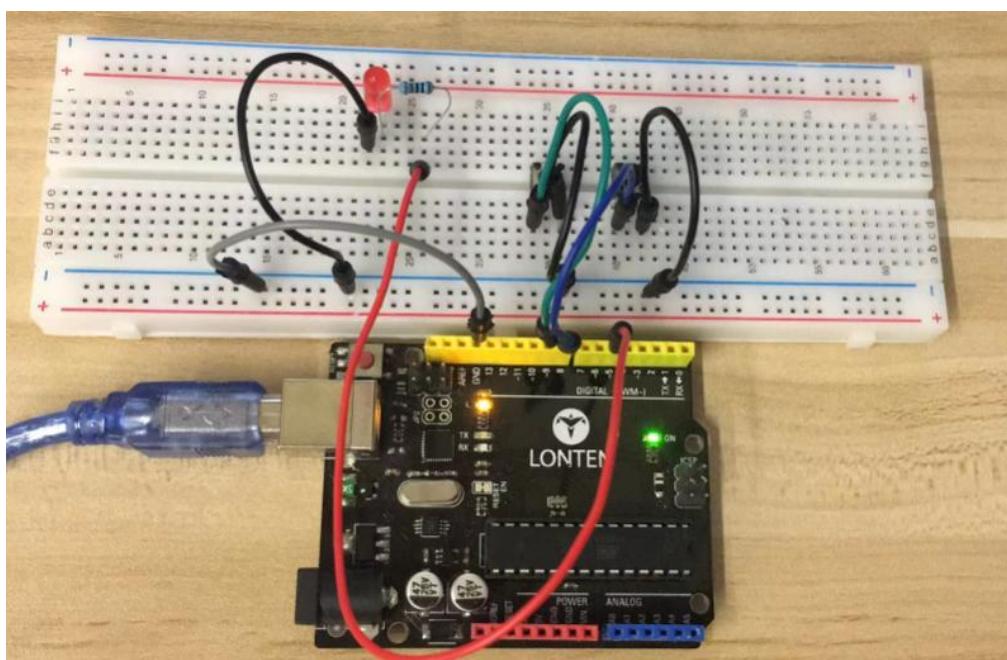

## Code

After wiring, please open program in the code folder- Lesson 3 Digital Inputs, and press UPLOAD to upload the program.

Load the sketch onto your UNO board. Pressing the left button will turn the LED on while pressing the right button will turn it off.

The first part of the sketch defines three variables for the three pins that are to be used. The 'ledPin' is the output pin and 'buttonApin' will refer to



---

the switch nearer the top of the breadboard and 'buttonBpin' to the other switch.

The 'setup' function defines the ledPin as being an OUTPUT as normal, but now we have the two inputs to deal with. In this case, we use the set the pinMode to be 'INPUT\_PULLUP' like this:

```
pinMode(buttonApin, INPUT_PULLUP);  
pinMode(buttonBpin, INPUT_PULLUP);
```

The pin mode of INPUT\_PULLUP means that the pin is to be used as an input, but that if nothing else is connected to the input, it should be 'pulled up' to HIGH. In other words, the default value for the input is HIGH, unless it is pulled LOW by the action of pressing the button.

This is why the switches are connected to GND. When a switch is pressed, it connects the input pin to GND, so that it is no longer HIGH.

Since the input is normally HIGH and only goes LOW when the button is pressed, the logic is a little upside down. We will handle this in the 'loop' function.

```
void loop()  
{  
if (digitalRead(buttonApin) == LOW)  
{
```



```
digitalWrite(ledPin,HIGH);  
}  
  
if (digitalRead(buttonBpin) == LOW)  
{  
    digitalWrite(ledPin, LOW);  
}  
}
```

In the 'loop' function there are two 'if' statements. One for each button.

Each does an 'digitalRead' on the appropriate input.

Remember that if the button is pressed, the corresponding input will be LOW, if button A is low, then a 'digitalWrite' on the ledPin turns it on.

Similarly, if button B is pressed, a LOW is written to the ledPin.

## Lesson 4 Active Buzzer

### Overview

In this lesson, you will learn how to generate a sound with an active buzzer.

#### **Component Required:**

(1) x LONTEN Uno R3

(1) x Active buzzer

# LROBRYA

---

(2) x F-M wires (Female to Male DuPont wires)

## Component Introduction

### BUZZER:



Active buzzer is widely used on computer, printer, alarm, electronic toy, telephone, timer etc.. It has an inner vibration source. Simply connect it with 5V power supply, it can buzz continuously.


Turn the pins of two buzzers face up. The one with a green circuit board is a passive buzzer, while the other enclosed with a black tape is an active one.

The difference between the two is that an active buzzer has a built-in oscillating source, so it will generate a sound when electrified. A passive buzzer does not have such a source so it will not tweet if DC signals are used; instead, you need to use square waves whose frequency is between 2K and 5K to drive it. The active buzzer is often more expensive than the passive one because of multiple built-in oscillating circuits.


## Connection

## Schematic

# LROBRUYA

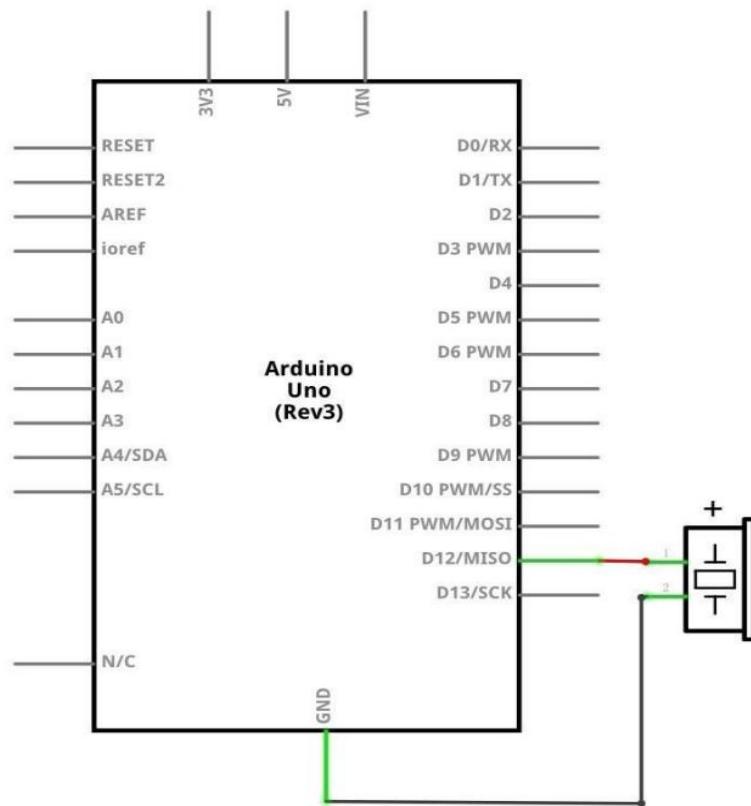


## Circuit Connection

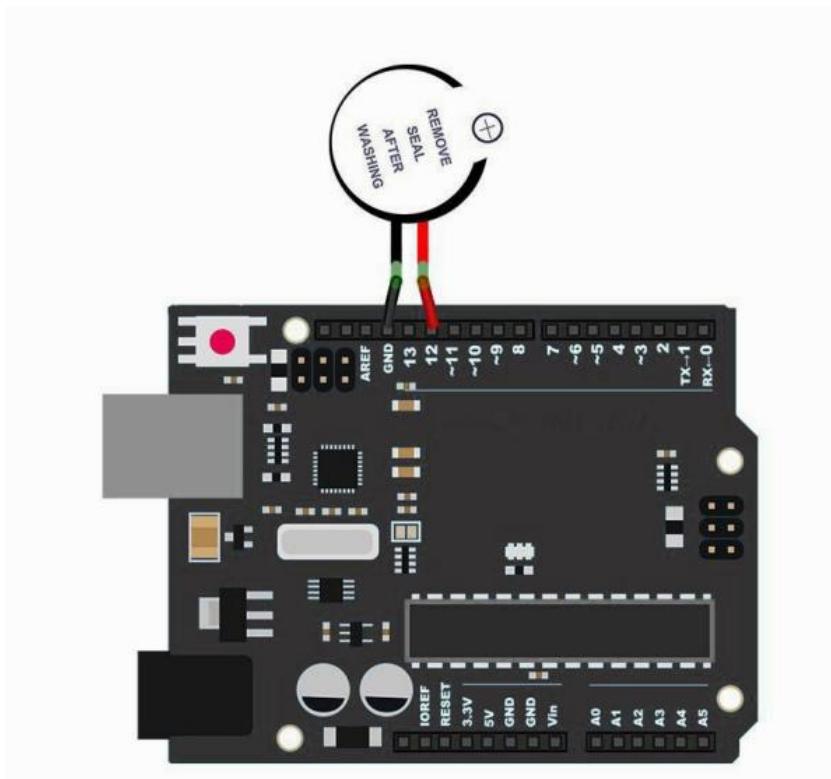

# LROBROUYA

---

## Example picture

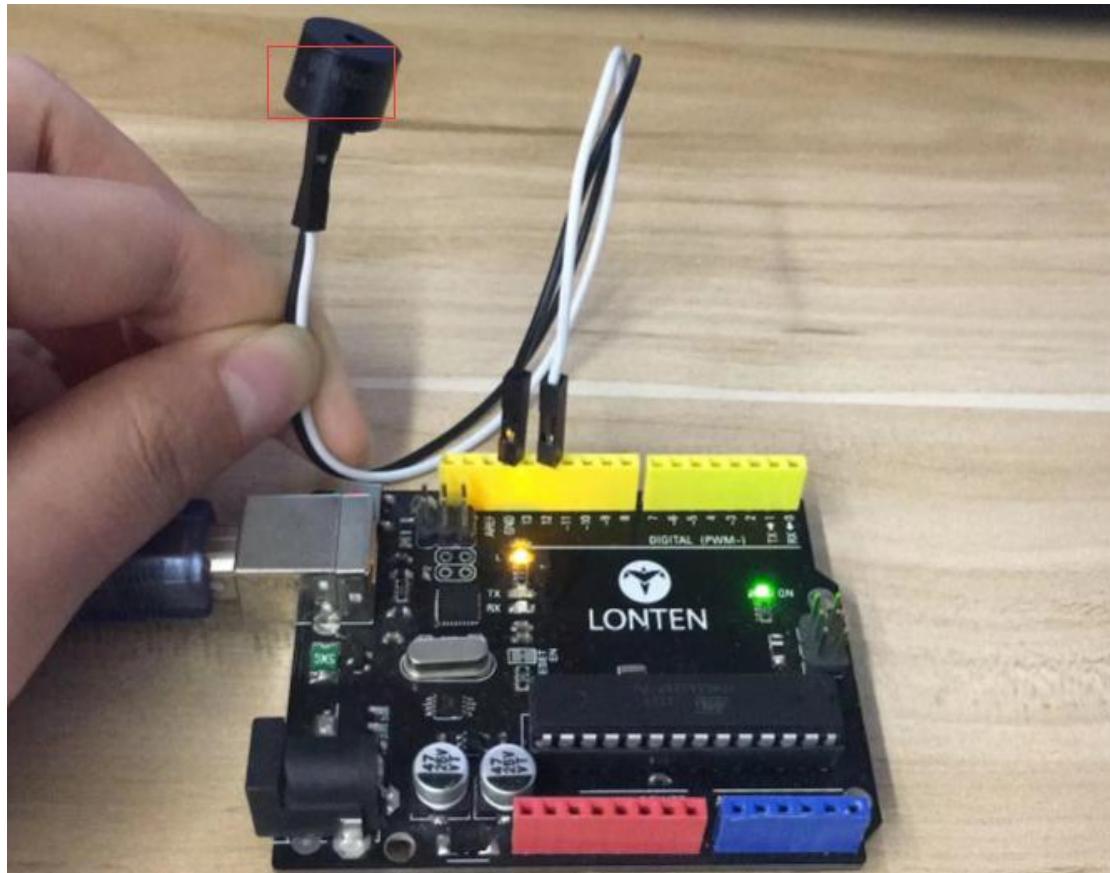

## Code

After wiring, please open the program in the code folder- Lesson 4

Making Sounds and click UPLOAD to upload the program.

## Lesson 5 Passive Buzzer

## Overview

In this lesson, you will learn how to use a passive buzzer.

The purpose of the experiment is to generate eight different sounds, each sound lasting 0.5 seconds: from Alto Do (523Hz), Re (587Hz), Mi

# LROBREUYA

---

(659Hz), Fa (698Hz), So (784Hz), La (880Hz), Si (988Hz) to Treble Do (1047Hz).

## **Component Required**

(1) x LONTEN Uno R3

(1) x Passive buzzer

(2) x F-M wires (Female to Male DuPont wires)

## **Component Introduction**

### **Passive Buzzer:**




The working principle of passive buzzer is using PWM generating audio to make the air to vibrate. Appropriately changed as long as the vibration frequency, it can generate different sounds. For example, sending a pulse of 523Hz, it can generate Alto Do, pulse of 587Hz, it can generate midrange Re, pulse of 659Hz, it can produce midrange Mi. By the buzzer, you can play a song.

# LROBRUYA

We should be careful not to use the UNO R3 board analog Write () function to generate a pulse to the buzzer, because the pulse output of analog Write () is fixed (500Hz).

## Connection


### Schematic

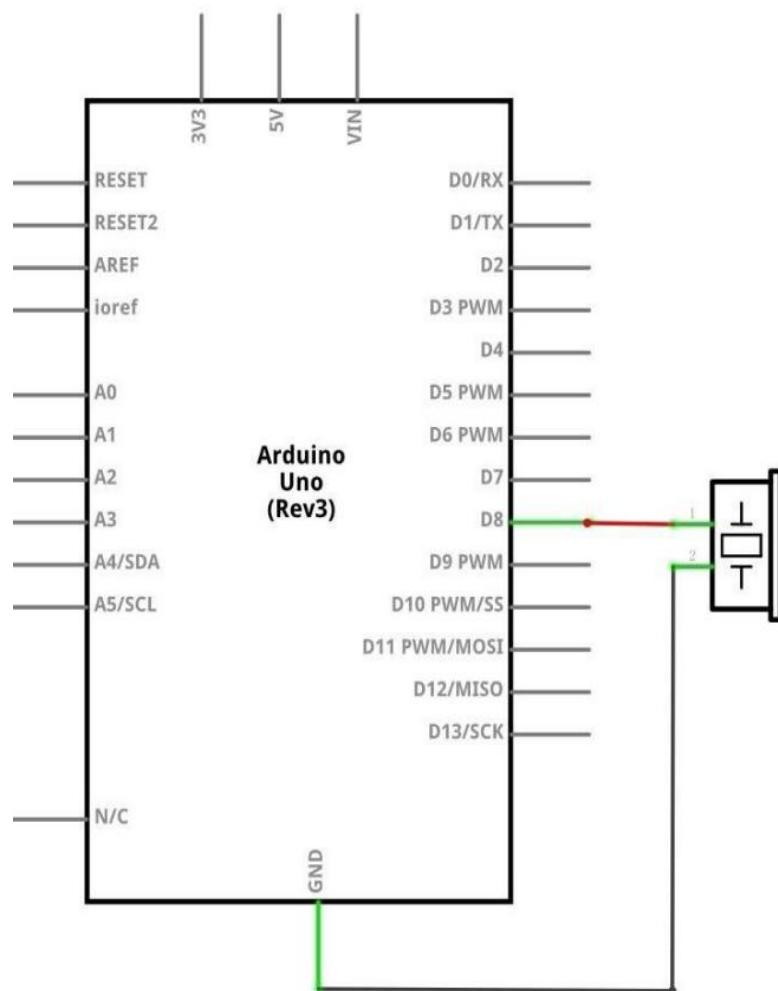

# LROBRYA


---

## Circuit Connection

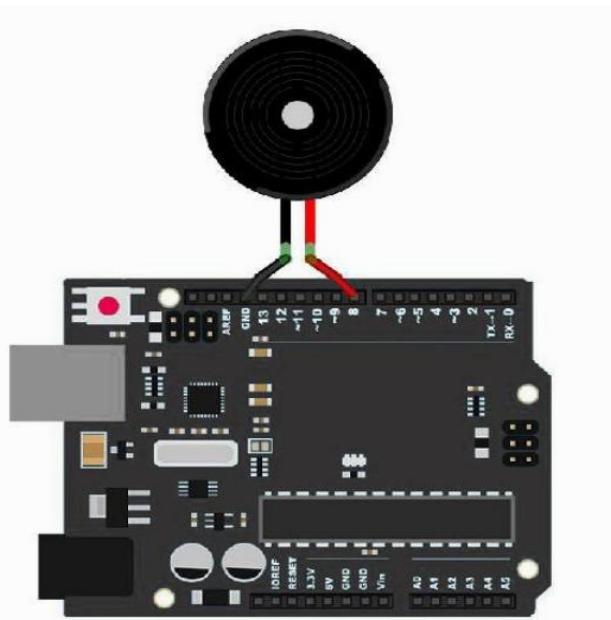

Wiring the buzzer connected to the UNO R3 board, the red (positive) to the pin8, black wire (negative) to the GND.

### Example picture

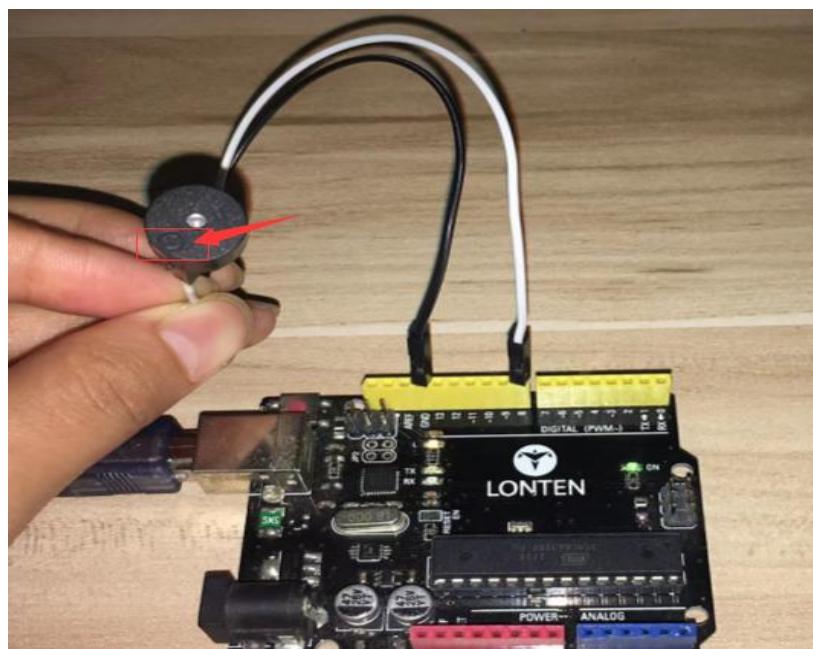



## Code

After wiring, please open the program in the code folder- Lesson 5

Passive Buzzer and click UPLOAD to upload the program.

Before you can run this, make sure that you have installed the <pitches> library or re-install it, if necessary. Otherwise, your code won't work.

## Lesson 6 Tilt Ball Switch

### Overview

In this lesson, you will learn how to use a tilt ball switch in order to detect small angle of inclination.

### Component Required

(1) x LONTEN Uno R3

(1) x Tilt Ball switch

(2) x F-M wires (Female to Male DuPont wires)

### Component Introduction

#### Tilt sensor:





Tilt sensors (tilt ball switch) allow you to detect orientation or inclination. They are small, inexpensive, low-power and easy-to-use. If used properly, they will not wear out. Their simplicity makes them popular for toys, gadgets and appliances. Sometimes, they are referred to as "mercury switches", "tilt switches" or "rolling ball sensors" for obvious reasons. They are usually made up of a cavity of some sort (cylindrical is popular, although not always) with a conductive free mass inside, such as a blob of mercury or rolling ball.

One end of the cavity has two conductive elements (poles). When the sensor is oriented so that that end is downwards, the mass rolls onto the poles and shorts them, acting as a switch throw.


While not as precise or flexible as a full accelerometer, tilt switches can detect motion or orientation. Another benefit is that the big ones can switch power on their own.

Accelerometers, on the other hand, output digital or analog voltage that must then be analyzed using extra circuitry.


## **Connection**

## **Schematic**

# LROBRUYA

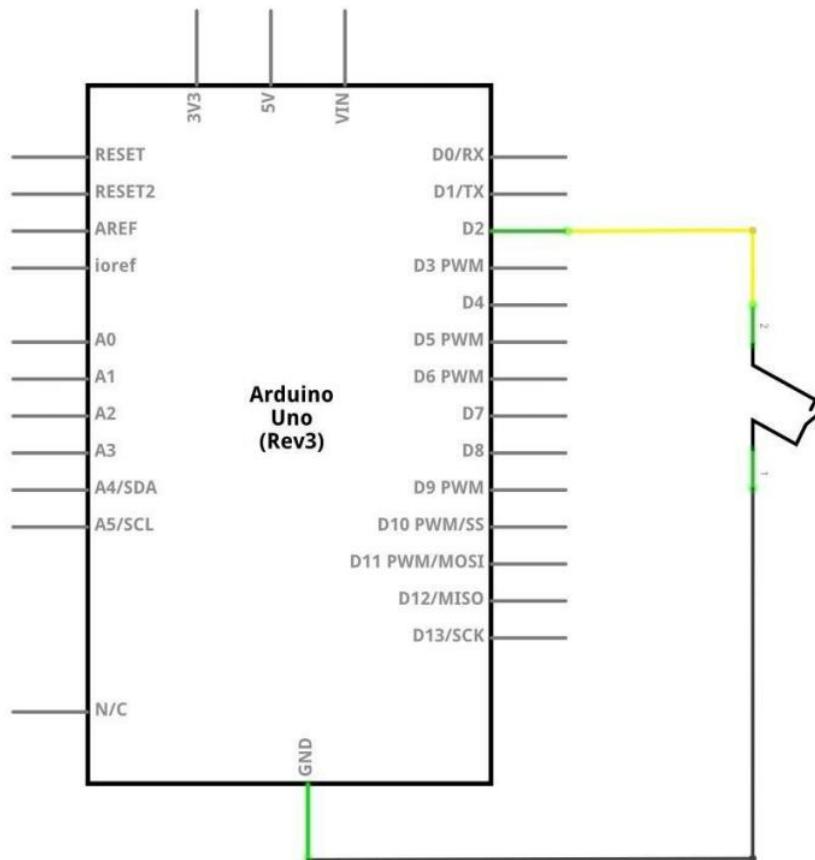


## Circuit Connection

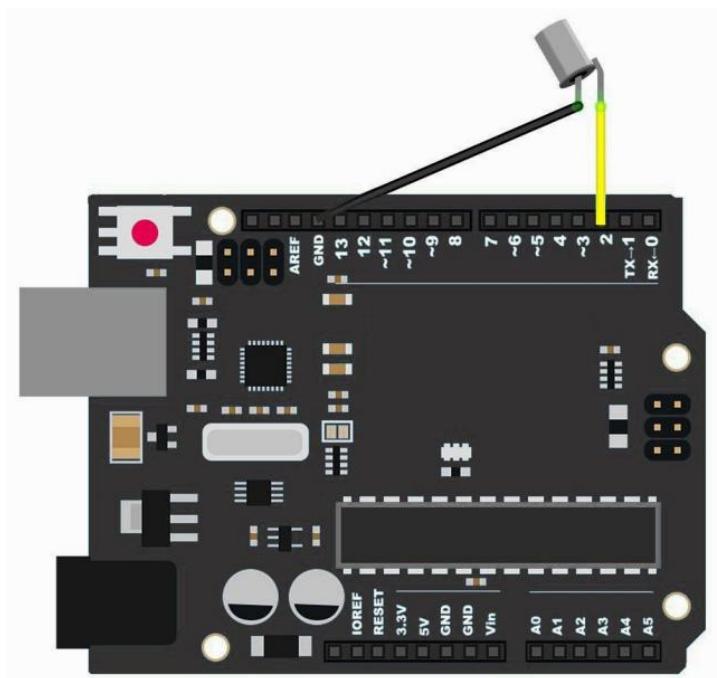

# LROBRYA

---

## Example picture

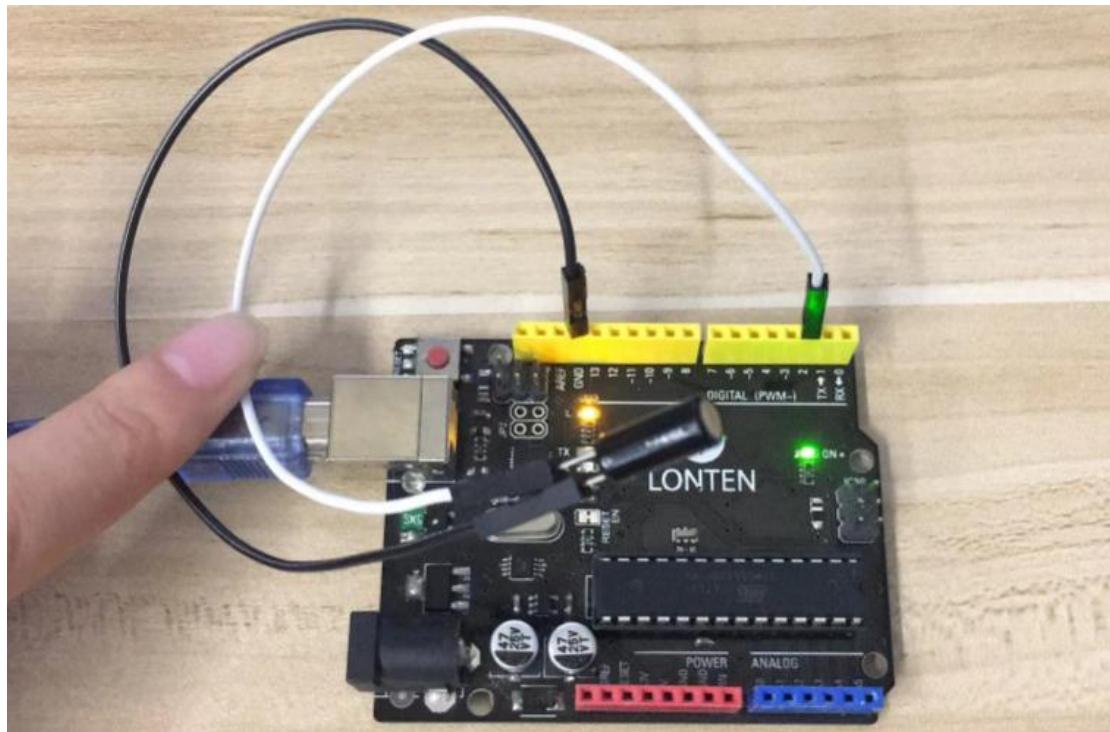

## Code

After wiring, please open the program in the code folder- Lesson 6 Ball  
Switch and click UPLOAD to upload the program.

## Lesson 7 Analog Value Reading

## Overview

In this experiment, we will begin the learning of analog I/O interfaces. On an Arduino, there are 6 analog interfaces numbered from A0 to A5. These 6 interfaces can also be used as digital ones numbered as D14-D19. After

a brief introduction, let's begin our project. Potentiometer used here is a typical output component of analog value that is familiar to us.



## Component Required

- (1) x LONTEN Uno R3
- (1) x Potentiometer
- (5) x F-M wires (Female to Male DuPont wires)


## Circuit Connection

In this experiment, we will convert the resistance value of the potentiometer to analog ones and display it on the screen. This is an application we need to master well for our future experiments.

Connection circuit as below:

# LROBRUYA

---

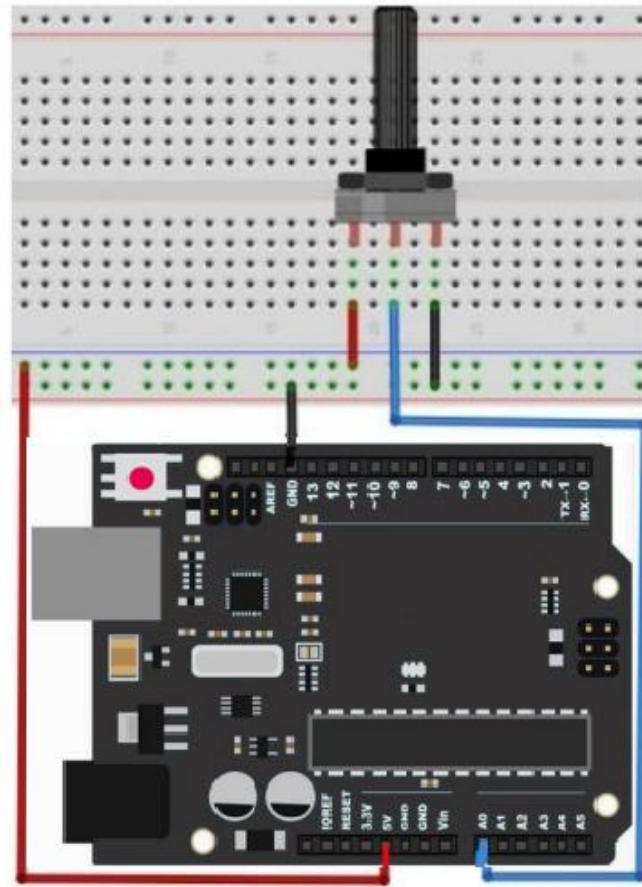


The analog interface we use here is interface A0.

## Example picture

# LROBRUYA


---

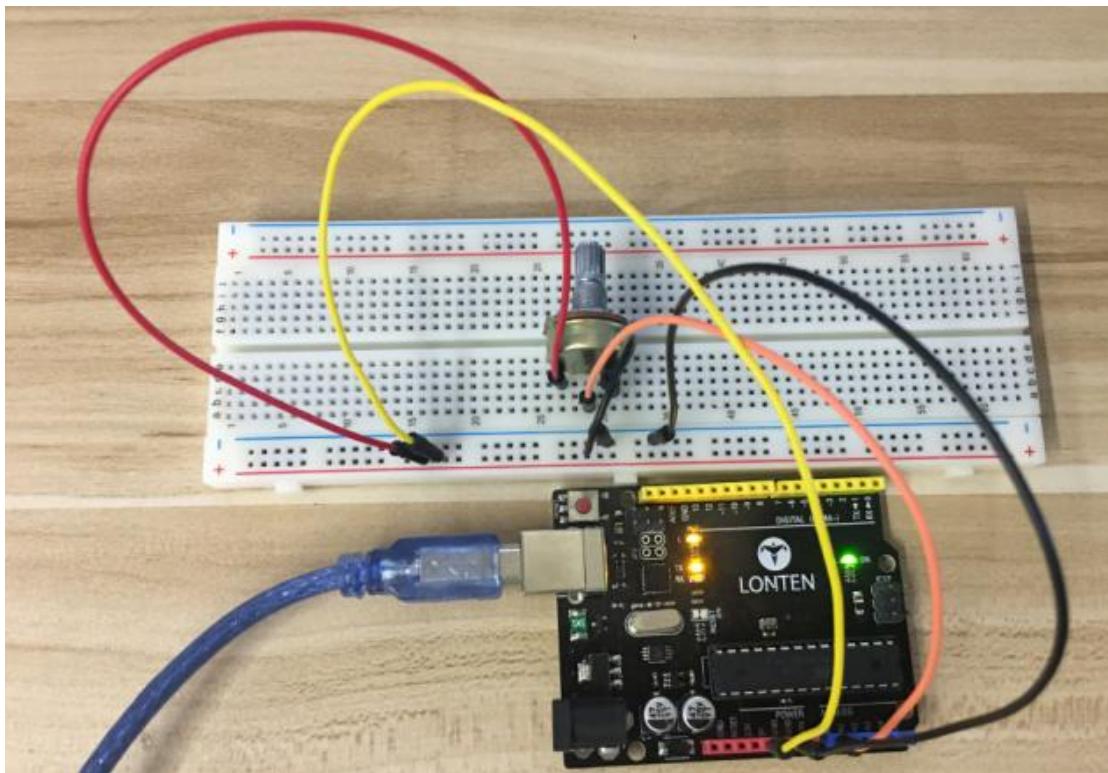

## Code

The Sample Program uses the built-in LED connected to pin 13. Each time the device reads a value, the LED blinks. Below is the analog value it reads.

# LROBRYA

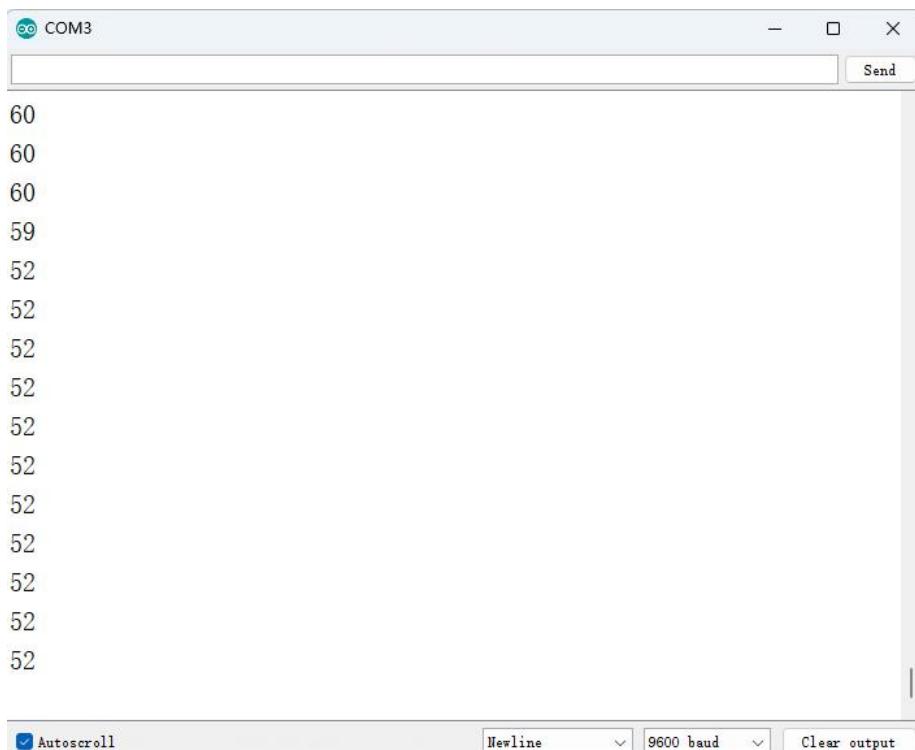

When you rotate the potentiometer knob, you can see the displayed value changes. The reading of analog value is a very common function since most sensors output analog value. After calculation, we can have the corresponding value we need.

## Lesson 8 Servo

### Overview

Servo is a type of geared motor that can only rotate 180 degrees. It is controlled by sending electrical pulses from your UNO R3 board. These pulses tell the servo what position it should move to. The Servo has three wires, of which the brown one is the ground wire and should be

connected to the GND port of UNO, the red one is the power wire and should be connected to the 5v port, and the orange one is the signal wire and should be connected to the Dig #9 port.

## Component Required

(1) x LONTEN Uno R3

(1) x Servo (SG90)

(3) x M-M wires (Male to Male jumper wires)

## Component Introduction

### SG90




- Universal for JR and FP connector
- Cable length : 25cm
- No load; Operating speed: 0.12 sec / 60 degree (4.8V), 0.10 sec / 60 degree (6.0V)
- Stall torque (4.8V): 1.6kg/cm
- Temperature : -30~60'C

# LROBRYA

- Dead band width: 5us Working voltage: 3.5~6V
- Dimension : 1.26 in x 1.18 in x 0.47 in (3.2 cm x 3 cm x 1.2 cm)
- Weight : 4.73 oz (134 g)


## Connection

### Schematic

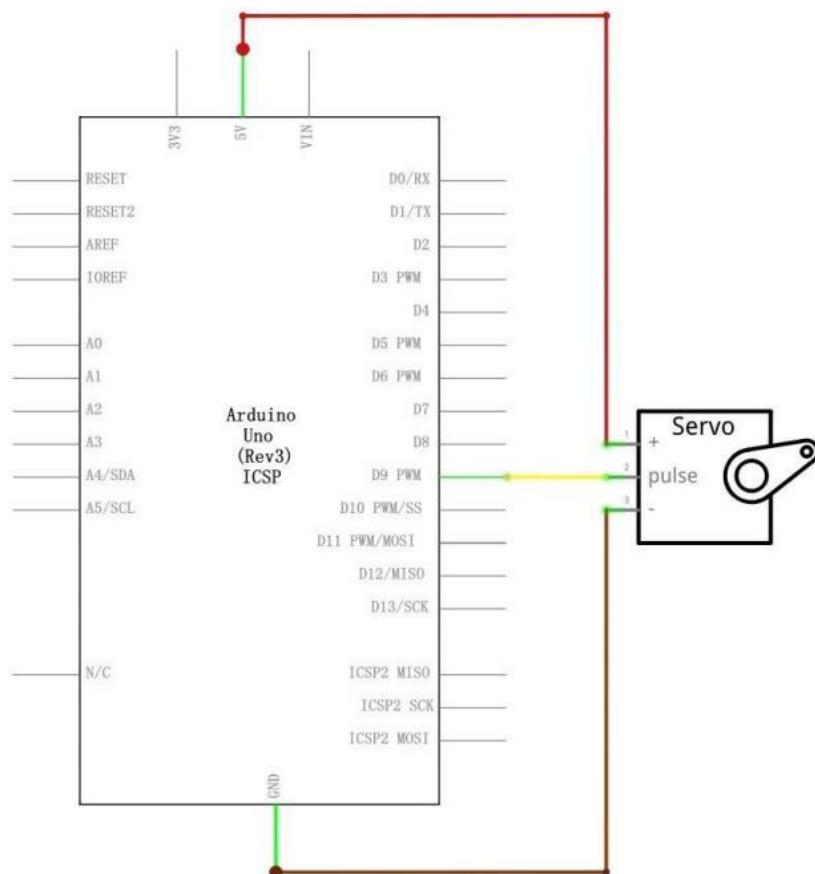


# LROBRUYA

## Circuit Connection

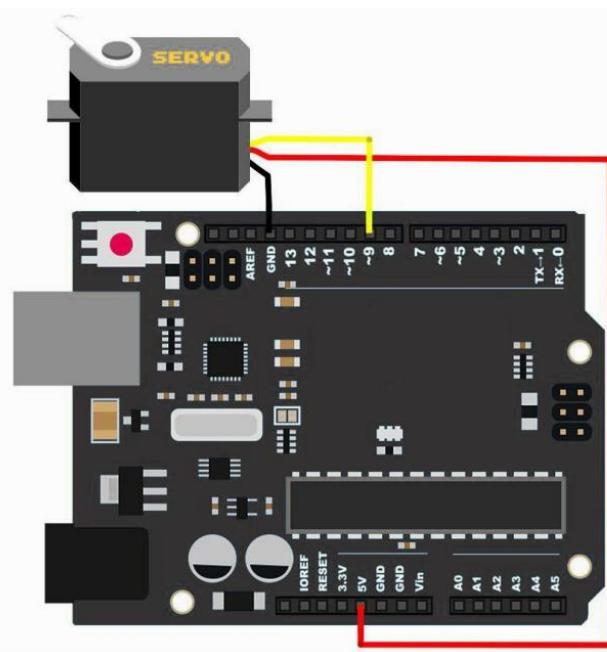
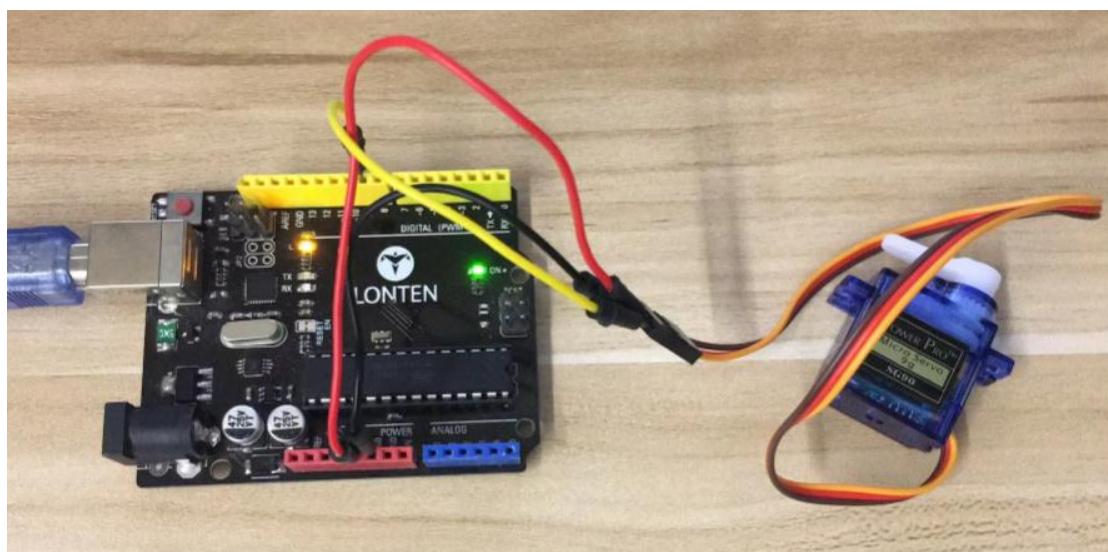
## Example picture

In the picture, the brown wire of servo is adapted via the black M-M wires, the red one is adapted via the red M-M wires, and the orange one is adapted via the yellow M-M wires.





## Code

After wiring, please open the program in the code folder- Lesson 8 Servo and click UPLOAD to upload the program.

Before you can run this, make sure that you have installed the < Servo> library or re-install it, if necessary. Otherwise, your code won't work.

## Lesson 9 Analog Joystick Module

### Overview

Analog joysticks are a great way to add some control in your projects. In this tutorial we will learn how to use the analog joystick module.

### Component


(1) x LONTEN Uno R3

(1) x Joystick module

(5) x F-M wires (Female to Male DuPont wires)

### Component Introduction

#### Joystick

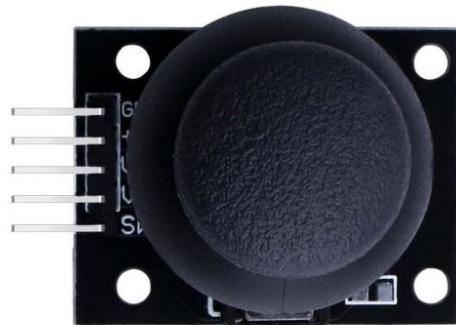




---

The module has 5 pins: VCC, Ground, X, Y, Key. Note that the labels on yours may be slightly different, depending on where you got the module from. The thumb stick is analog and should provide more accurate readings than simple ‘directional’ joysticks tact use some forms of buttons, or mechanical switches. Additionally, you can press the joystick down (rather hard on mine) to activate a ‘press to select’ push-button. We have to use analog Arduino pins to read the data from the X/Y pins, and a digital pin to read the button. The Key pin is connected to ground, when the joystick is pressed down, and is floating otherwise. To get stable readings from the Key /Select pin, it needs to be connected to VCC via a pull-up resistor. The built in resistors on the Arduino digital pins can be used. For a tutorial on how to activate the pull-up resistors for Arduino pins, configured as inputs.


# LROBRUYA

## Connection

### Schematic

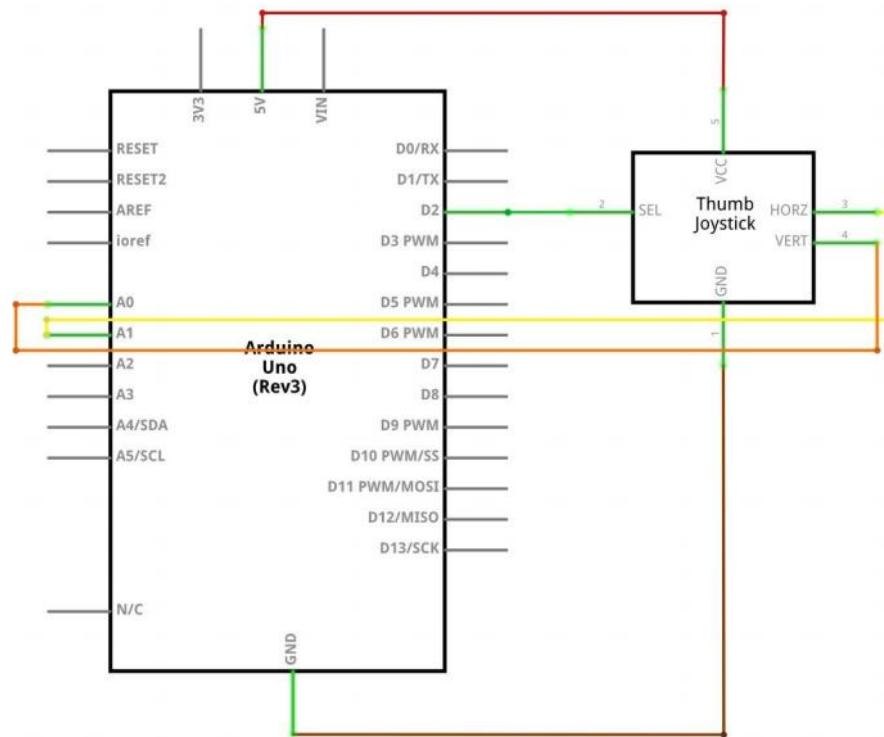

### Circuit Connection

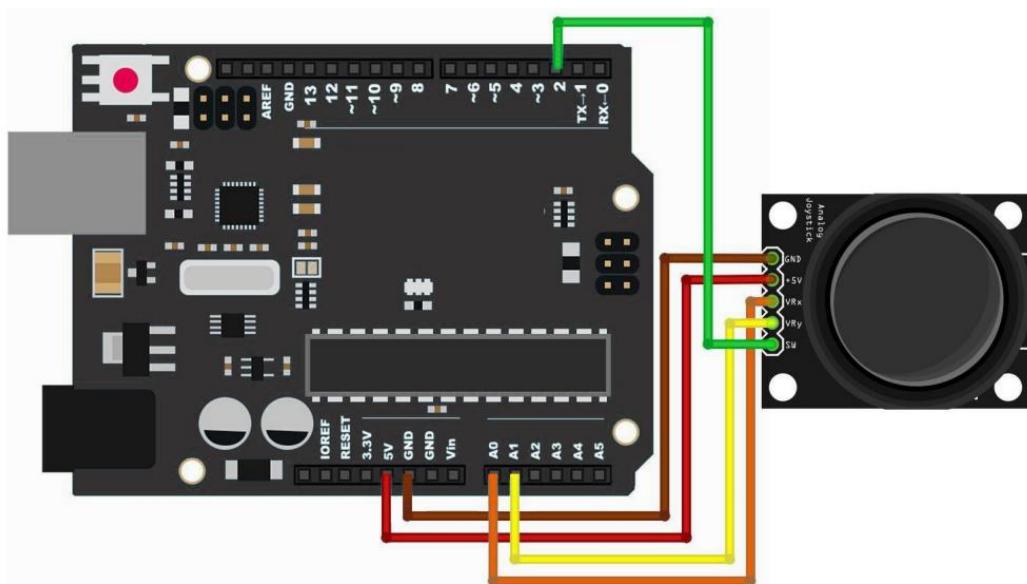

# LROBRYA


---

We need 5 connections to the joystick.

The connections are: Key, Y, X, Voltage and Ground.

“Y and X” are Analog and “Key” is Digital. If you don’t need the switch then you can use only 4 pins.

## Example picture

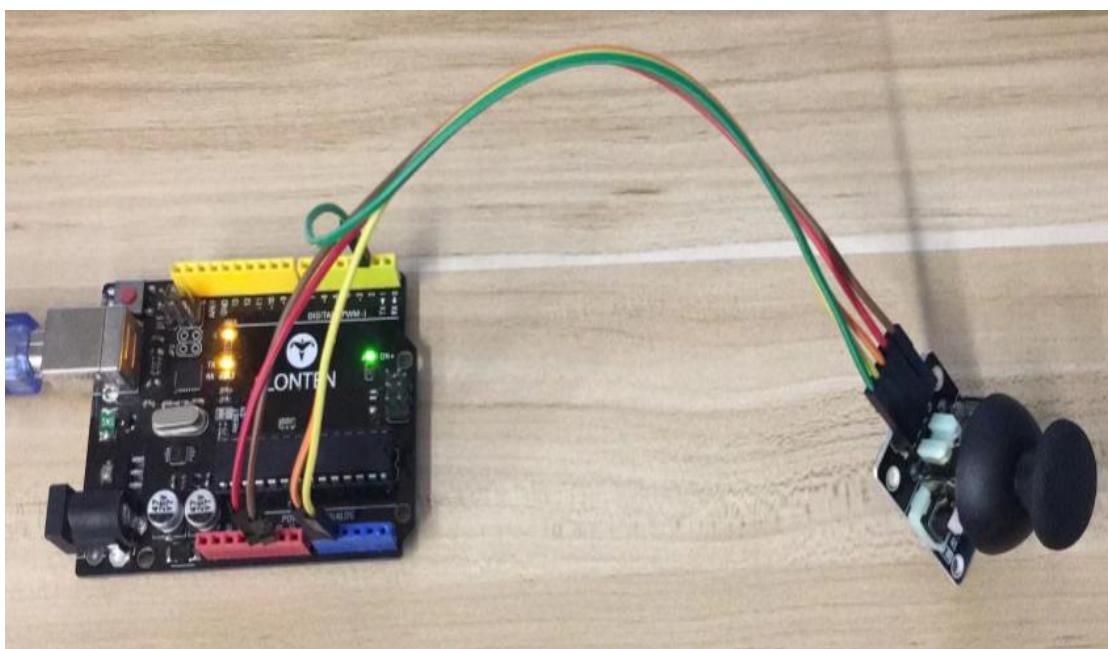

## Code

[After wiring, please open the program in the code folder- Lesson 9](#)

[Analog Joystick Module and click UPLOAD to upload the program.](#)

Analog joysticks are basically potentiometers so they return analog values.

When the joystick is in the resting position or middle, it should return a value of about 512.

# LROBRYA

The range of values goes from 0 to 1024.

```
Switch: 1
X-axis: 0
Y-axis: 1023

Switch: 1
X-axis: 1023
Y-axis: 1023

Switch: 1
X-axis: 0
Y-axis: 0
```

## Lesson 10 Water Level Detection Sensor Module

### Overview

In this lesson, you will learn how to use a water level detection sensor module. This module can perceive the depth of water and the core component is an amplifying circuit which is made up of a transistor and several pectinate PCB routings. When put into the water, these routings will present a resistor that can change along with the change of the water's depth. Then, the signal of water's depth is converted into the


electrical signal, and we can know the change of water's depth through the ADC function of UNO R3.

## Component Required

- (1) x LONTEN Uno R3
- (3) x F-M wires (Female to Male DuPont wires)
- (1) x Water lever detection sensor module

## Component Introduction

### Water sensor:

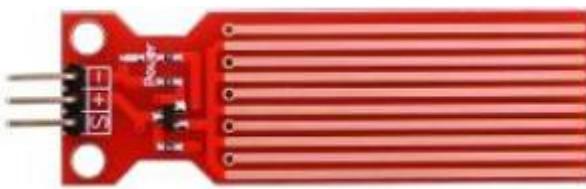

A water sensor brick is designed for water detection, which can be widely used in sensing the rainfall, water level, even the liqueate leakage. The brick is mainly composed of three parts: an electronic brick connector, a  $1\text{ M}\Omega$  resistor, and several lines of bare conducting wires. You can use it with the analog pins to detect the amount of water induced contact between the grounded and sensor traces. This item can judge the water level through with a series of exposed parallel wires stitch to measure the water droplet/water size. It can easily change the water size to analog signal, and output analog value can directly be used in the program

# LROBRYA


function, then to achieve the function of water level alarm. It has low power consumption, and high sensitivity.

## Features:

- 1、Working voltage: 5V
- 2、Working Current: <20ma
- 3、Interface: Analog
- 4、Width of detection: 40mm×16mm
- 5、Working Temperature: 10°C~30°C
- 6、Output voltage signal: 0~4.2V


## Connection

## Schematic

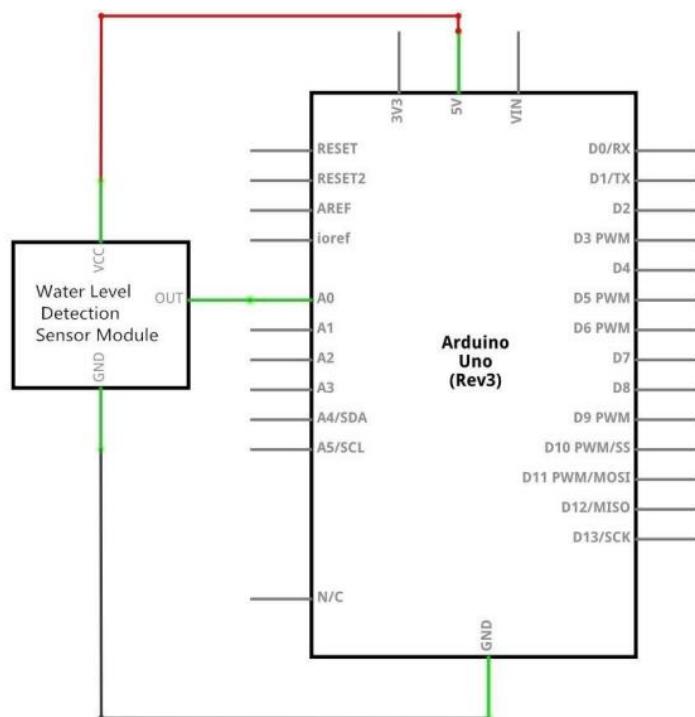


# LROBRUYA

## Circuit Connection

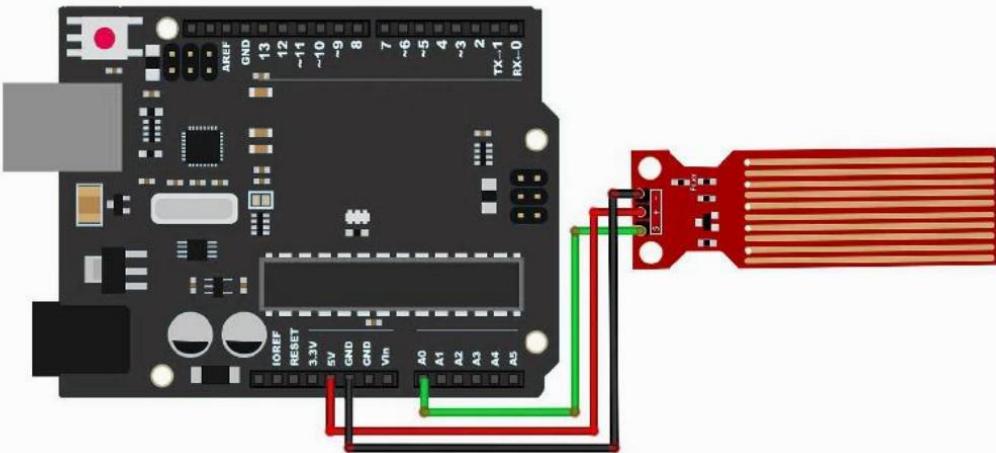

Wiring tips: Power supply (+) is connected to 5V of UNO R3 board, ground electrode (-) is connected to GND. Signal output (S) is connected to the ports (A0-A5) which have function of inputting analog signal in UNO R3 board, random one is OK, but it should define the same demo code as the routine.

## Example picture

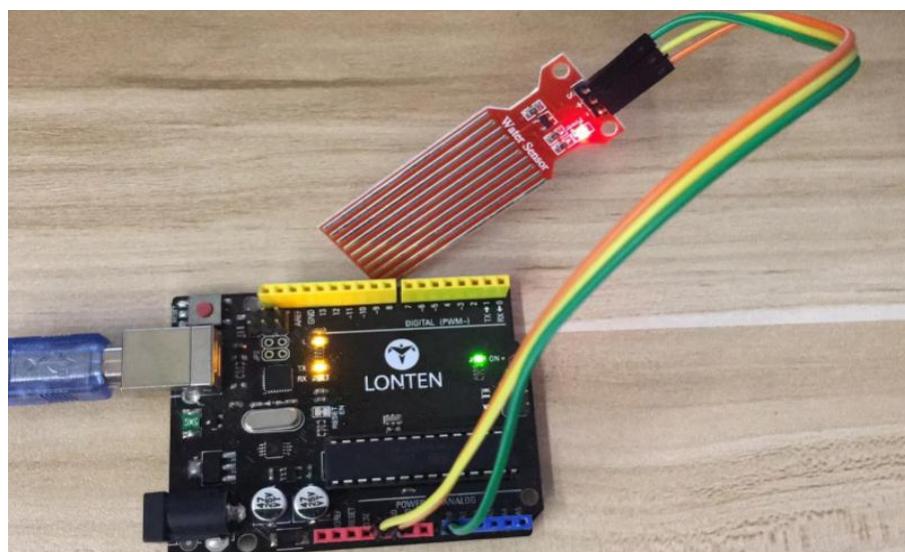

# LROBRYA


---

## Code

After wiring, please open the program in the code folder- Lesson 10

Water Level Detection Sensor Module and click UPLOAD to upload the program.

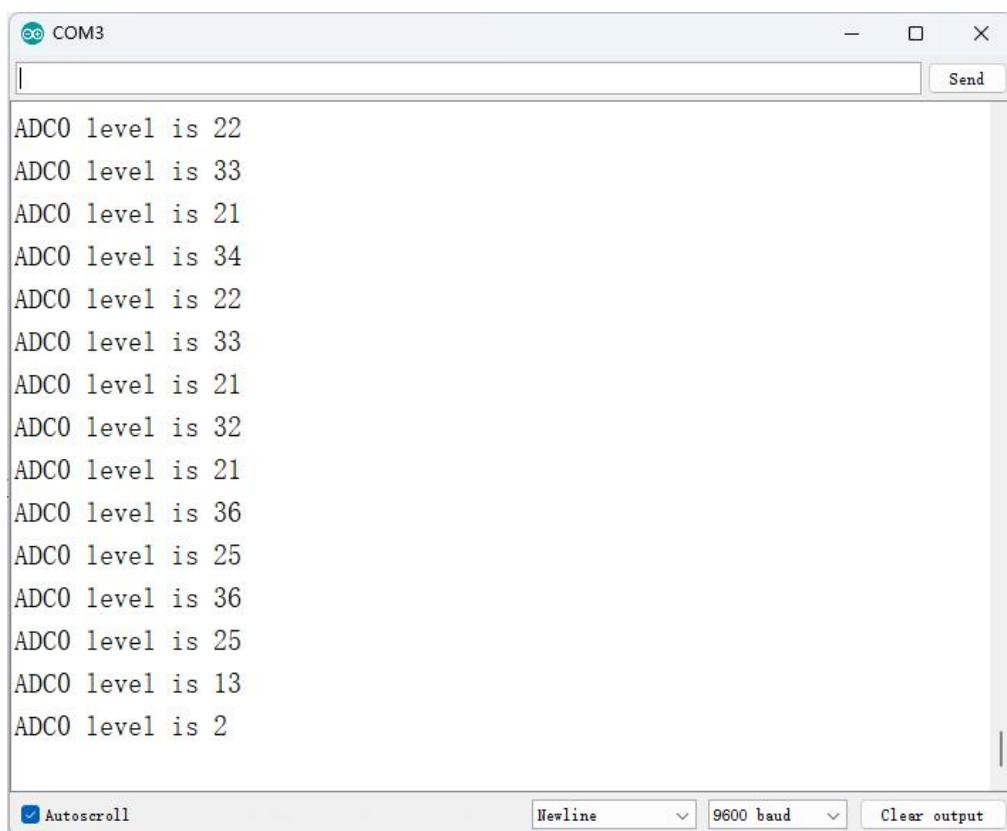Open the monitor then you can see the data as below:



The screenshot shows a terminal window titled "COM3". The window has a "Send" button at the top right and three dropdown menus at the bottom: "Autoscroll" (checked), "Newline", and "9600 baud". The main text area displays a series of lines of text representing ADC0 level measurements. The data is as follows:

```
ADC0 level is 22
ADC0 level is 33
ADC0 level is 21
ADC0 level is 34
ADC0 level is 22
ADC0 level is 33
ADC0 level is 21
ADC0 level is 32
ADC0 level is 21
ADC0 level is 36
ADC0 level is 25
ADC0 level is 36
ADC0 level is 25
ADC0 level is 13
ADC0 level is 2
```

## Lesson 11 Sound Sensor Module

## Overview

In this lesson, you will learn how to use a sound sensor module. This module has two outputs:


# LROBRYA

---

AO: analog output, real-time output voltage signal of microphone

DO: when the intensity of the sound reaches a certain threshold, the output is a high or low level signal. The threshold sensitivity can be achieved by adjusting the potentiometer.

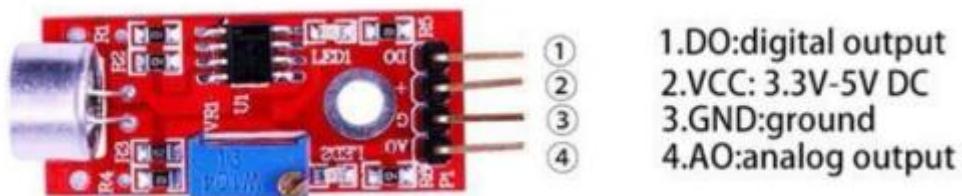To make sure the microphone can detect your voice normally, please try to change its sensitivity by turning the blue precise potentiometer on the module.



## Component Required

(1) x LONTEN Uno R3

(1) x Sound sensor module

(4) x F-M wires (Female to Male DuPont wires)

## Component Introduction

### Ultrasonic sensor

### Microphone

Transducers are devices which convert energy from one form to other. A microphone is a transducer which converts sound energy to electrical signals. It works opposite to a speaker. Microphones are available in

# LROBRYA

---

different shapes and sizes. Depending on the application, a microphone may use different technologies to convert sound to electrical signals. Here, we are going to discuss about the electret condenser microphone which is widely used in mobile phones, laptops, etc.

As the name suggests, the electret condenser microphone is a parallel plate capacitor and works on the principle of a variable capacitance. It consists of two plates, one fixed (called the back plate) and the other moveable (called the diaphragm) with a small gap between them. An electric potential charges the plate. When sound strikes the diaphragm it starts moving, thereby changing the capacitance between the plates which in turn results in a variable electric current to flow.



These microphones are widely used in electronic circuits to detect minor sounds or air vibrations which in turn are converted to electrical signals for further use. The two legs as shown in the image above are used to make electrical connection with the circuit.

# LROBRYA

---




A solid conducting metal body encapsulates the various parts of the microphone. The top face is covered with a porous material with the help of glue. It acts as a filter for the dust particles. The sound signals/air vibrations passes through the porous material and falls on the diaphragm through the hole shown in the image above.


## Connection

## Schematic

# LROBRUYA

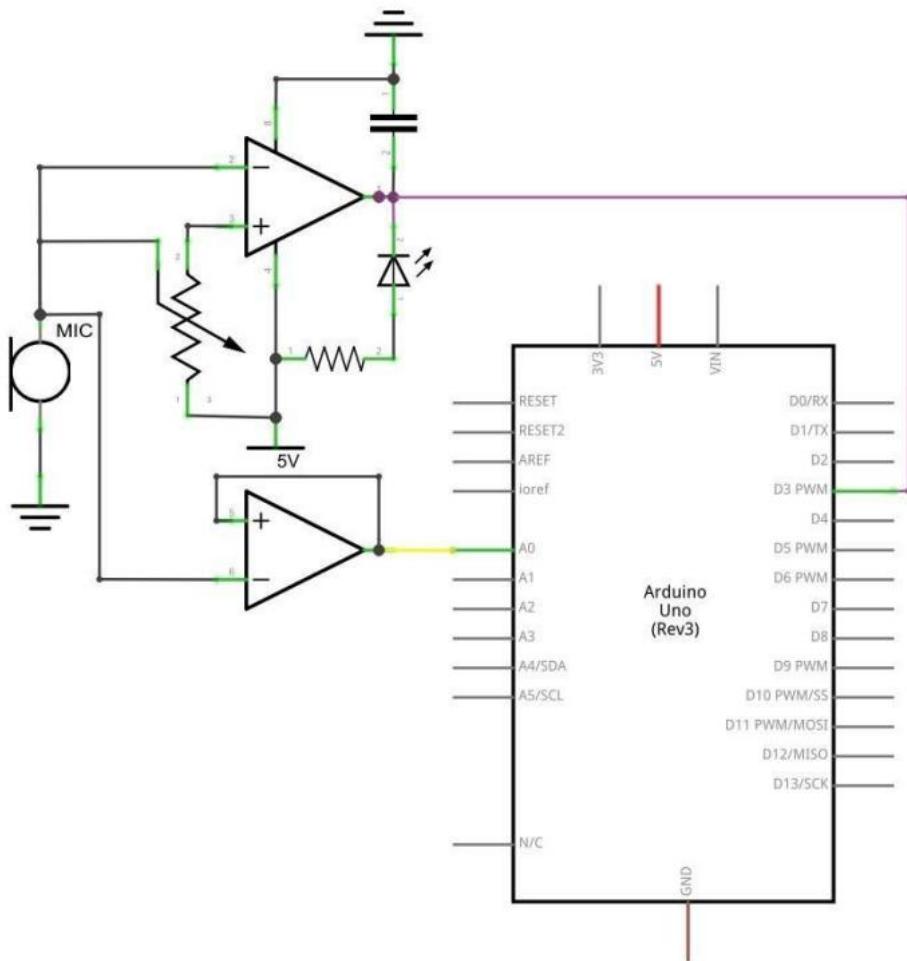


## Circuit Connection

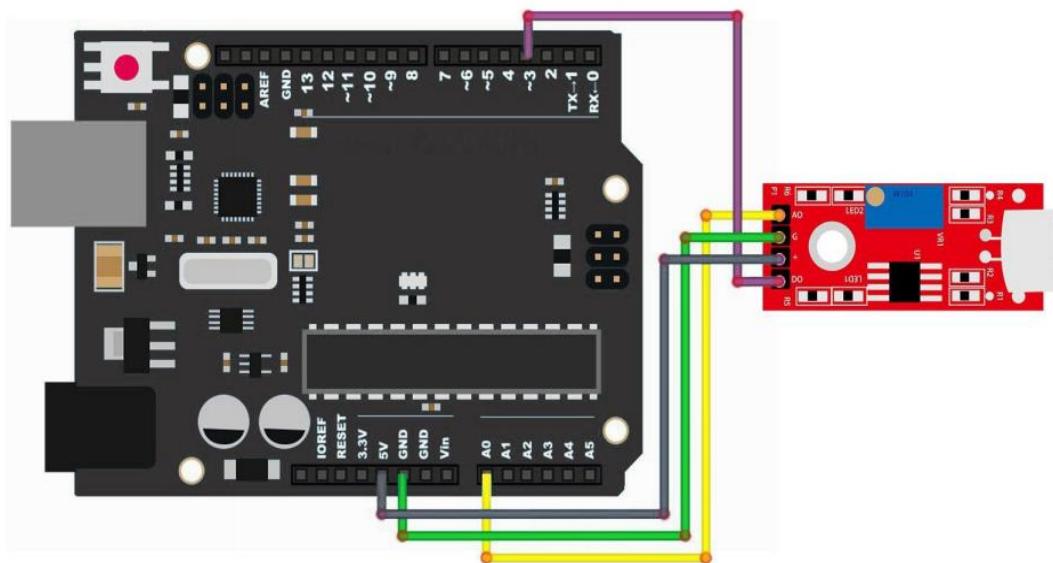

# LROBRYA

---

## Example picture

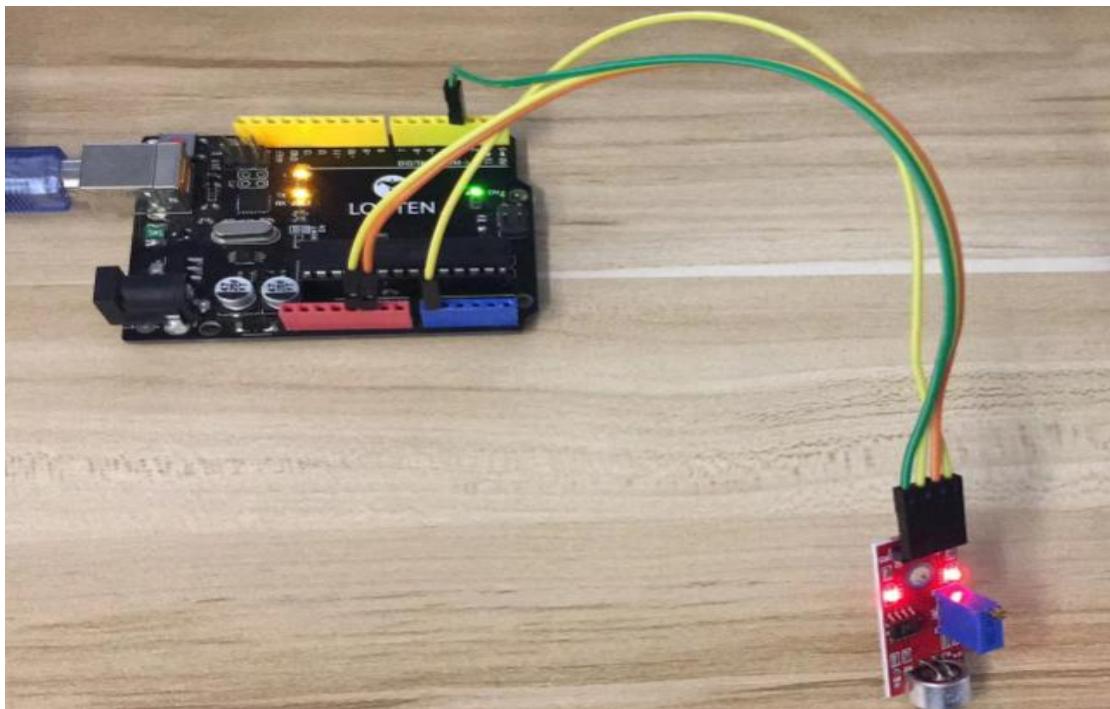

## Code

After wiring, please open the program in the code folder- Lesson 11

[Sound Sensor Module](#) and click UPLOAD to upload the program.

This module provides two signal output modes, for which we wrote two codes:


`digital_signal_output` and `analog_signal_output`. The code of `digital_signal_output` works when the voice reaches a certain value, it will trigger a digital signal and the dig #11 pin on Arduino will output a high level and the indicator L will be lit up at the same time. This

# LROBRYA

---

triggering value may be changed according to the sensitivity adjustment method mentioned above. The code of `analog_signal_output` will read the analog value of the module and directly display it on the serial monitor, likewise, this value can also be changed according to the sensitivity adjustment method mentioned above.

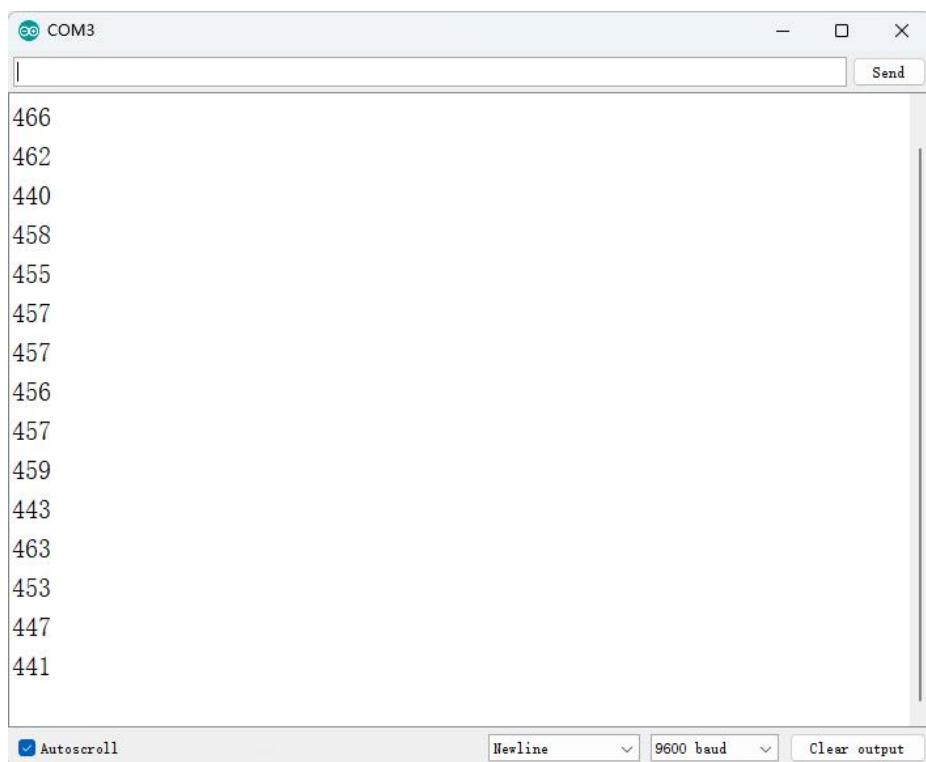Open the monitor then you can see the data as below:



## Lesson 12 DHT11 Temperature and Humidity Sensor

### Overview

This DHT11 Temperature and Humidity Sensor features calibrated digital signal output with the temperature and humidity sensor complex. Its



---

technology ensures high reliability and excellent long-term stability.

A high-performance 8-bit microcontroller is connected. This sensor includes a resistive element and a sense of wet NTC temperature measuring devices. It has excellent quality, fast response, anti-interference ability and high cost performance advantages.

### **Component Required**

- (1) x LONTEN Uno R3
- (1) x DHT11 Temperature and Humidity module
- (3) x F-M wires (Female to Male DuPont wires)

### **Component Introduction**

#### **Temp and humidity sensor:**




Each DHT11 sensor features extremely accurate calibration data of humidity calibration chamber. The calibration coefficients stored in the OTP program memory, internal sensors detect signals in the process, and we should call these calibration coefficients. The single-wire serial interface system is integrated to make it quick and easy. Qualities of

# LROBRUYA


small size, low power, and 20-meter signal transmission distance make it a wide applied application and even the most demanding one. Convenient connection, special packages can be provided according to users need.

## Connection

### Schematic

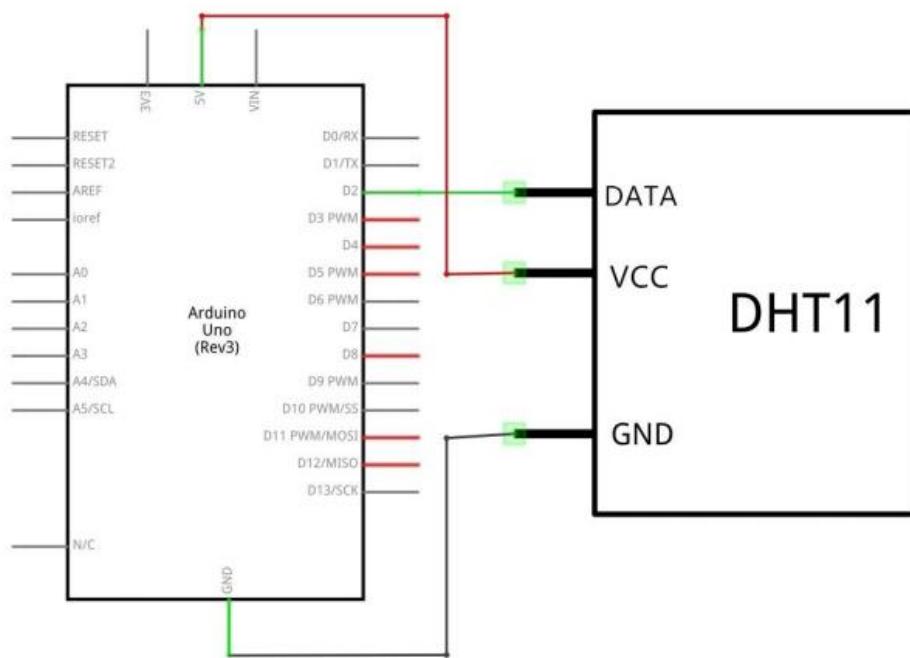

### Circuit Connection

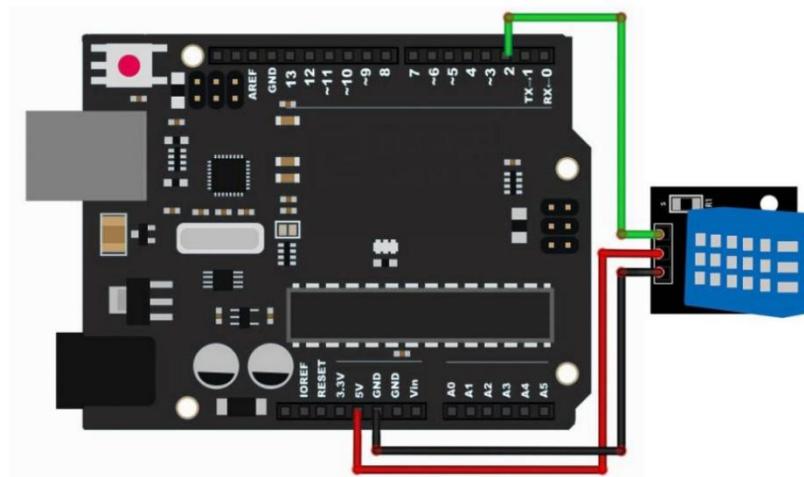


# LROBRYA

---

As you can see we only need 3 connections to the sensor, since one of the pin is not used.

The connections are: Voltage, Ground and Signal which can be connected to any Pin on our UNO.

## Example picture

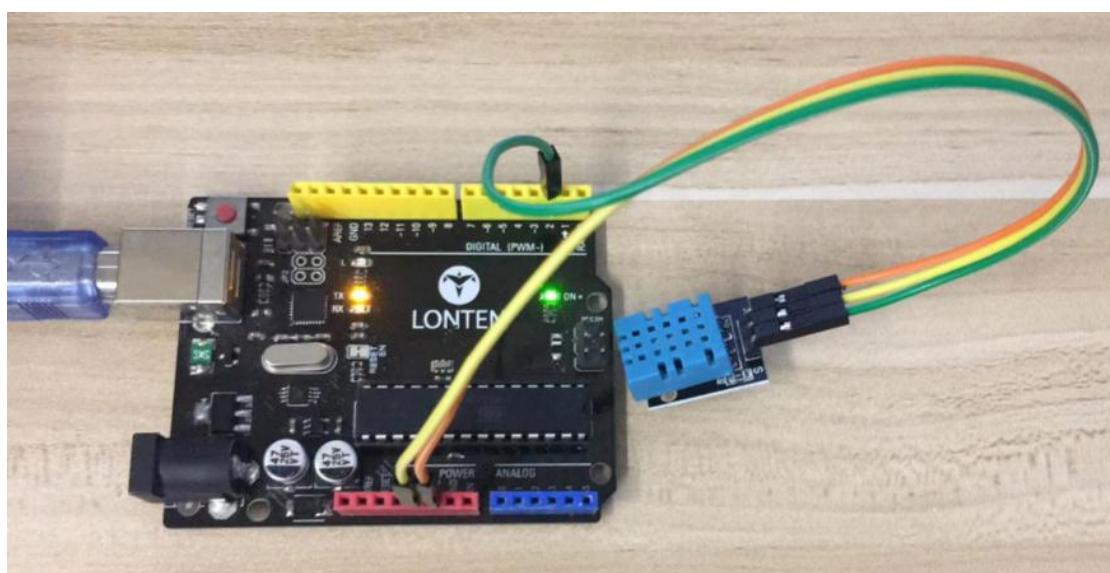

## Code


After wiring, please open the program in the code folder- Lesson 12 DHT11 Temperature and Humidity Sensor and click UPLOAD to upload the program.

Before you can run this, make sure that you have installed the <SimpleDHT> library or re-install it, if necessary. Otherwise, your code won't work.
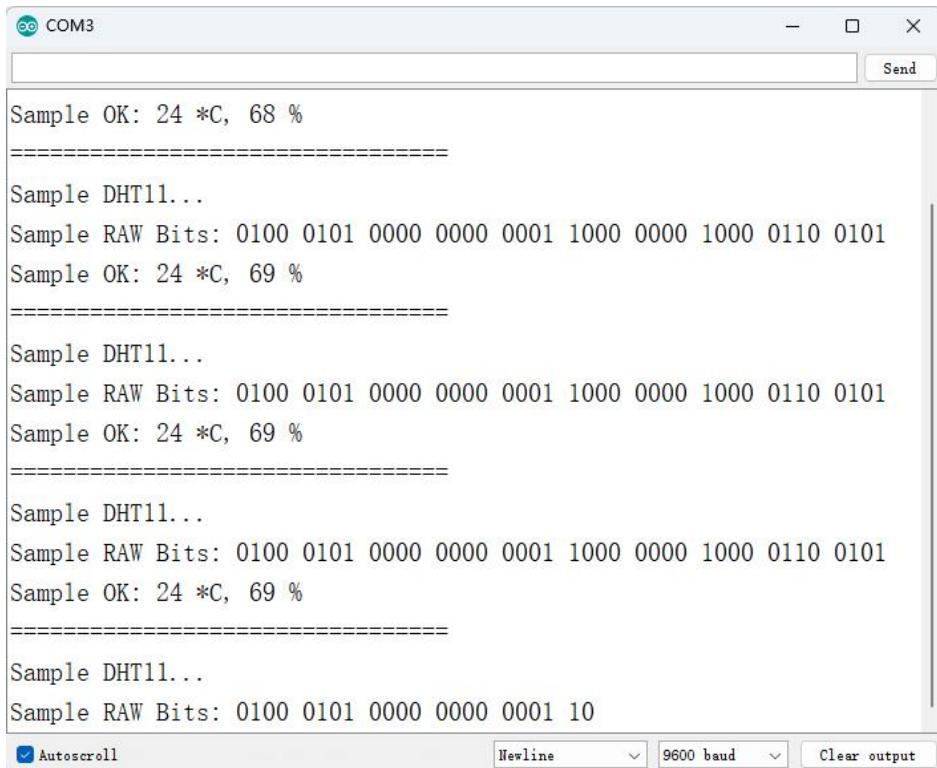
# LROBRYA

Upload the program then open the monitor, we can see the data as below:

(It shows the temperature of the environment, we can see it is 24 degree)



```
Sample OK: 24 *C, 68 %
=====
Sample DHT11...
Sample RAW Bits: 0100 0101 0000 0000 0001 1000 0000 1000 0110 0101
Sample OK: 24 *C, 69 %
=====
Sample DHT11...
Sample RAW Bits: 0100 0101 0000 0000 0001 1000 0000 1000 0110 0101
Sample OK: 24 *C, 69 %
=====
Sample DHT11...
Sample RAW Bits: 0100 0101 0000 0000 0001 1000 0000 1000 0110 0101
Sample OK: 24 *C, 69 %
=====
```

The terminal window has a title bar 'COM3'. At the bottom, there are buttons for 'Autoscroll' (checked), 'Newline', '9600 baud', and 'Clear output'.

## Lesson 13 Ultrasonic Sensor Module

### Overview

Ultrasonic sensor is great for all kind of projects that need distance measurements, avoiding obstacles as examples.

The HC-SR04 is inexpensive and easy to use since we will be using a Library specifically designed for these sensor.

### Component Required:

(1) x LONTEN Uno R3

# LROBRYA

---

- (1) x Ultrasonic sensor module
- (4) x F-M wires (Female to Male DuPont wires)

## Component Introduction

### Ultrasonic sensor



Ultrasonic sensor module HC-SR04 provides 2cm-400cm non-contact measurement function, the ranging accuracy can reach to 3mm. The module includes ultrasonic transmitters, receiver and control circuit. The basic principle of work:

- (1) Using IO trigger for at least 10us high level signal,
- (2) The Module automatically sends eight 40 kHz and detect whether there is a pulse signal back.
- (3) If the signal back, through high level , time of high output IO duration is the time from sending ultrasonic to turning.

$$\text{Test distance} = (\text{high level time} \times \text{velocity of sound (340m/s)}) / 2$$


# LROBRYA

The Timing diagram is shown below. You only need to supply a short 10us pulse to the trigger input to start the ranging, and then the module will send out an 8 cycle burst of ultrasound at 40 kHz and raise its echo.

The Echo is a distance object that is pulse width and the range in proportion .You can calculate the range through the time interval between sending trigger signal and receiving echo signal.

Formula: us / 58 = centimeters or us / 148 =inch; or: the range = high level time \* velocity (340M/S) / 2;

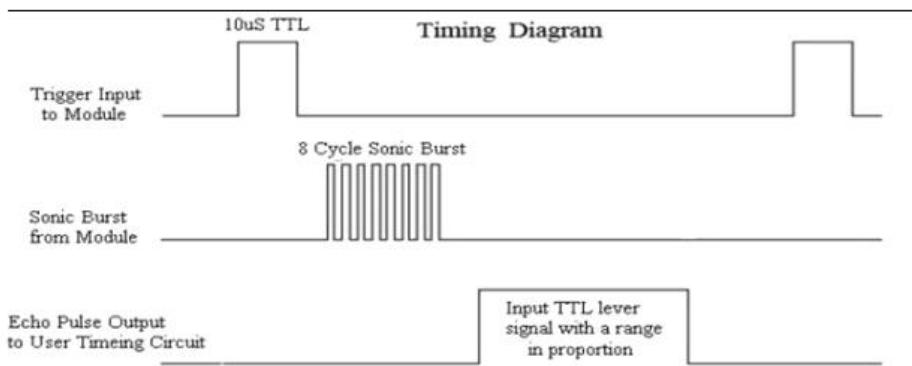
we suggest to use over 60ms measurement cycle, in order to prevent trigger signal to the echo signal.




## Connection

## Schematic

# LROBRUYA

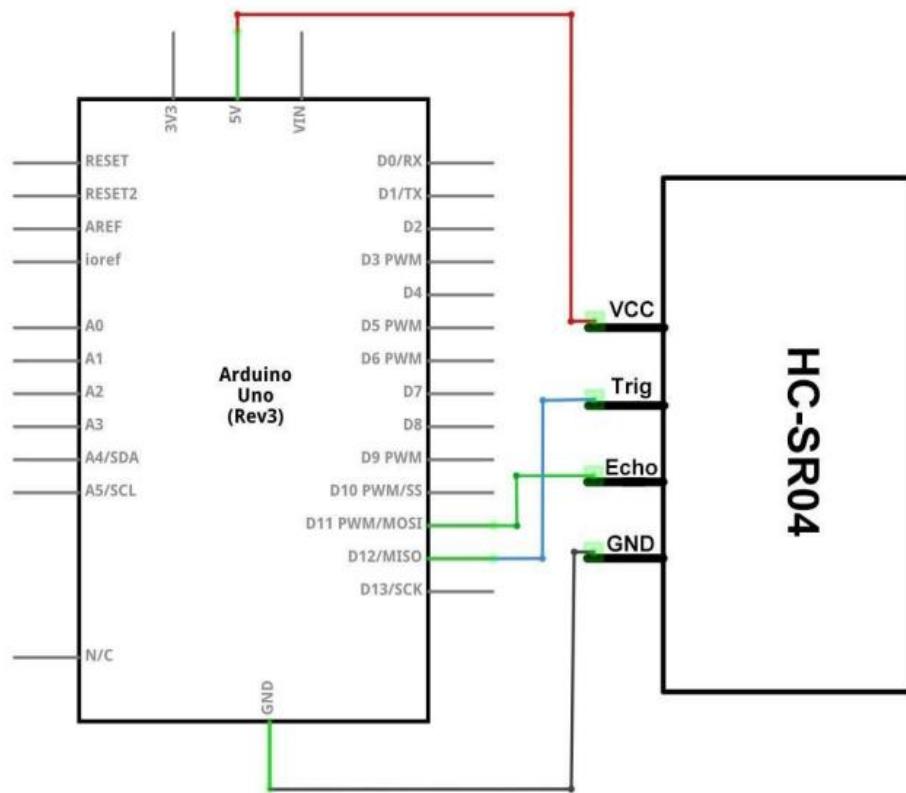


## Circuit Connection

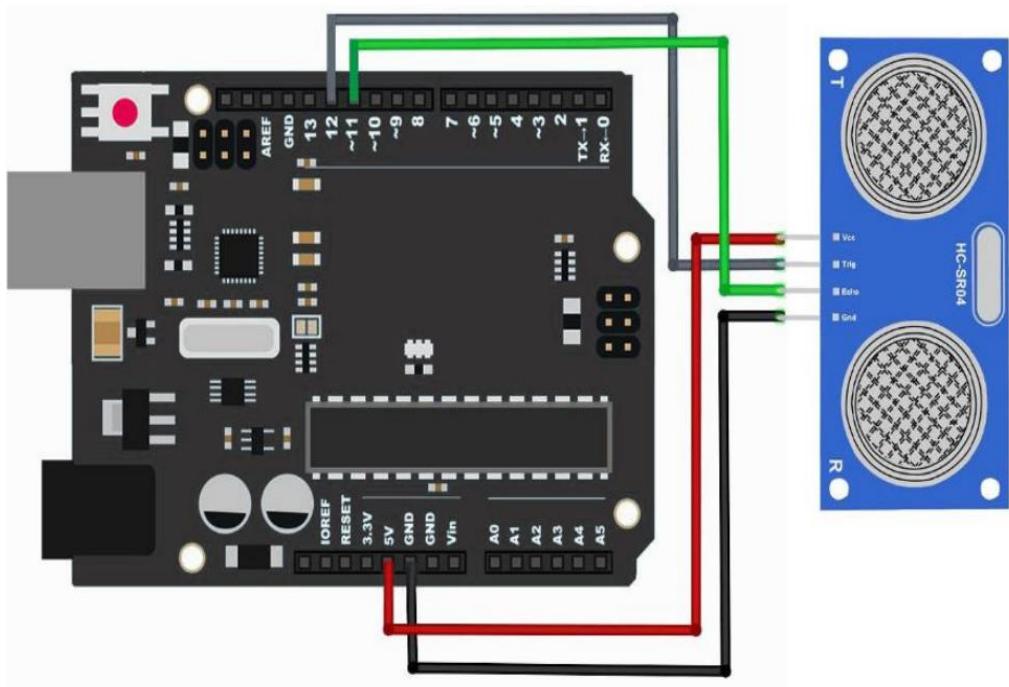

# LROBRYA

---

## Example picture

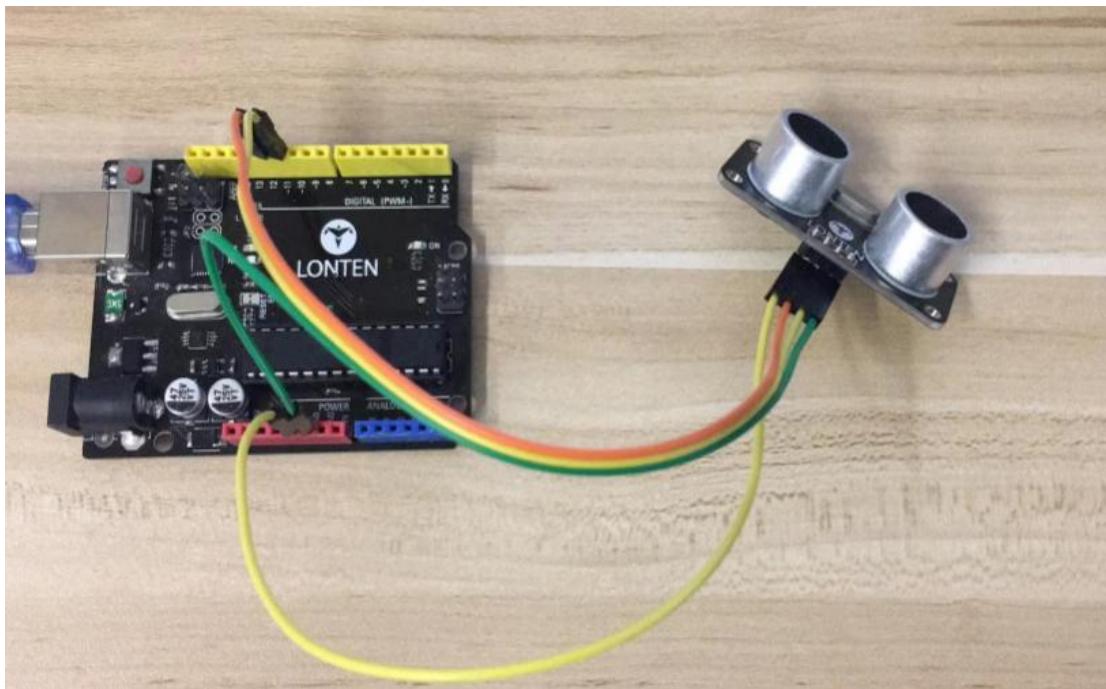

## Code

Using a Library designed for these sensors will make our code short and simple. We include the library at the beginning of our code, and then by using simple commands we can control the behavior of the sensor.


[After wiring, please open the program in the code folder- Lesson 13](#)

[Ultrasonic Sensor Module and click UPLOAD to upload the program.](#)

[Before you can run this, make sure that you have installed the <HC-SR04> library or re-install it, if necessary. Otherwise, your code won't work.](#)

Open the monitor then you can see the data as blow:

# LROBRYA

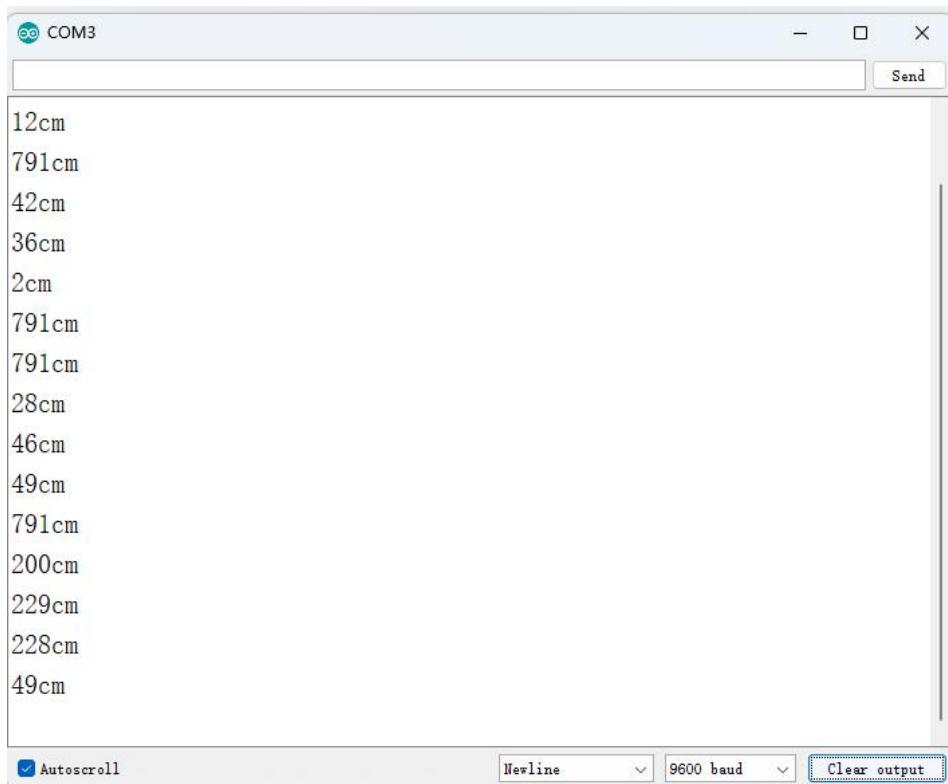

## Lesson 14 HC-SR501 PIR Sensor

### Overview

In this lesson you will learn how to use a PIR movement detector with an UNO. The UNO is the heart of this project. It 'listens' to the PIR sensor and when motion is detected, instructs the LED to light on or shut off.

### Component Required:

- (1) x LONTEN Uno R3
- (1) x HC-SR501 PIR motion sensor
- (3) x F-M wires (Female to Male DuPont wires)

### Component Introduction

# LROBRYA

---


## PIR SENSOR:



PIR sensors are more complicated than many of the other sensors explained in this tutorial (like photocells, FSRs and tilt switches) because there are multiple variables that affect the sensors input and output.

The PIR sensor itself has two slots. Each slot is made of a special material that is sensitive to IR. The lens used here is not really doing much and so we see that the two slots can 'see' out past some distance (basically the sensitivity of the sensor). When the sensor is idle, both slots detect the same amount of IR, the ambient amount radiated from the room or walls or outdoors. When a warm body like a human or an animal passes by, it first intercepts one half of the PIR sensor, which causes a positive differential change between the two halves. When the warm body leaves the sensing area, the reverse happens, whereby the sensor generates a negative differential change. These change pulses are what is detected.

# LROBRYA

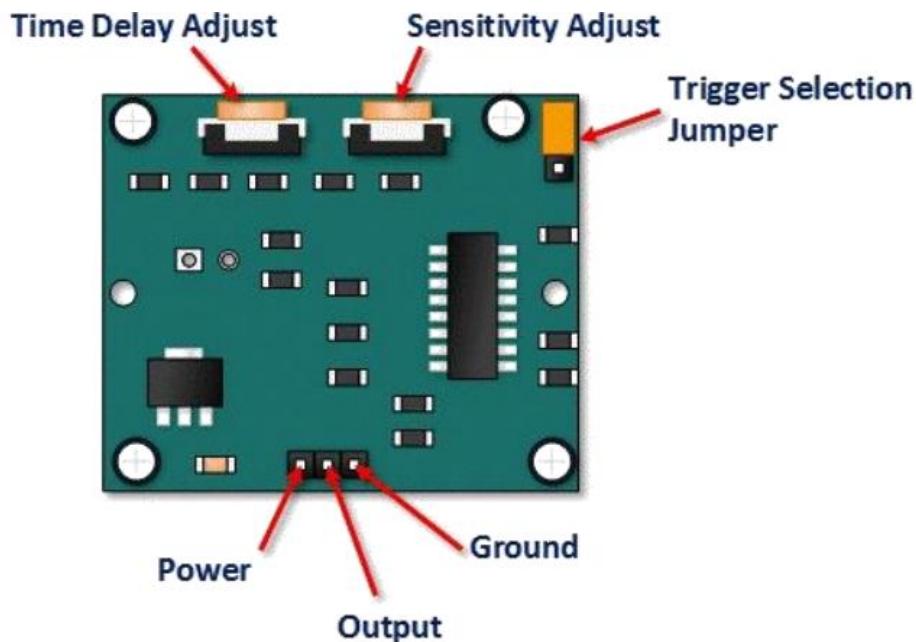

Pin or Control	Function
Time Delay Adjust	Sets how long the output remains high after detecting motion.... Anywhere from 5 seconds to 5 minutes.
Sensitivity Adjust	Sets the detection range.... from 3 meters to 7 meters
Trigger Selection Jumper	Set for single or repeatable triggers.
Ground pin	Ground input
Output Pin	Low when no motion is detected.. High when motion is detected. High is 3.3V
Power Pin	5 to 20 VDC Supply input

## HC SR501 PIR Functional Description

The SR501 will detect infrared changes and if interpreted as motion, will set its output low. What is or is not interpreted as motion is largely dependent on user settings and adjustments.

# LROBRYA


---

## Device Initialization

The device requires nearly a minute to initialize. During this period, it can and often will output false detection signals. Circuit or controller logic needs to take this initialization period into consideration.
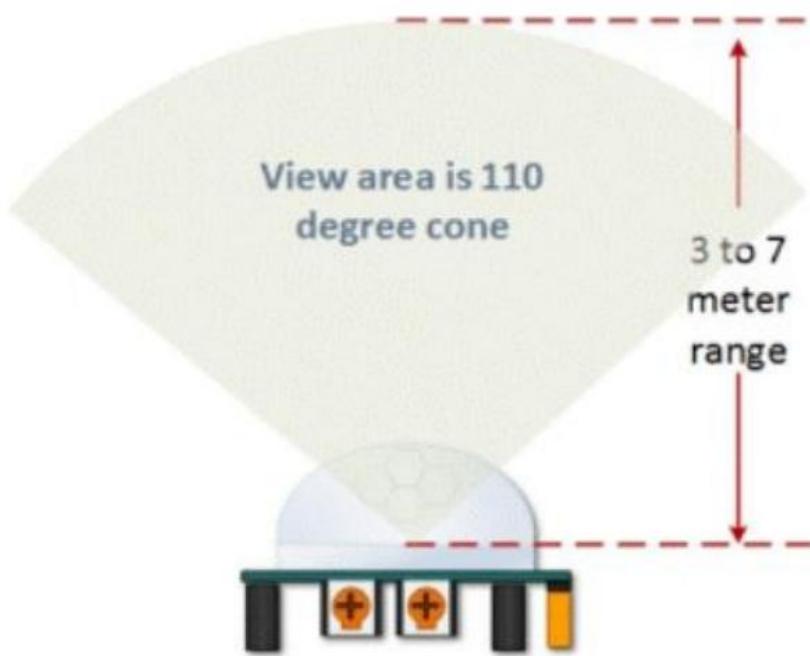
## Device Area of Detection

The device will detect motion inside a 110 degree cone with a range of 3 to 7 meters.




## HC SR501 View Area

### PIR Range (Sensitivity) Adjustment

As mentioned, the adjustable range is from approximately 3 to 7 meters.


The illustration below shows this adjustment.

# LROBRYA

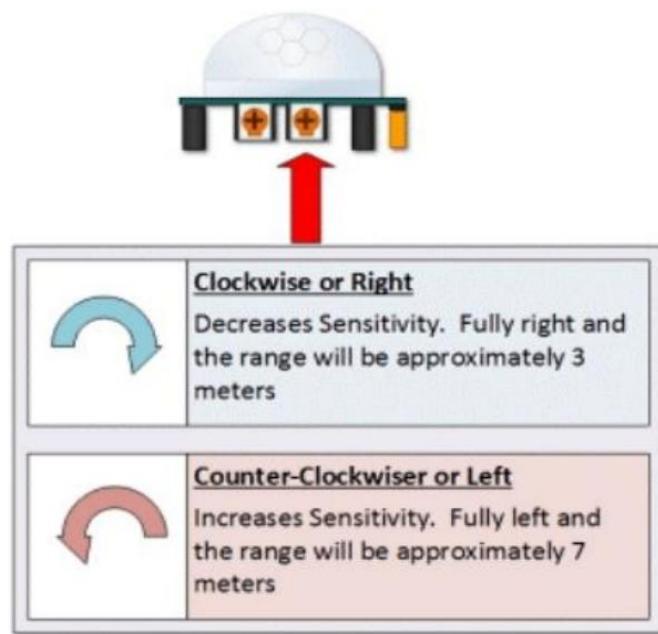
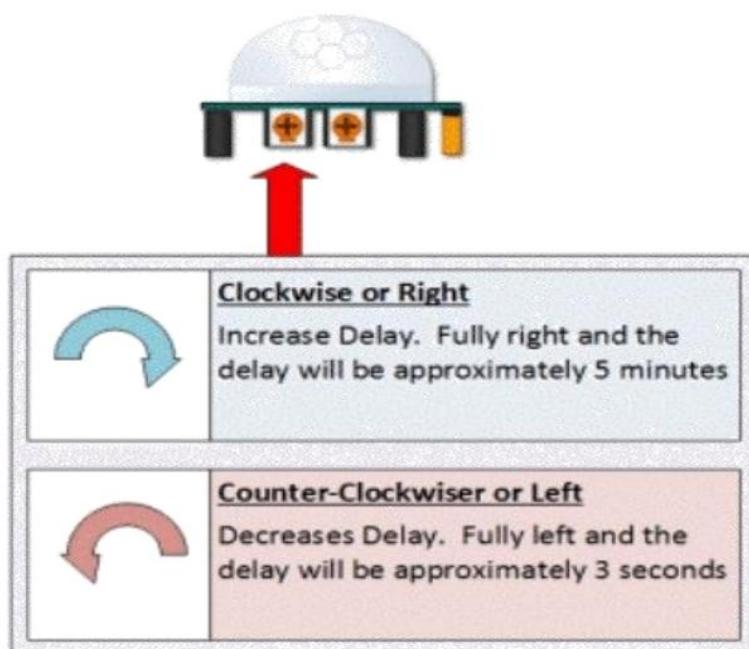
## HC SR501 Sensitivity Adjust Time Delay Adjustment

The time delay adjustment determines how long the output of the PIR sensor module will remain high after detection motion. The range is from about 3 seconds to five minutes.





---

## HC SR501 Time Delay Adjustment

### 3 Seconds Off After Time Delay Completes – IMPORTANT

The output of this device will go LOW (or Off) for approximately 3 seconds AFTER the time delay completes. In other words, ALL motion detection is blocked during this three second period.

#### **For Example:**

Imagine you're in the single trigger mode and your time delay is set 5 seconds.

The PIR will detect motion and set it high for 5 seconds.

After five seconds, the PIR will sets its output low for about 3 seconds.

During the three seconds, the PIR will not detect motion.

After three seconds, the PIR will detect motion again and detected motion will once again set the output high.

#### **Trigger Mode Selection Jumper**


The trigger mode selection jumper allows you to select between single and repeatable triggers. The affect of this jumper setting is to determine when the time delay begins.

**SINGLE TRIGGER** – The time delay begins immediately when motion is first detected.
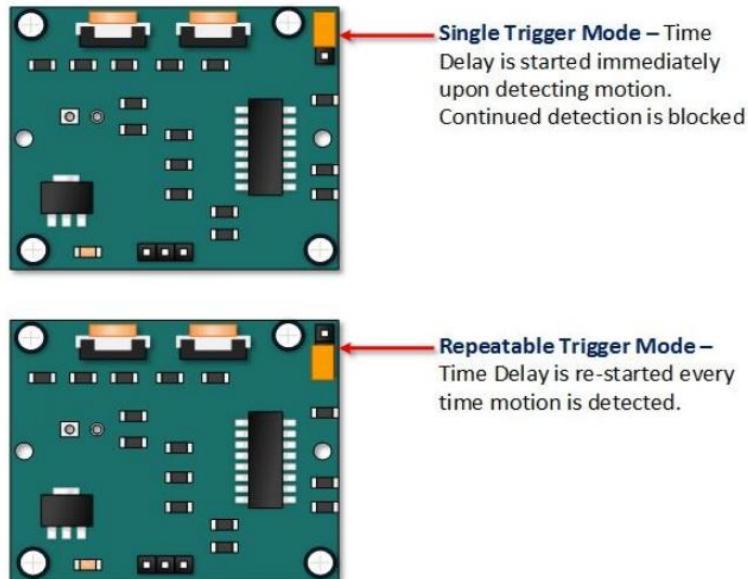
# LROBRYA

**REPEATABLE TRIGGER** – Each detected motion resets the time delay.

Thus the time delay begins with the last motion detected.



## HC-SR501 Dance Floor Application Examples


Imagine that you want to control lighting on a dance floor based upon where the dancers are dancing. Understanding how the time delay and trigger mode interact will be necessary to controlling that lighting in the manner that you want.

### Example One

In this first example, the time delay is set to three seconds and the trigger mode is set to single. As you can see in the illustration below, the motion is not always detected. In fact, there is a period of about six seconds
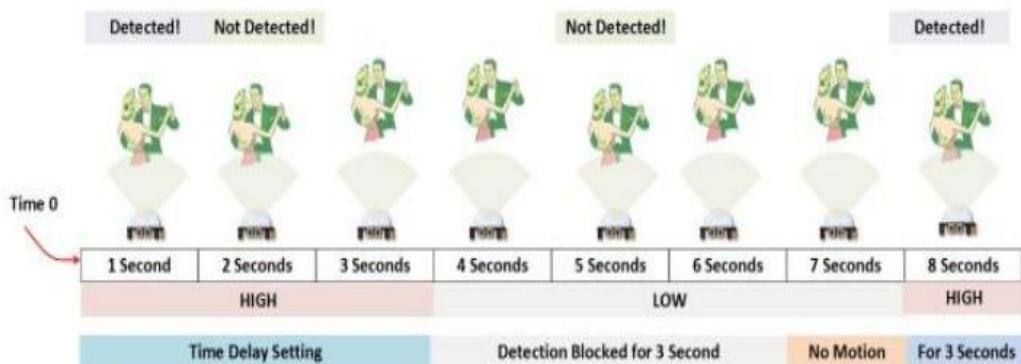
# LROBRYA

where motion can not be detected. Feel free to click on the image to enlarge.




## Example Two

In the next example, the time delay is still at three seconds and the trigger is set to repeatable. In the illustration below, you can see that the time delay period is restarted. However, after that three seconds, detection will still be blocked for three seconds.


As I mentioned previously, you could override the 3 second blocking period with some creative code, but do give that consideration. Some of the electronics you use may not like an on and then off jolt. The three seconds allows for a little rest before starting back up.

# LROBRUYA

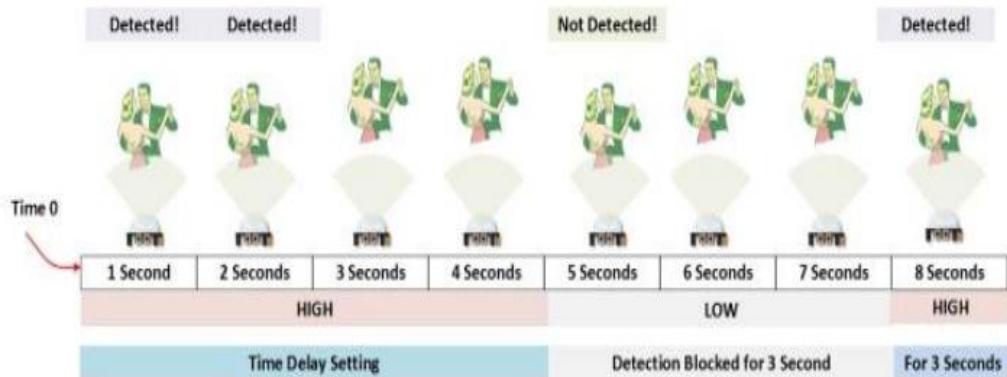


## Connection

### Schematic

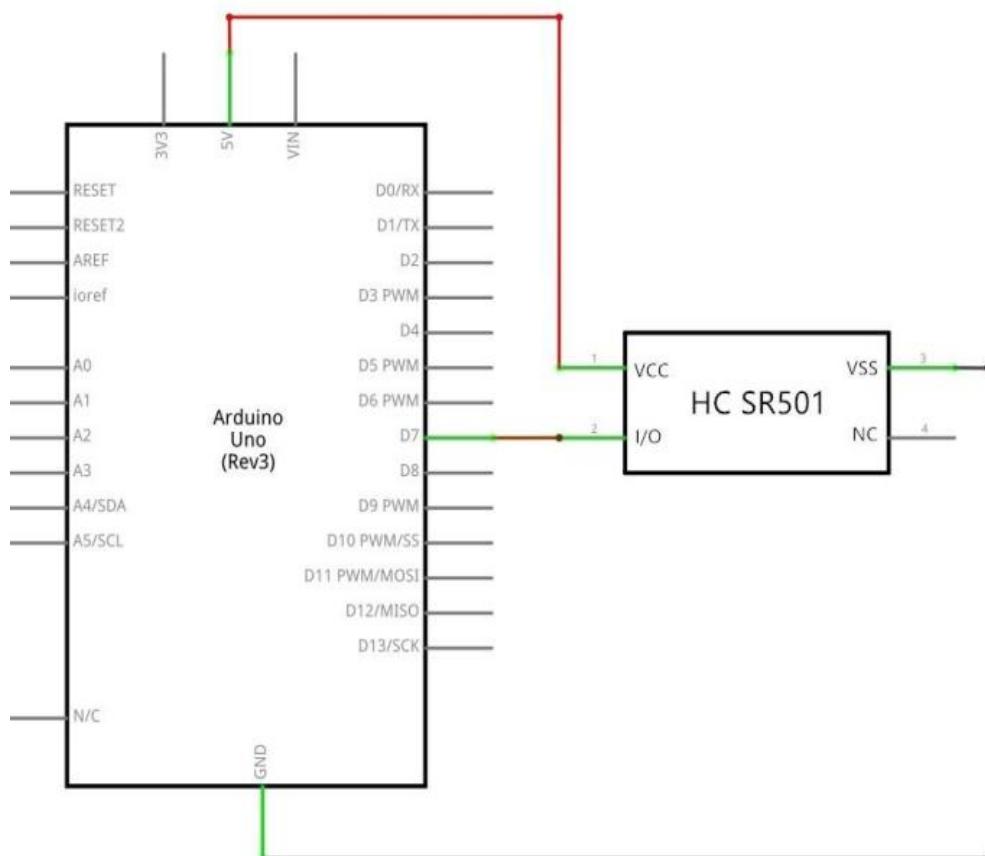


# LROBRUYA

## Circuit Connection

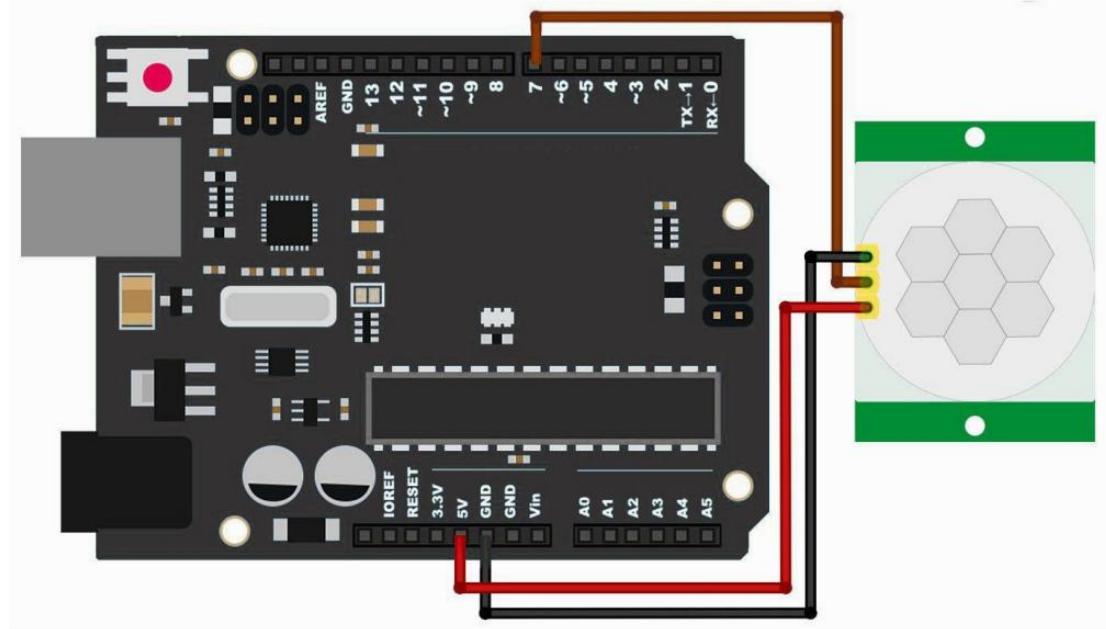

Example picture

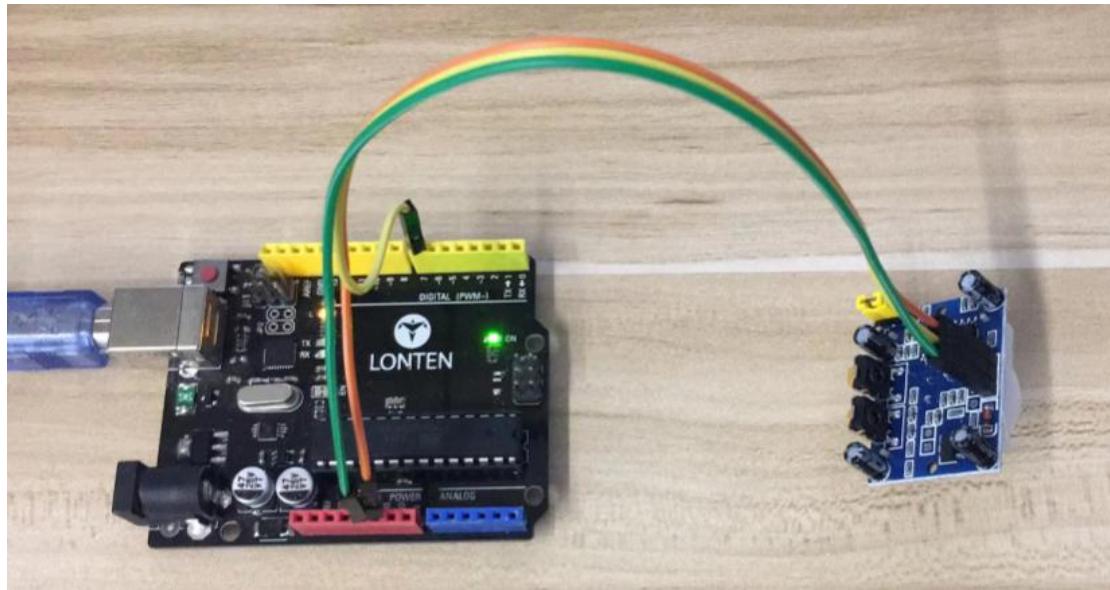

Connecting PIR sensors to a microcontroller is really simple. The PIR acts as a digital output so all you need to do is listen for the pin to flip high (detected) or low (not detected).



---

It's likely that you'll want retriggering, so be sure to put the jumper in the H position!

Power the PIR with 5V and connect ground to ground. Then connect the output to a digital pin. In this example, we'll use pin 7.

## Code

[After wiring, please open the program in the code folder- Lesson 14](#)

[HC-SR501 PIR Sensor and click UPLOAD to upload the program.](#)

The sketch simply turns on Your Arduino LED connected to Pin 13 whenever motion is detected.

**Be sure to beware of and somehow handle the 1 minute initialization in whatever application you develop.**

## Lesson 15 IR Receiver Module

### Overview

Using an IR Remote is a great way to have wireless control of your project. Infrared remotes are simple and easy to use. In this tutorial we will be connecting the IR receiver to the UNO, and then use a Library that was designed for this particular sensor.

# LROBRYA

---

In our sketch we will have all the IR Hexadecimal codes that are available on this remote, we will also detect if the code was recognized and also if we are holding down a key.

## **Component Required:**

- (1) x LONTEN Uno R3
- (1) x IR receiver module
- (1) x IR remote
- (3) x F-M wires (Female to Male DuPont wires)

## **Component Introduction**

### **IR RECEIVER SENSOR:**



IR detectors are little microchips with a photocell that are tuned to listen to infrared light. They are almost always used for remote control detection - every TV and DVD player has one of these in the front to listen for the IR signal from the clicker. Inside the remote control is a



matching IR LED, which emits IR pulses to tell the TV to turn on, off or change channels. IR light is not visible to the human eye, which means it takes a little more work to test a setup.

There are a few difference between these and say a CdS Photocells:


IR detectors are specially filtered for IR light, they are not good at detecting visible light. On the other hand, photocells are good at detecting yellow/green visible light, and are not good at IR light.

IR detectors have a demodulator inside that looks for modulated IR at 38 KHz. Just shining an IR LED won't be detected, it has to be PWM blinking at 38KHz.

Photocells do not have any sort of demodulator and can detect any frequency (including DC) within the response speed of the photocell (which is about 1Khz)IR detectors are digital out - either they detect 38Khz IR signal and output low (0V) or they do not detect any and output high (5V). Photocells act like resistors, the resistance changes depending on how much light they are exposed to.

# LROBRYA

## What You Can Measure

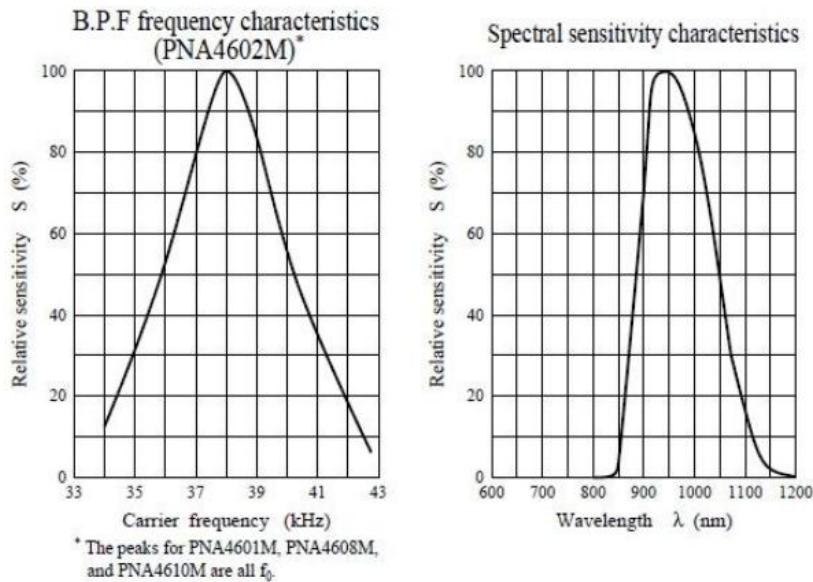

As you can see from these datasheet graphs, the peak frequency detection is at 38 KHz and the peak LED color is 940 nm. You can use from about 35 KHz to 41 KHz but the sensitivity will drop off so that it won't detect as well from afar. Likewise, you can use 850 to 1100 nm LEDs but they won't work as well as 900 to 1000nm so make sure to get matching LEDs! Check the datasheet for your IR LED to verify the wavelength. Try to get a 940nm - remember that 940nm is not visible light!

# LROBRUYA


Remote control code:



1	FFA25D	2	FF629D	3	FFE21D
4	FF22DD	5	FF02FD	6	FFC23D
7	FFE01F	8	FFA857	9	FF906F
*	FF6897	0	FF9867	#	FFB04F
			▲ FF18E7		
			◀ FF10EF	OK FF38C7	▶ FF5AA5
				▼ FF4AB5	

Connection


Schematic

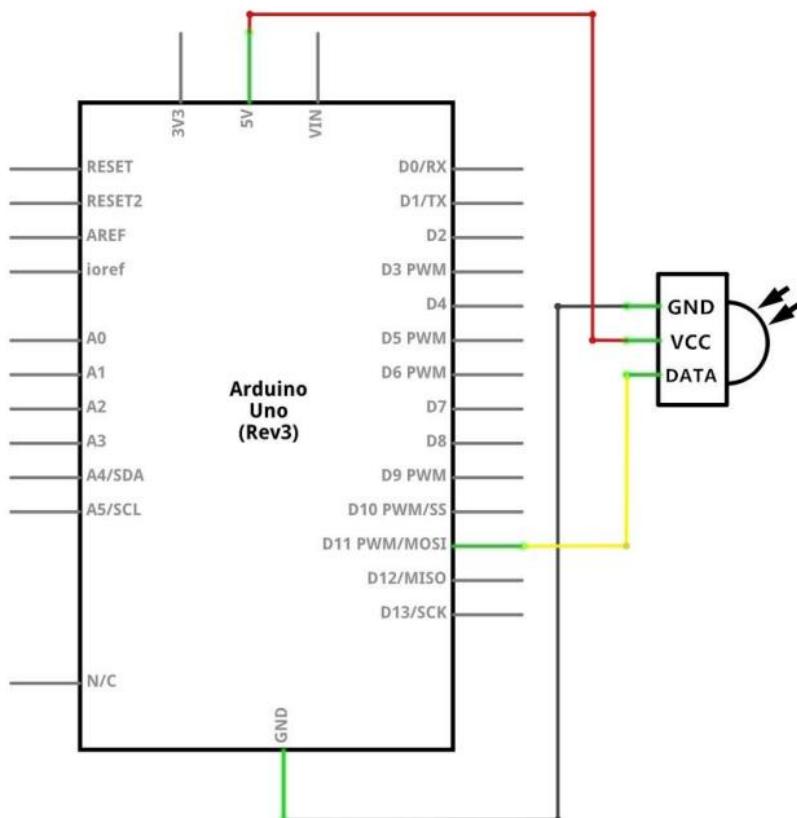

# LROBRYA

---

## Circuit Connection

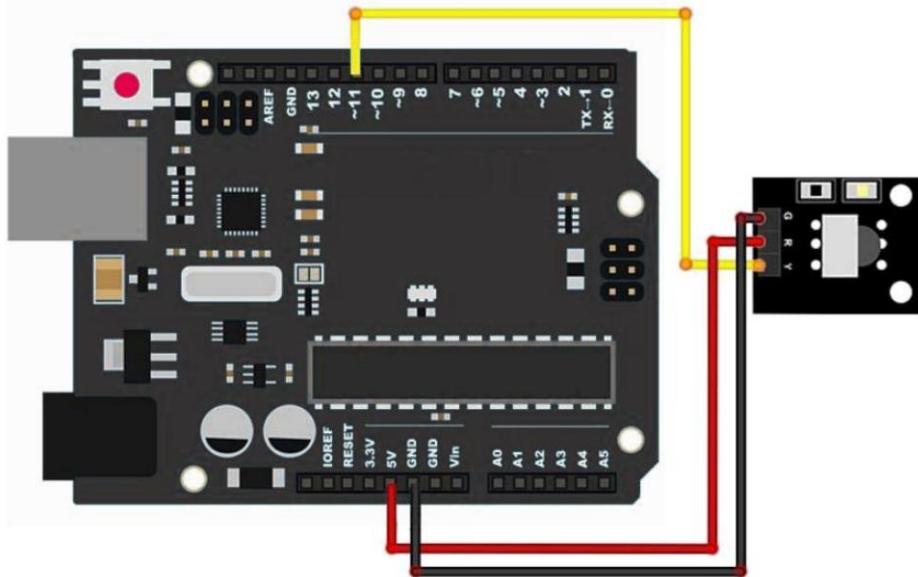


There are 3 connections to the IR Receiver.

The connections are: Signal, Voltage and Ground.

The “-” is the Ground, “S” is signal, and middle pin is Voltage 5V.

## Example picture

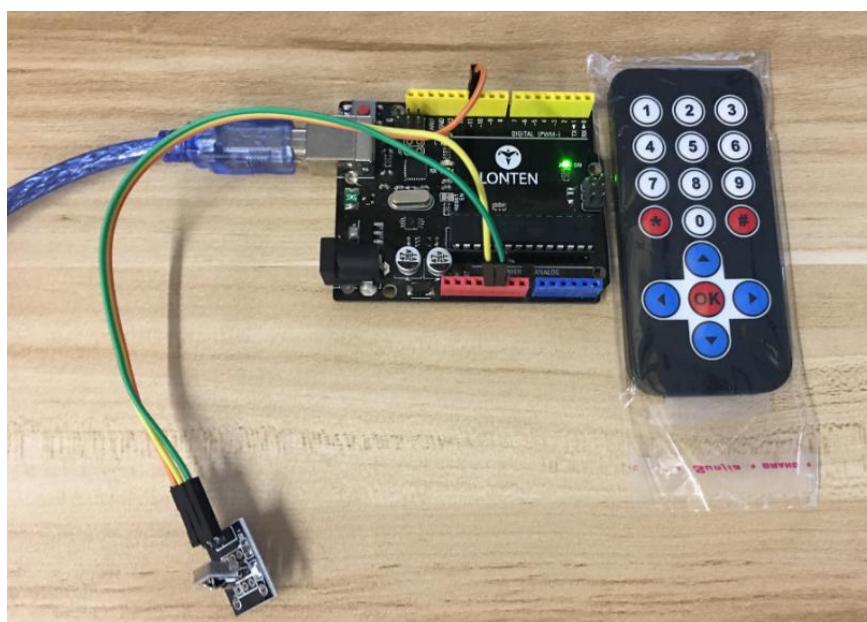



## Code

After wiring, please open the program in the code folder- Lesson 15 IR

Receiver Module and click UPLOAD to upload the program.

Before you can run this, make sure that you have installed the

<IRremote> library or re-install it, if necessary. Otherwise, your code

won't work.

Next we will move the <RobotIRremote> out of the Library folder, we do this because that library conflicts with the one we will be using. You can just drag it back inside the library folder once you are done programming your microcontroller. Once you have installed the Library, just go ahead and restart your IDE Software.

Open the monitor then you can see the data as blow:

A screenshot of a Windows-style serial monitor window titled "COM3". The window shows the output of an IR receiver button decode. The text in the window reads:

```
IR Receiver Button Decode
UP
REPEAT
DOWN
other button
LEFT
RIGHT
RIGHT
1
other button
other button
2
3
4
other button
```

At the bottom of the window, there are several control buttons: "Autoscroll" (checked), "Newline", "9600 baud" (selected), and "Clear output".



---

## Lesson 16 Membrane Switch Module

### Overview

In this project, we will go over how to integrate a keyboard with an UNO R3 board so that the UNO R3 can read the keys being pressed by a user.

Keypads are used in all types of devices, including cell phones, fax machines, microwaves, ovens, door locks, etc. They're practically everywhere. Tons of electronic devices use them for user input.

So knowing how to connect a keypad to a microcontroller such as an UNO R3 board is very valuable for building many different types of commercial products.

At the end when all is connected properly and programmed, when a key is pressed, it shows up at the Serial Monitor on your computer. Whenever you press a key, it shows up on the Serial Monitor. For simplicity purposes, we start at simply showing the key pressed on the computer.

For this project, the type of keypad we will use is a matrix keypad. This is a keypad that follows an encoding scheme that allows it to have much less output pins than there are keys. For example, the matrix keypad we are using has 16 keys (0-9, A-D, \*, #), yet only 8 output pins. With a linear keypad, there would have to be 17 output pins (one for each key and a ground pin) in order to work. The matrix encoding scheme allows

# LROBRYA

for less output pins and thus much less connections that have to make for the keypad to work. In this way, they are more efficient than linear keypads, being that they have less wiring.




## Component Required:

- (1) x LONTEN Uno R3
- (1) x Membrane switch module
- (8) x M-M wires (Male to Male jumper wires)


## Connection

### Schematic

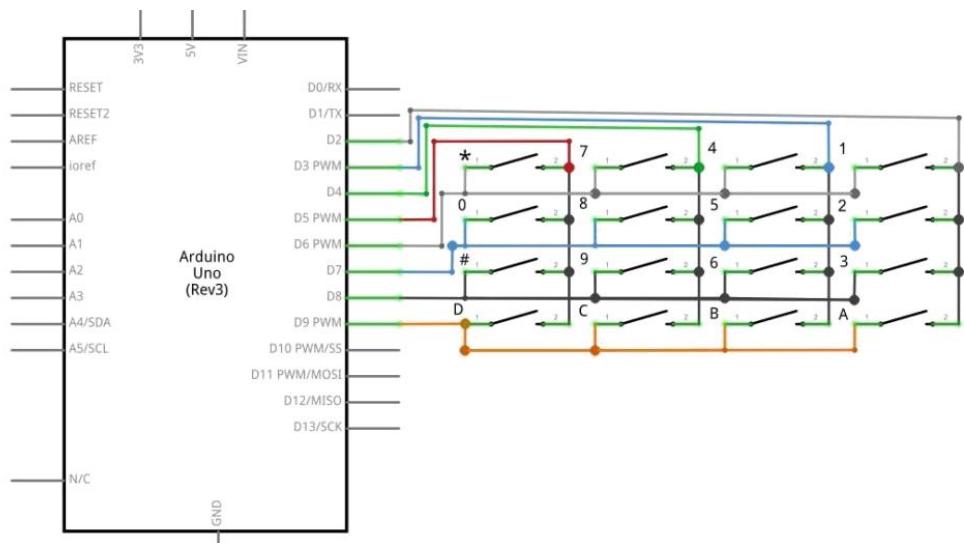

# LROBRUYA

## Circuit Connection

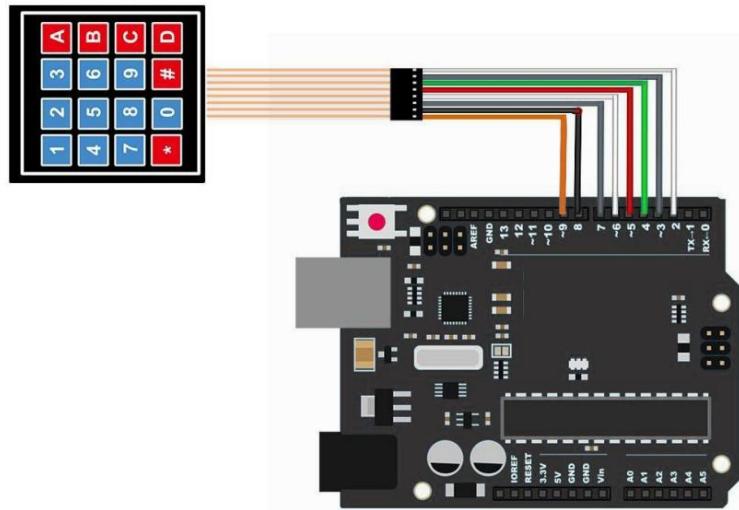

When connecting the pins to the UNO R3 board, we connect them to the digital output pins, D9-D2. We connect the first pin of the keypad to D9, the second pin to D8, the third pin to D7, the fourth pin to D6, the fifth pin to D5, the sixth pin to D4, the seventh pin to D3, and the eighth pin to D2.


These are the connections in a table:

Keypad Pin	Connects to Arduino Pin...
1	D9
2	D8
3	D7
4	D6
5	D5
6	D4

# LROBRYA

7	D3
8	D2

## Example picture

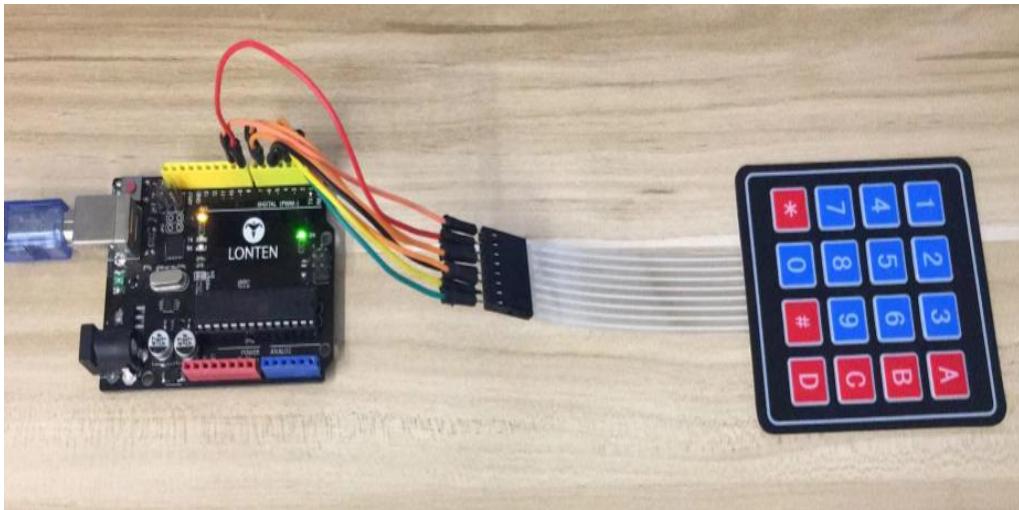

## Code

After wiring, please open the program in the code folder- Lesson 16

Membrane Switch Module and click UPLOAD to upload the program.

Before you can run this, make sure that you have installed the < Keypad> library or re-install it, if necessary. Otherwise, your code won't work.

With this code, once we press a key on the keypad, it should show up on the serial monitor of the Arduino software once the code is compiled and uploaded to the UNO R3 board.



---

## Lesson 17 Eight LED with 74HC595

### Overview

In this lesson, you will learn how to use eight large red LEDs with an UNO without needing to give up 8 output pins!

Although you could wire up eight LEDs each with a resistor to an UNO pin you would rapidly start to run out of pins on your UNO. If you don't have a lot of stuff connected to your UNO. It's OK to do so - but often times we want buttons, sensors, servos, etc. and before you know it you've got no pins left. So, instead of doing that, you are going to use a chip called the 74HC595 Serial to Parallel Converter. This chip has eight outputs (perfect) and three inputs that you use to feed data into it a bit at a time.

This chip makes it a little slower to drive the LEDs (you can only change the LEDs about 500,000 times a second instead of 8,000,000 a second) but it's still really fast, way faster than humans can detect, so it's worth it!

### Component Required:

(1) x LONTEN Uno R3

(1) x 830 tie-points breadboard

(8) x leds

(8) x 220 ohm resistors

# LROBRUYA

---

(1) x 74hc595 IC

(14) x M-M wires (Male to Male jumper wires)



## Component Introduction

### 74HC595 Shift Register:



The shift register is a type of chip that holds what can be thought of as eight memory locations, each of which can either be a 1 or a 0. To set each of these values on or off, we feed in the data using the 'Data' and 'Clock' pins of the chip.

# LROBRYA

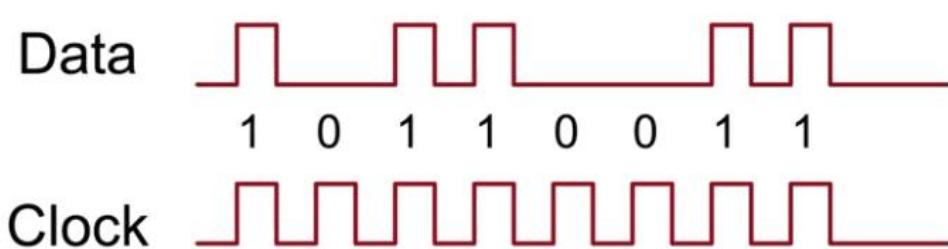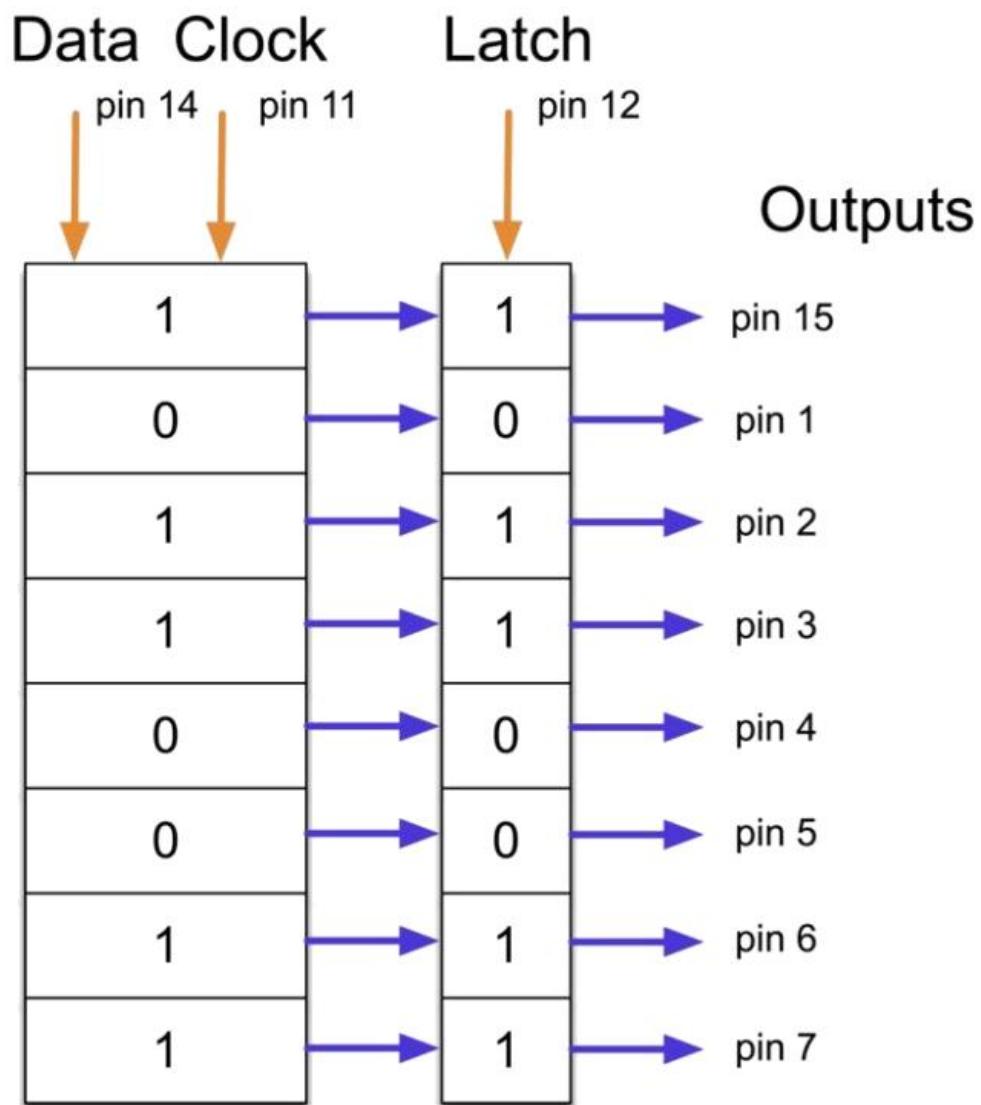

# LROBRYA


The clock pin needs to receive eight pulses. At each pulse, if the data pin is high, then a 1 gets pushed into the shift register; otherwise, a 0. When all eight pulses have been received, enabling the 'Latch' pin copies those eight values to the latch register. This is necessary; otherwise, the wrong LEDs would flicker as the data is being loaded into the shift register.

The chip also has an output enable (OE) pin, which is used to enable or disable the outputs all at once. You could attach this to a PWM-capable UNO pin and use 'analogWrite' to control the brightness of the LEDs.

This pin is active low, so we tie it to GND.


## Connection

### Schematic

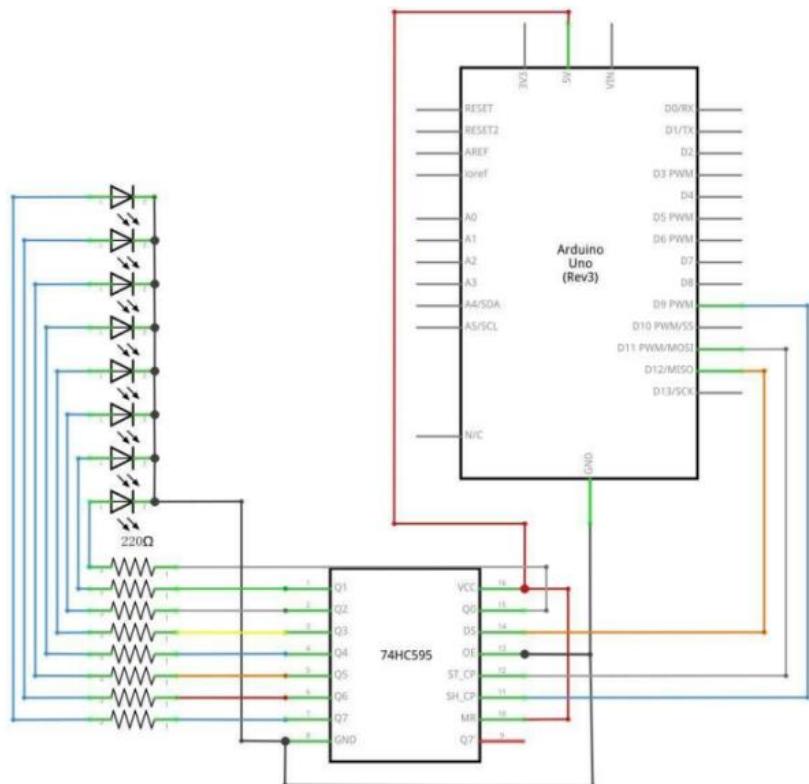

# LROBRYA

## Circuit Connection

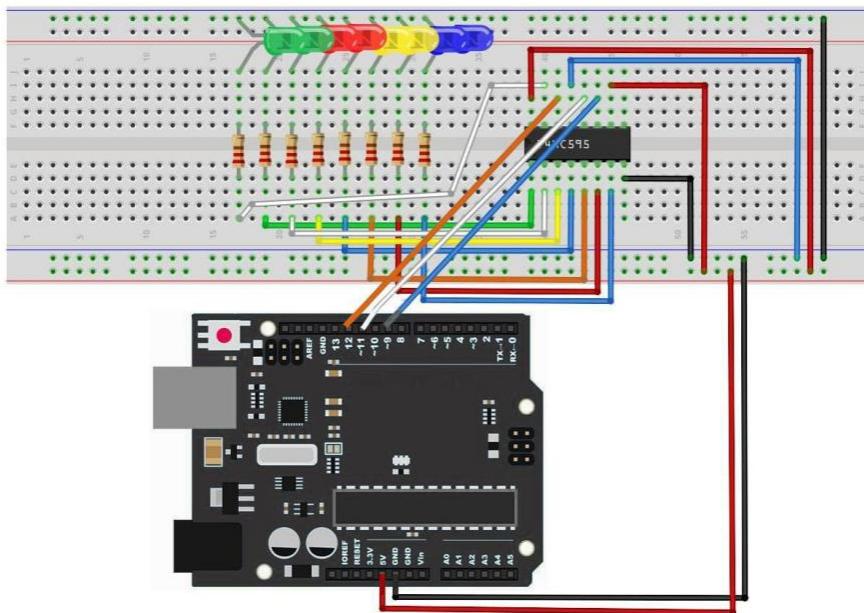

As we have eight LEDs and eight resistors to connect, there are actually quite a few connections to be made.

It is probably easiest to put the 74HC595 chip in first, as pretty much everything else connects to it. Put it so that the little U-shaped notch is towards the top of the breadboard. Pin 1 of the chip is to the left of this notch.

Digital 12 from the UNO goes to pin #14 of the shift register

Digital 11 from the UNO goes to pin #12 of the shift register

Digital 9 from the UNO goes to pin #11 of the shift register

All but one of the outputs from the IC is on the left side of the chip.

Hence, for ease of connection, that is where the LEDs are, too.

# LROBRYA

---


After the chip, put the resistors in place. You need to be careful that none of the leads of the resistors are touching each other. You should check this again before you connect the power to your UNO. If you find it difficult to arrange the resistors without their leads touching, then it helps to shorten the leads so that they are lying closer to the surface of the breadboard.

Next, place the LEDs on the breadboard. The longer positive LED leads must all be towards the chip, whichever side of the breadboard they are on.

Attach the jumper leads as shown above. Do not forget the one that goes from pin 8 of the IC to the GND column of the breadboard.

Load up the sketch listed a bit later and try it out. Each LED should light in turn until all the LEDs are on, and then they all go off and the cycle repeats.

## Example picture

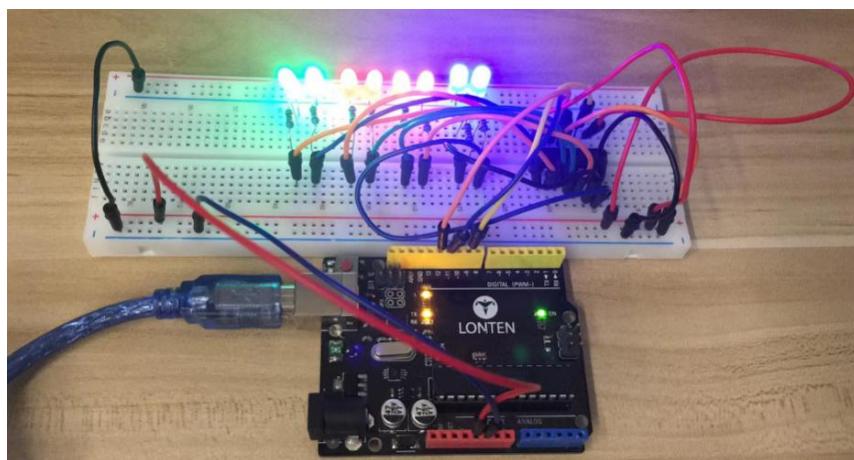



## Code

After wiring, please open the program in the code folder- Lesson 17 Eight LED with 74HC595 and click UPLOAD to upload the program.

The first thing we do is define the three pins we are going to use. These are the UNO digital outputs that will be connected to the latch, clock and data pins of the 74HC595.

```
int latchPin = 11;  
int clockPin = 9;  
int dataPin = 12;
```

Next, a variable called 'leds' is defined. This will be used to hold the pattern of which LEDs are currently turned on or off. Data of type 'byte' represents numbers using eight bits. Each bit can be either on or off, so this is perfect for keeping track of which of our eight LEDs are on or off.

```
byte leds = 0;
```

The 'setup' function just sets the three pins we are using to be digital outputs.

```
void setup()  
{  
    pinMode(latchPin, OUTPUT);  
    pinMode(dataPin, OUTPUT);
```



```
pinMode(clockPin, OUTPUT);  
}
```

The 'loop' function initially turns all the LEDs off, by giving the variable 'leds' the value 0. It then calls 'updateShiftRegister' that will send the 'leds' pattern to the shift register so that all the LEDs turn off. We will deal with how 'updateShiftRegister' works later.

The loop function pauses for half a second and then begins to count from 0 to 7 using the 'for' loop and the variable 'i'. Each time, it uses the Arduino function 'bitSet' to set the bit that controls that LED in the variable 'leds'. It then also calls 'updateShiftRegister' so that the leds update to reflect what is in the variable 'leds'.

There is then a half second delay before 'i' is incremented and the next LED is lit.

```
void loop()  
{  
    leds = 0;  
    updateShiftRegister();  
    delay(500);  
    for (int i = 0; i < 8; i++)  
    {
```



```
bitSet(leds, i);

updateShiftRegister();

delay(500);

}

}
```

The function 'updateShiftRegister', first of all sets the latchPin to low, then calls the UNO function 'shiftOut' before putting the 'latchPin' high again. This takes four parameters, the first two are the pins to use for Data and Clock respectively.

The third parameter specifies which end of the data you want to start at. We are going to start with the right most bit, which is referred to as the 'Least Significant Bit' (LSB).

The last parameter is the actual data to be shifted into the shift register, which in this case is 'leds'.

```
void updateShiftRegister()

{
    digitalWrite(latchPin, LOW);
    shiftOut(dataPin, clockPin, LSBFIRST, leds);
    digitalWrite(latchPin, HIGH);
}
```



---

If you wanted to turn one of the LEDs off rather than on, you would call a similar Arduino function (`bitClear`) with the '`leds`' variable. This will set that bit of '`leds`' to be 0 and you would then just need to follow it with a call to '`updateShiftRegister`' to update the actual LEDs.

## **Lesson 18 Photocell**

### **Overview**

In this lesson, you will learn how to measure light intensity using an Analog Input.

You will build on lesson 17 and use the level of light to control the number of LEDs to be lit.

The photocell is at the bottom of the breadboard, where the pot was above.

### **Component Required:**

- (1) x LONTEN Uno R3
- (1) x 830 tie-points breadboard
- (8) x leds
- (8) x 220 ohm resistors
- (1) x 1k ohm resistor
- (1) x 74hc595 IC

# LROBRYA

---

(1) x Photoresistor (Photocell)

(16) x M-M wires (Male to Male jumper wires)

## Component Introduction


### PHOTOCELL:



The photocell used is of a type called a light dependent resistor, sometimes called an LDR. As the name suggests, these components act just like a resistor, except that the resistance changes in response to how much light is falling on them.

This one has a resistance of about  $50\text{ k}\Omega$  in near darkness and  $500\text{ }\Omega$  in bright light.

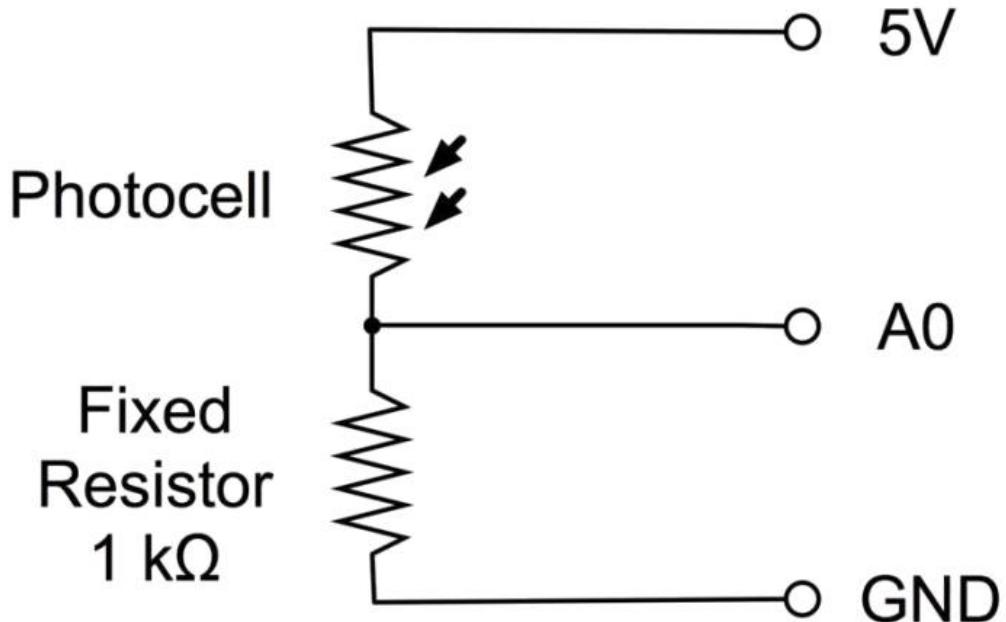To convert this varying value of resistance into something we can measure on an UNO R3 board's analog input, it needs to be converted into a voltage. The simplest way to do that is to combine it with a fixed resistor.



The resistor and photocell together behave like a pot. When the light is very bright, then the resistance of the photocell is very low compared with the fixed value resistor, and so it is as if the pot were turned to maximum.


When the photocell is in dull light, the resistance becomes greater than the fixed  $1\text{ k}\Omega$  resistor and it is as if the pot were being turned towards GND.

Load up the sketch given in the next section and try covering the photocell with your finger, and then holding it near a light source.

## Connection


## Schematic

# LROBRUYA

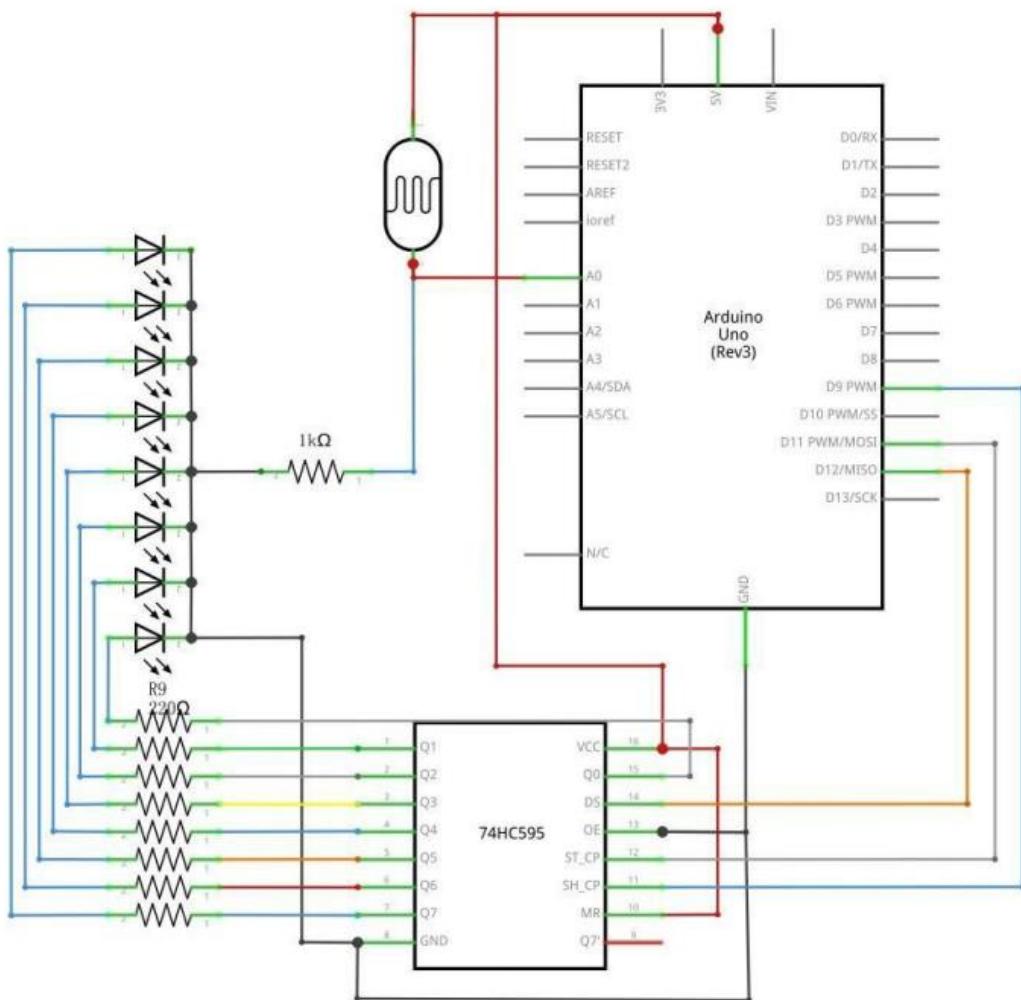


## Circuit Connection

# LROBRYA

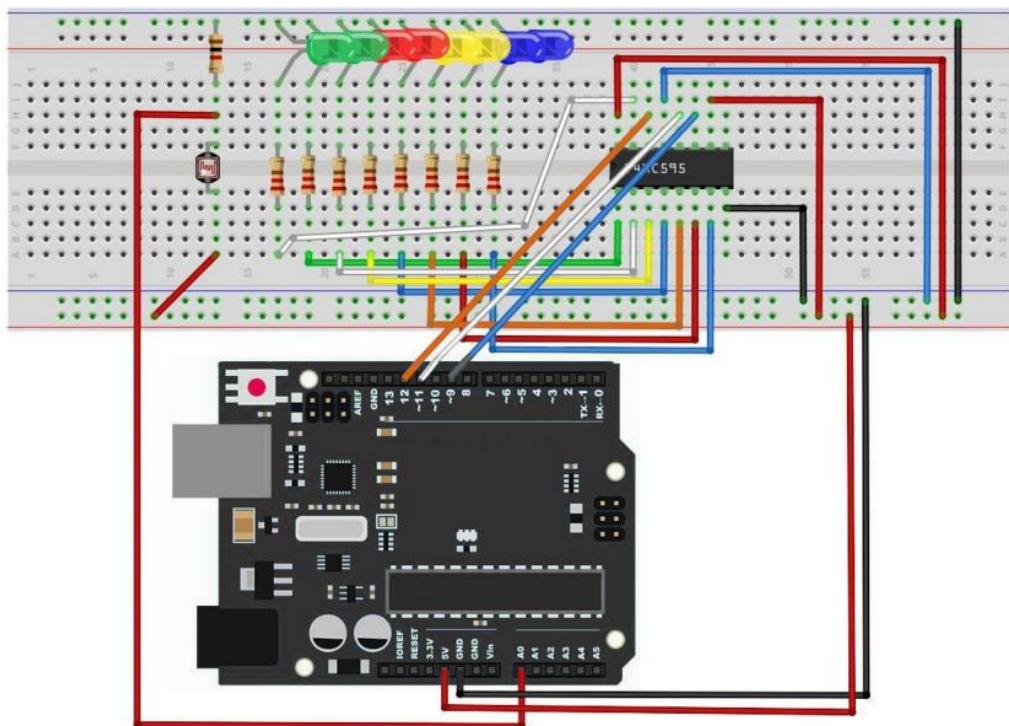

Example picture

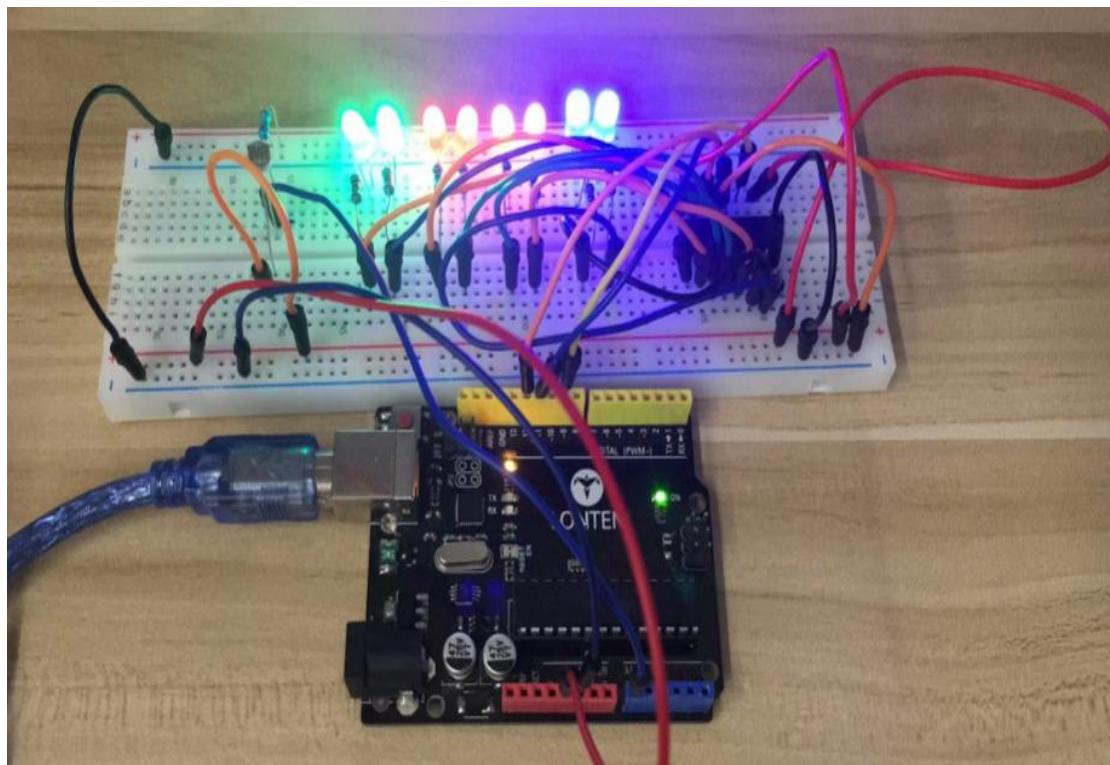



## Code

After wiring, please open the program in the code folder- Lesson 18

Photocell and click UPLOAD to upload the program.

The first thing to note is that we have changed the name of the analog pin to be 'lightPin' rather than 'potPin' since we no longer have a pot connected.

The only other substantial change to the sketch is the line that calculates how many of the LEDs to light:

```
int numLEDSLit = reading / 57; // all LEDs lit at 1k
```

This time, we divide the raw reading by 57 rather than 114. In other words, we divide it by half as much as we did with the pot to split it into nine zones, from no LEDs lit to all eight lit. This extra factor is to account for the fixed 1 kΩ resistor. This means that when the photocell has a resistance of 1 kΩ (the same as the fixed resistor), the raw reading will be  $1023 / 2 = 511$ . This will equate to all the LEDs being lit and then a bit (numLEDSLit) will be 8.



---

## Lesson 19 74HC595 And Segment Display

### Overview

In learning Lesson, we will use the 74HC595 shift register to control the segment display. The segment display will show number from 9-0.

### Component Required

(1) x LONTEN Uno R3

(1) x 830 tie-points breadboard

(1) x 74HC595 IC

(1) x 1 Digit 7-Segment Display

(8) x 220 ohm resistors

(26) x M-M wires (Male to Male jumper wires)

### Component Introduction


#### Seven segment display

LED segment displays are common for displaying numerical information.

It's widely applied on displays of electromagnetic oven, full automatic washing machine, water temperature display, electronic clock etc. It is necessary that we learn how it works. LED segment display is a semiconductor light-emitting device. Its basic unit is a light-emitting diode (LED). LED segment display can be divided into 7-segment display and 8-segment display according to the number of segments.

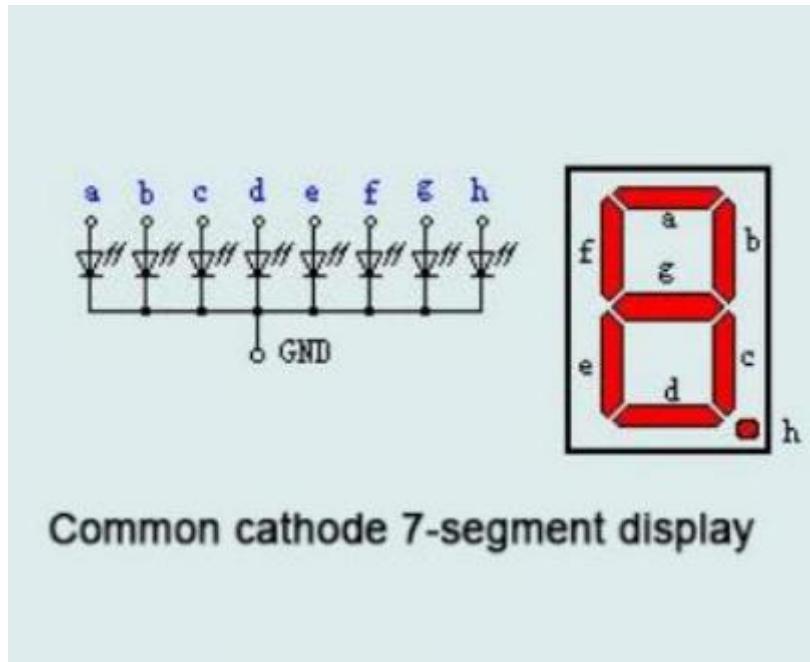
# LROB RUYA

8-segment display has one more LED unit ( for decimal point display) than 7-segment one. In this experiment, we use a 8-segment display.



According to the wiring method of LED units, LED segment displays can be divided into display with common anode and display with common cathode. Common anode display refers to the one that combine all the anodes of LED units into one common anode (COM).For the common anode display, connect the common anode (COM) to +5V. When the cathode level of a certain segment is low, the segment is on; when the cathode level of a certain segment is high, the segment is off. For the common cathode display, connect the common cathode (COM) to GND. When the anode level of a certain segment is high, the segment is on; when the anode level of a certain segment is low, the segment is off.

# LROB RUYA

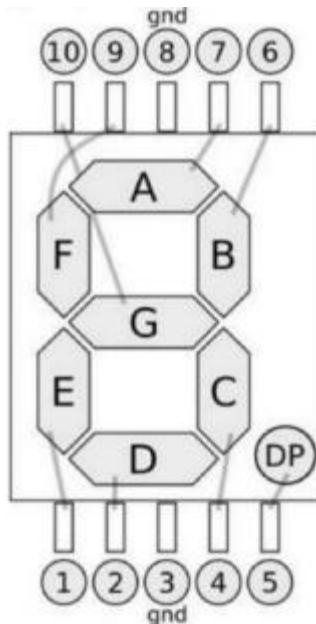

Each segment of the display consists of an LED. So when you use it, you also need use a current-limiting resistor. Otherwise, LED will be burnt out. In this experiment, we use a common cathode display. As we mentioned above, for common cathode display, connect the common cathode (COM) to GND. When the anode level of a certain segment is high, the segment is on; when the anode level of a certain segment is low, the segment is off.

## 74HC595

The following table shows the seven-segment display 74HC595 pin correspondence table:

74HC595 pin	Seven shows remarkable control pin (stroke)
-------------	---

# LROBRYA

---

Q0	7(A)
Q1	6(B)
Q2	4(C)
Q3	2(D)
Q4	1(E)
Q5	9(F)
Q6	10(G)
Q7	5(DP)

Step one: Connect 74HC595

First, the wiring is connected to power and ground:

**VCC** (pin 16) and **MR** (pin 10) connected to 5V

**GND** (pin 8) and **OE** (pin 13) to ground

Connection **DS**, **ST\_CP** and **SH\_CP**

pin:

**DS** (pin 14) connected to UNO R3 board pin 2 (the figure below the yellow line)

**ST\_CP** (pin 12, latch pin) connected to UNO R3 board pin 3 (FIG blue line below)

**SH\_CP** (pin 11, clock pin) connected to UNO R3 board pin 4 (the figure below the white line)

# LROBRYA


Step two: Connect the seven segment display

The seven-segment display 3, 8 pin to UNO R3 board GND (This example uses the common cathode, if you use the common anode, please connect the 3, 8 pin to UNO R3 board + 5V)

According to the table above, connect the 74HC595 Q0 ~ Q7 to seven-segment display corresponding pin (A ~ G and DP), and then each foot in a 220 ohm resistor in series.


## Connection

### Schematic

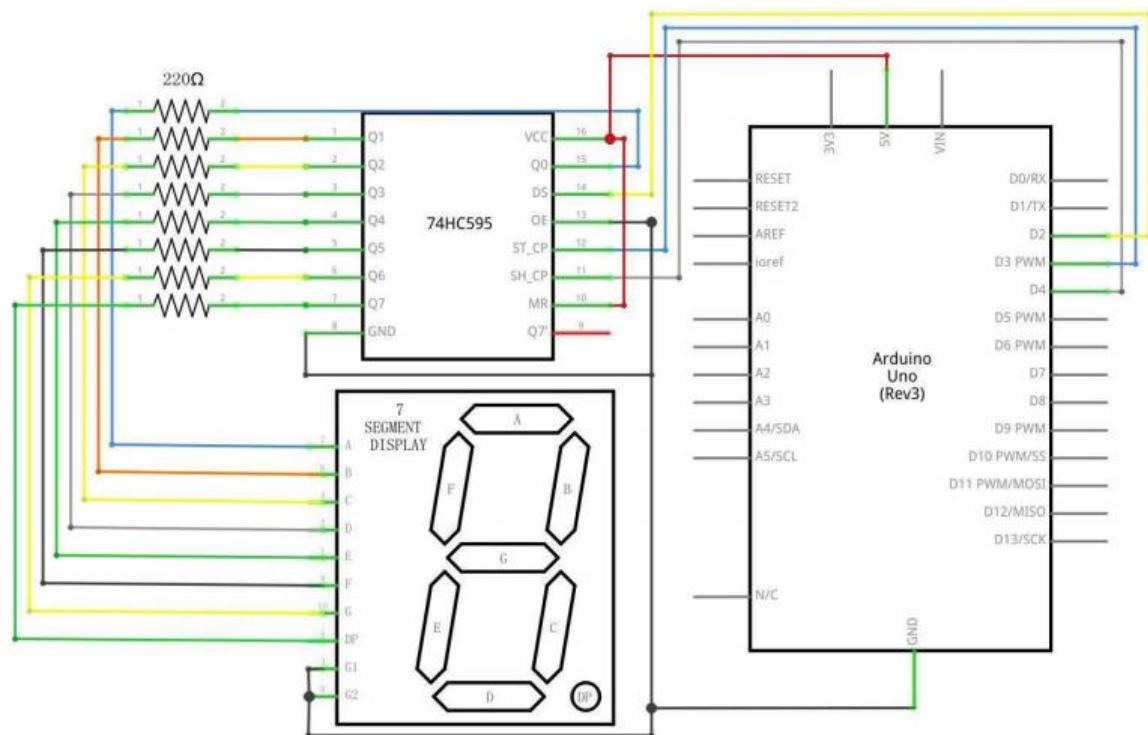


## Circuit Connection

# LROBRYA

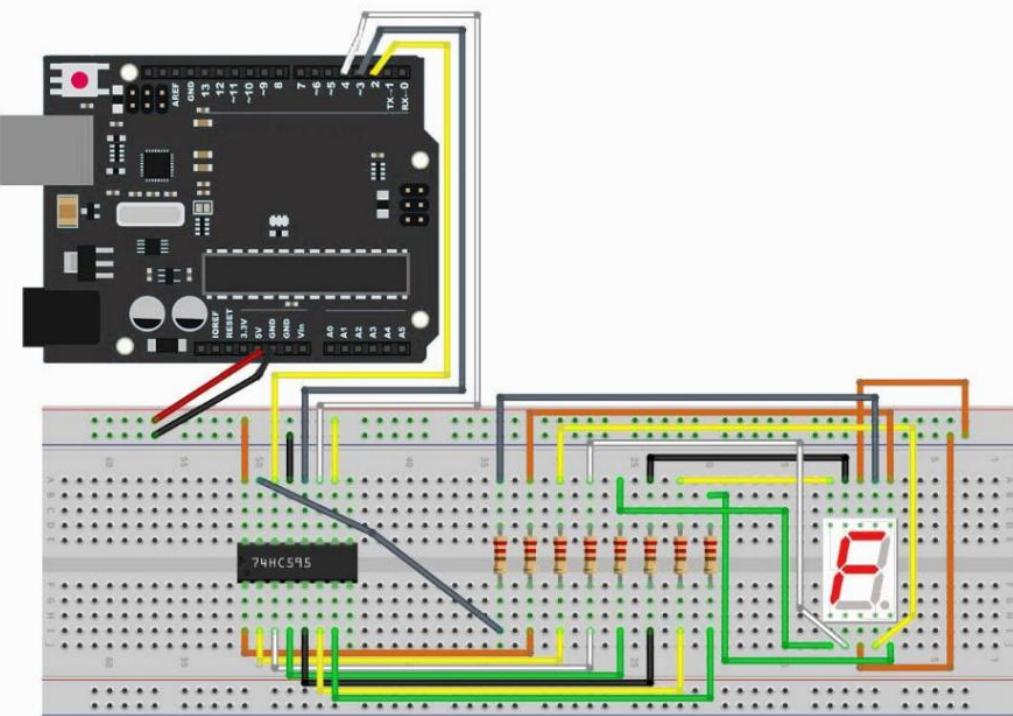

Example picture

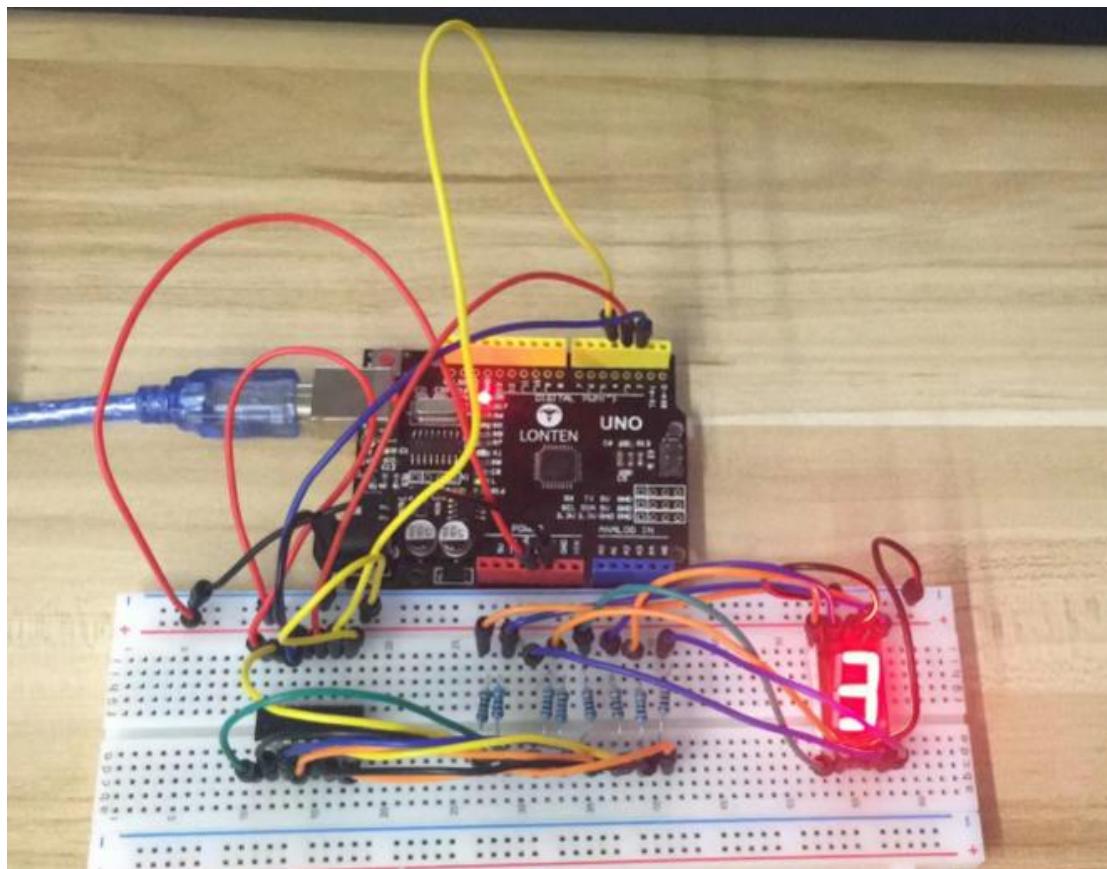



---

## Code

After wiring, please open the program in the code folder- Lesson 19 74HC595 And Segment Display and click UPLOAD to upload the program.

LED segment display repeat displays number 9 to 0.

## Lesson 20 Four Digital Seven Segment Display

### Overview

In this lesson, you will learn how to use a 4-digit 7-segment display.

When using 1-digit 7-segment display, please notice that if it is common anode, the common anode pin connects to the power source; if it is common cathode, the common cathode pin connects to the GND.

When using 4-digit 7-segment display, the common anode or common cathode pin is used to control which digit is displayed. Even though there is only one digit working, the principle of Persistence of Vision enables you to see all numbers displayed because each the scanning speed is so fast that you hardly notice the intervals.

### Component Required:

(1) x LONTEN Uno R3

(1) x 830 tie-points breadboard



---

(1) x 74HC595 IC

(1) x 4 Digit 7-Segment Display

(4) x 220 ohm resistors


(23) x M-M wires (Male to Male jumper wires)



## **Component Introduction**


### **Four Digital Seven segment display**

# LROBRUYA

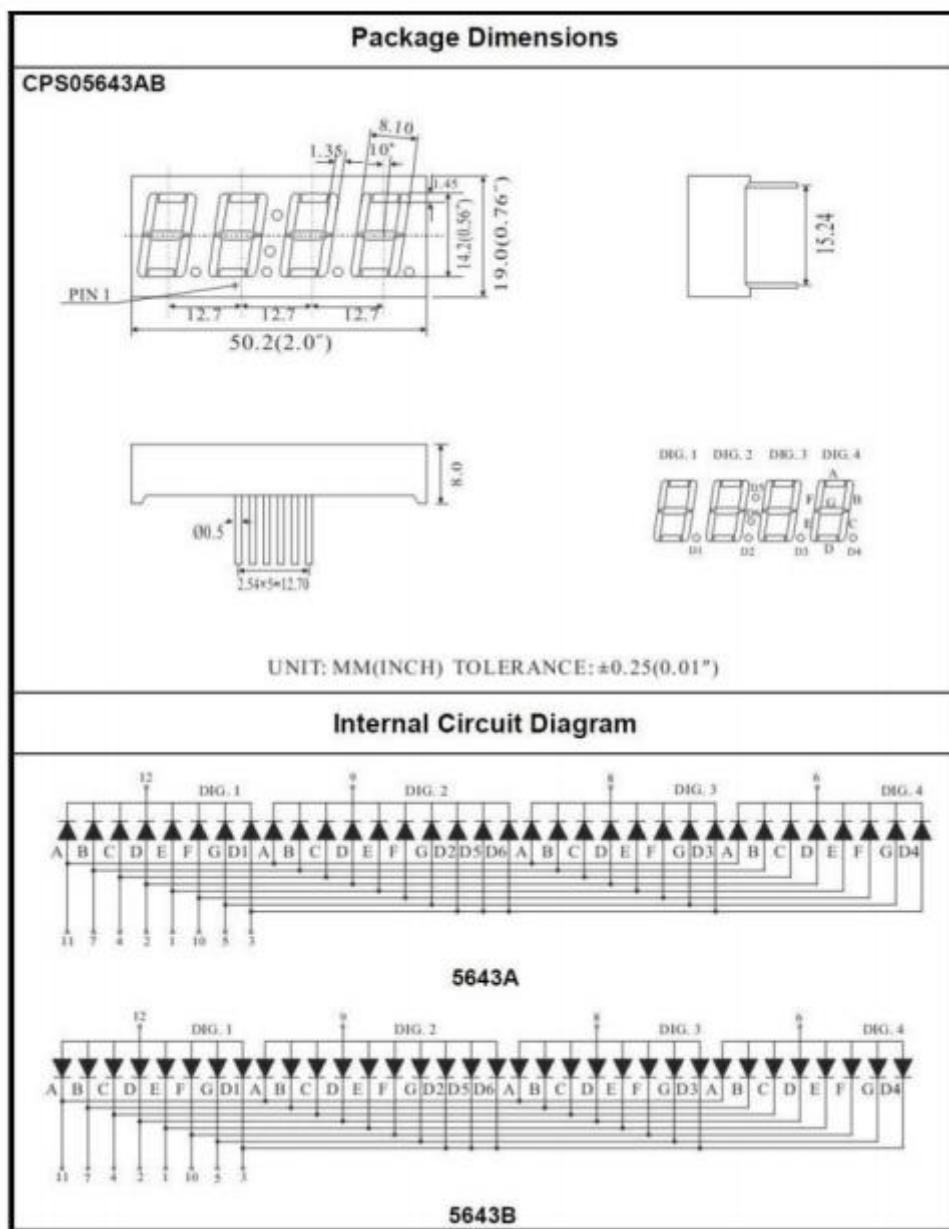


**Connection  
Schematic**

# LROBRYA

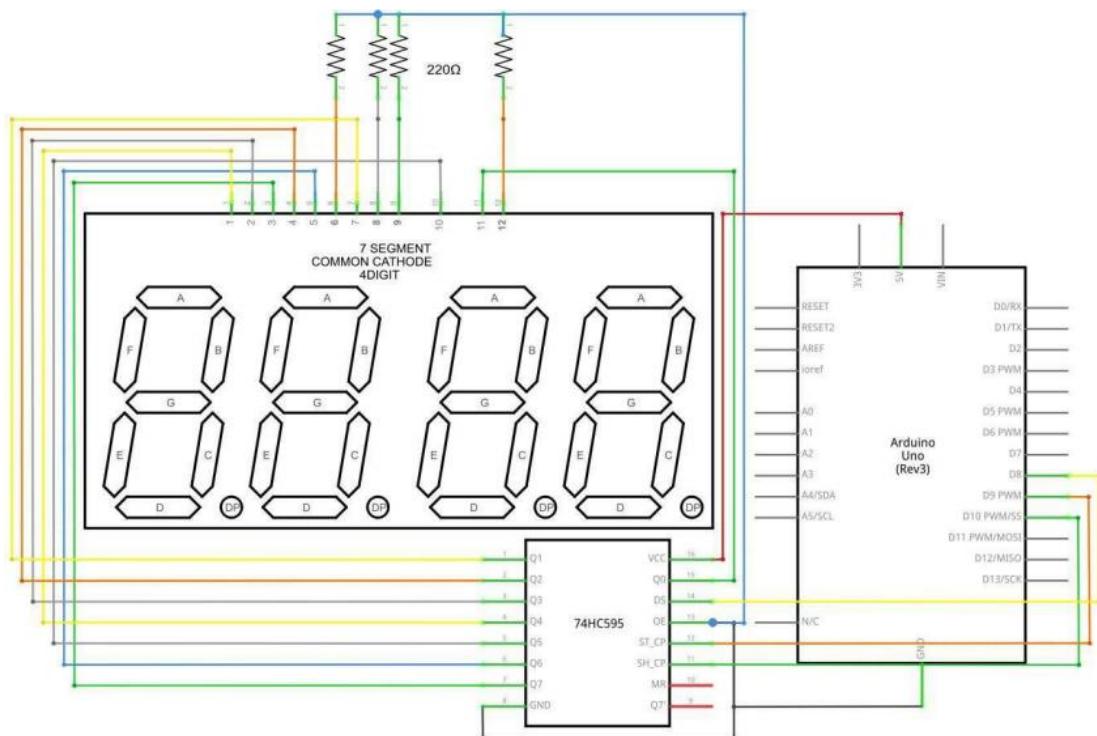


## Circuit Connection

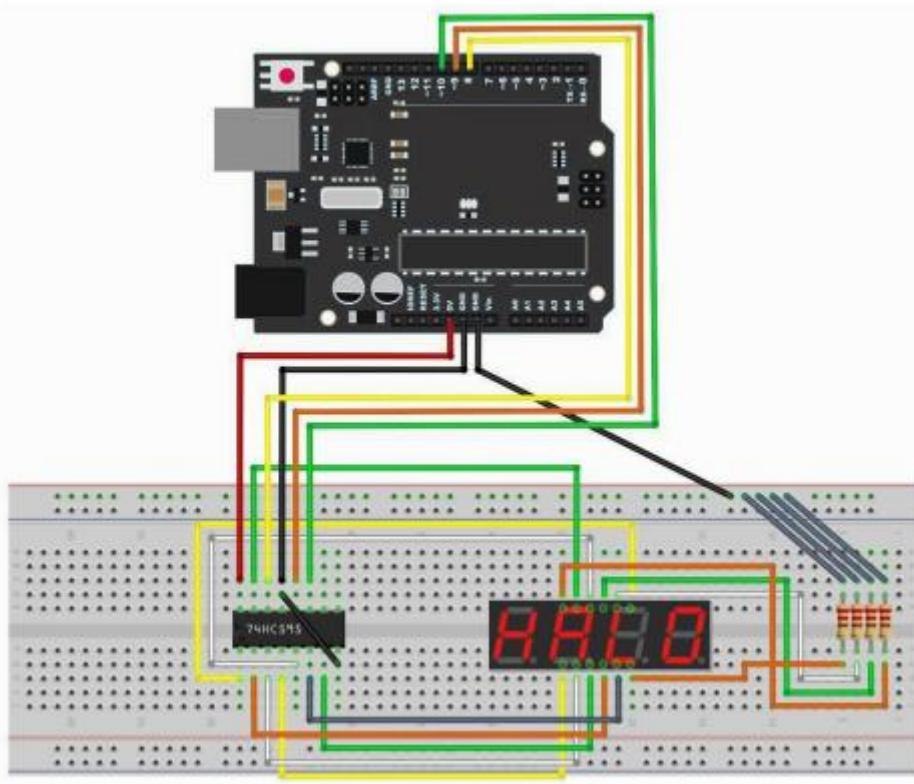

# LROBROUYA

---

## Example picture

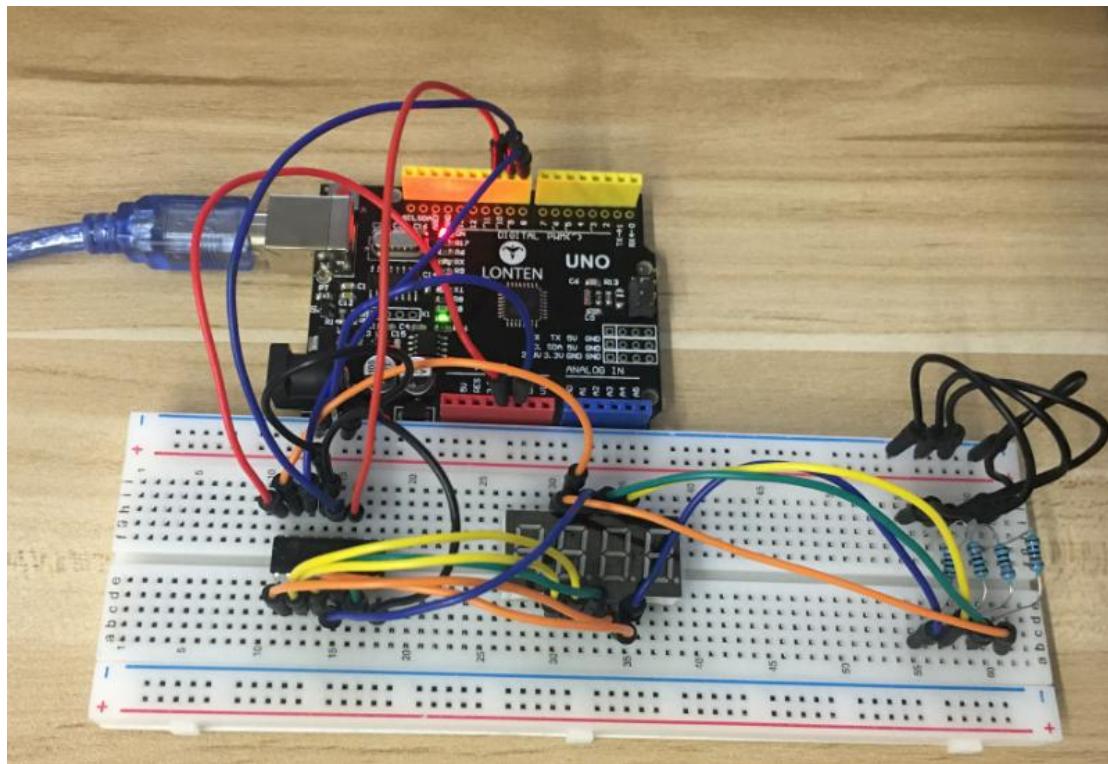

## Code

After wiring, please open the program in the code folder- Lesson 20 Four Digital Seven Segment Display and click UPLOAD to upload the program.

## Lesson 21 GY-521 Module

### Overview

In this lesson, we will learn how to use GY-521 module which is one of the best IMU (Inertia Measurement Unit) sensors, compatible with

# LROBRYA

---

Arduino. IMU sensors like the GY-521 are used in self balancing robots, UAVs, smart phones, etc.

## **Component Required:**

(1) x LONTEN Uno R3

(1) x GY-521 module

(4) x F-M wires

## **Component Introduction**

### **GY-521 SENSOR**

The InvenSense GY-521 sensor contains a MEMS accelerometer and a MEMS gyro in a single chip. It is very accurate, as it contains 16-bits analog to digital conversion hardware for each channel. Therefore it captures the x, y, and z channel at the same time. The sensor uses the I2C-bus to interface with the Arduino.

The GY-521 is not expensive, especially given the fact that it combines both an accelerometer and a gyro.





---

IMU sensors are one of the most inevitable type of sensors used today in all kinds of electronic gadgets. They are seen in smart phones, wearables, game controllers, etc.

IMU sensors help us in getting the attitude of an object, attached to the sensor in three dimensional space. These values usually in angles, thus help us to determine its attitude. Thus, they are used in smart phones to detect its orientation. And also in wearable gadgets like the nike fuel band or fit bit, which use IMU sensors to track movement.


### **How does it work?**

IMU sensors usually consists of two or more parts. Listing them by priority, they are : accelerometer, gyroscope, magnetometer and altimeter. The GY-521 is a 6 DOF (Degrees of Freedom) or a six axis IMU sensor, which means that it gives six values as output.

Three values from the accelerometer and three from the gyroscope. The GY-521 is a sensor based on MEMS (Micro Electro Mechanical Systems) technology. Both the accelerometer and the gyroscope is embedded inside a single chip. This chip uses I2C (Inter Integrated Circuit) protocol for communication

### **How does an accelerometer work?**

# LROBRYA

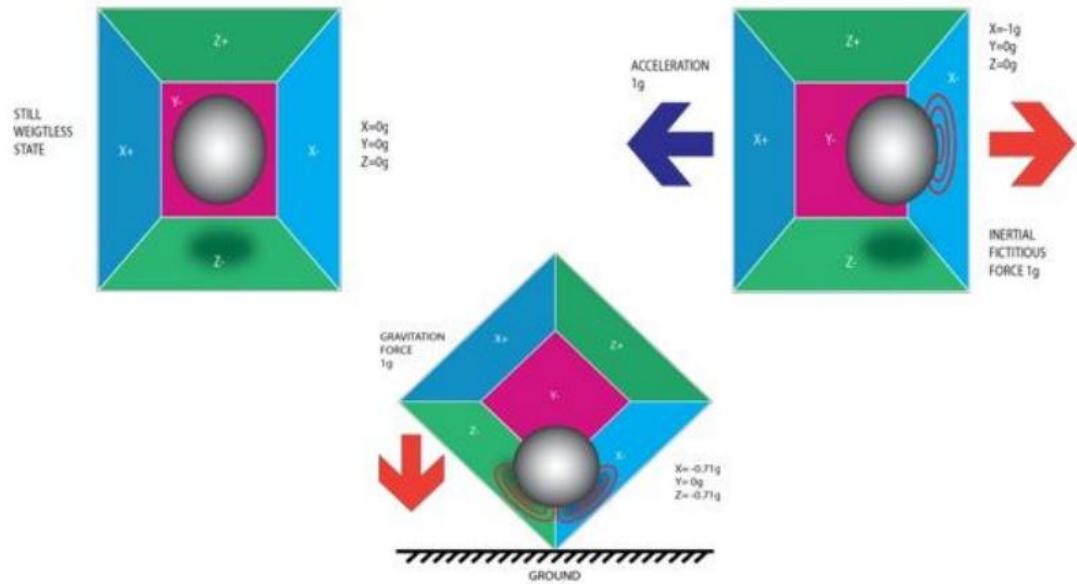


An accelerometer works on the principle of piezo electric effect. Here, imagine a cuboidal box, having a small ball inside it, like in the picture above. The walls of this box are made with piezo electric crystals. Whenever you tilt the box, the ball is forced to move in the direction of the inclination, due to gravity. The wall with which the ball collides, creates tiny piezo electric currents. There are totally, three pairs of opposite walls in a cuboid. Each pair corresponds to an axis in 3D space: X, Y and Z axes.


Depending on the current produced from the piezo electric walls, we can determine the direction of inclination and its magnitude. For more information check this.

# LROBRYA

---

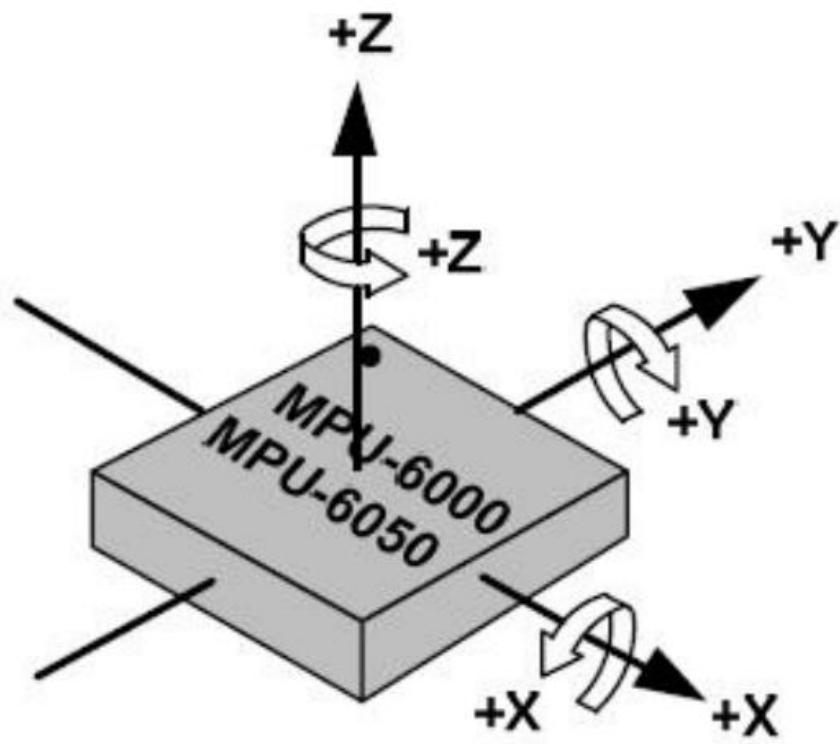

## How does a gyroscope work?

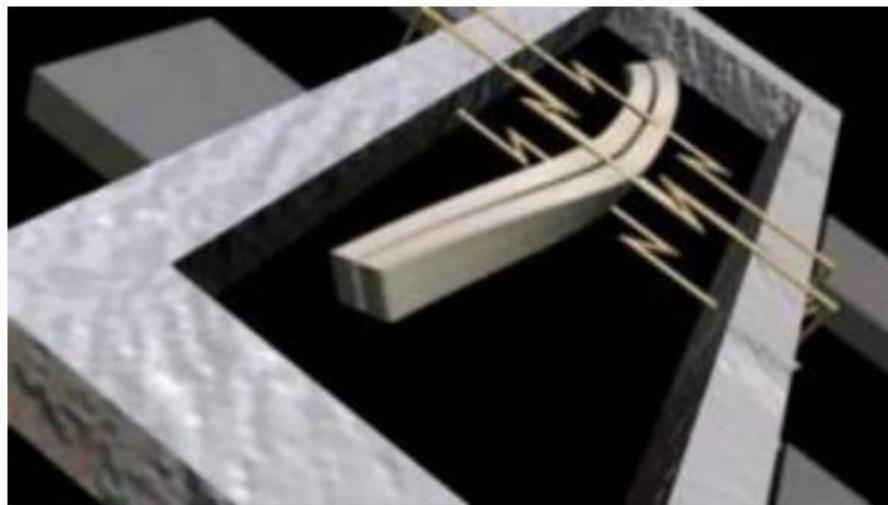


Gyrosopes work on the principle of Coriolis acceleration. Imagine that there is a fork like structure, which is in constant back and forth motion. It is held in place using piezo electric crystals. Whenever, you try to tilt

# LROBRYA


this arrangement, the crystals experience a force in the direction of inclination. This is caused as a result of the inertia of the moving fork. The crystals thus produce a current in consensus with the piezo electric effect, and this current is amplified. The values are then refined by the host microcontroller.

## Connection Schematic

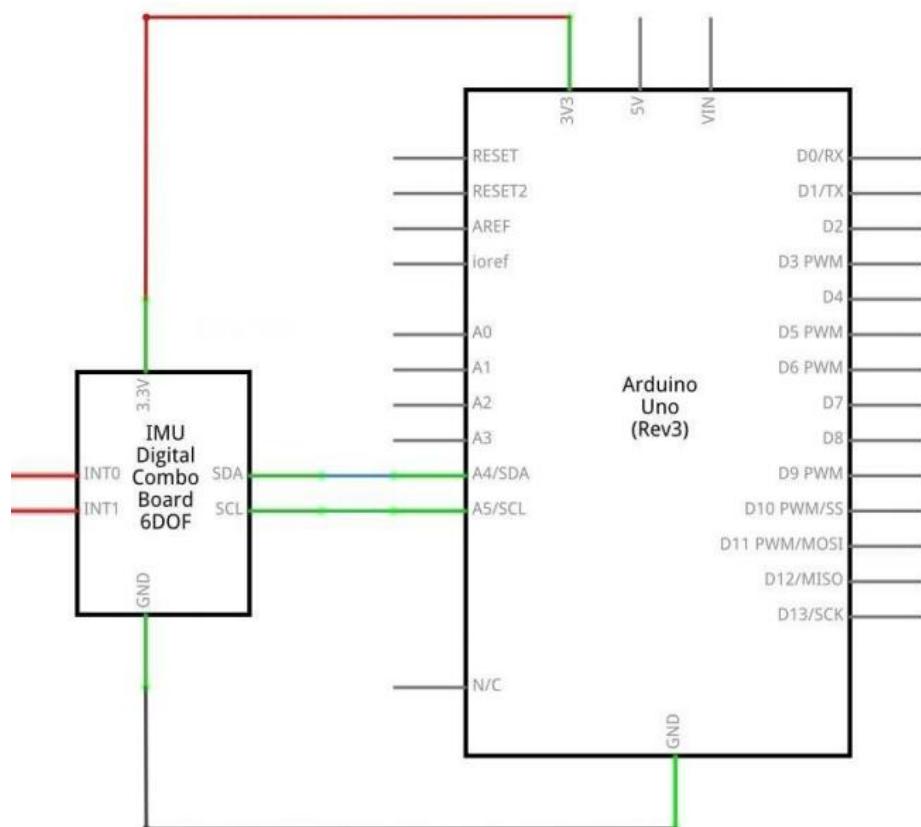

## Circuit Connection

# LROBRUYA

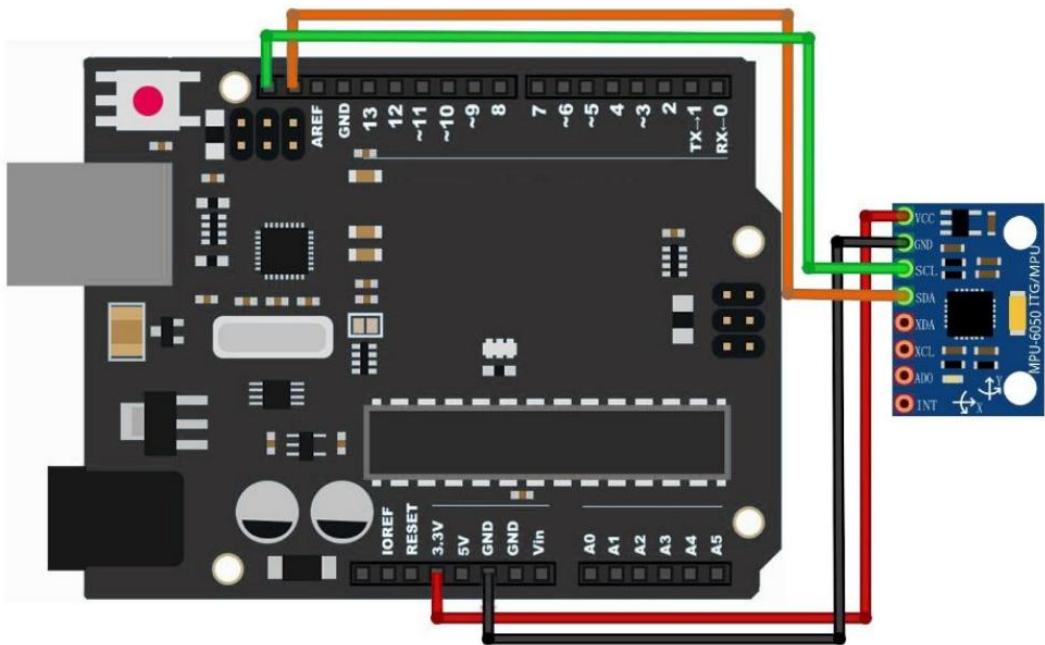

Next, we need to set up the I2C lines. For this connect the pin labelled as SDA on the GY-521 to the Arduino's analog pin 4 (SDA). And the pin labelled as SCL on the GY-521 to the Arduino's analog pin 5 (SCL). And that's it, you have finished wiring up the Arduino GY-521.


## Libraries needed

MPU-6050

## Example picture

# LROBRYA

---

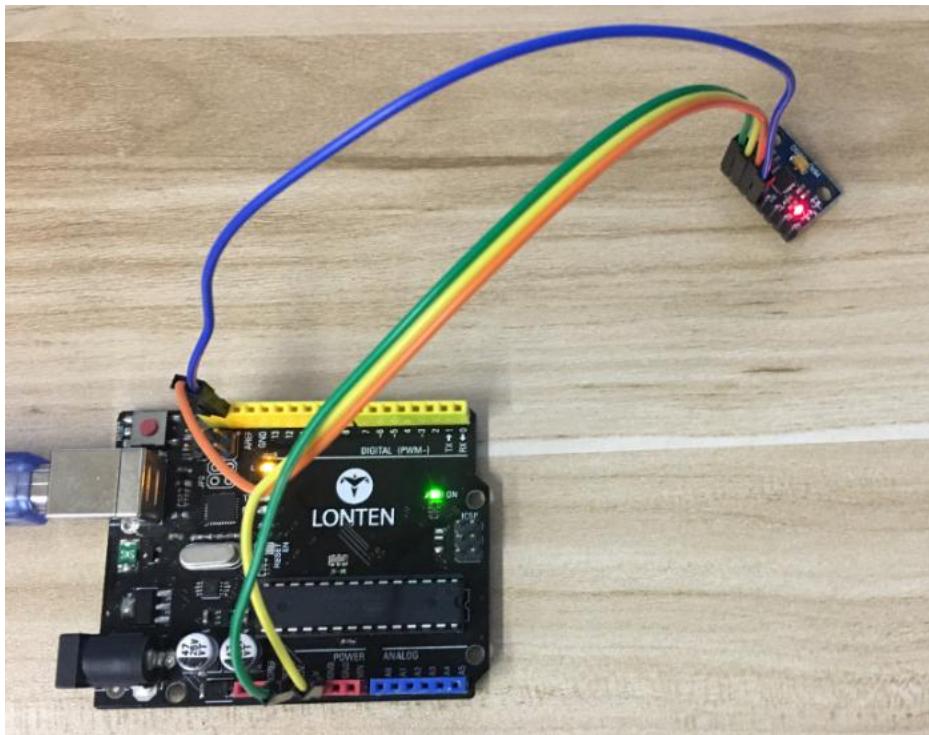

## Code

The short example sketch is a very short sketch and it shows all the raw values (accelerometer, gyro and temperature). It should work on Arduino Uno, Nano, Leonardo, and also Due.

[After wiring, please open the program in the code folder- Lesson 21 GY-521 Module and click UPLOAD to upload the program.](#)

[Before you can run this, make sure that you have installed the <GY-521> library or re-install it, if necessary. Otherwise, your code won't work.](#)



## Lesson 22 MAX7219 LED Dot Matrix Module

### Overview

In this lesson we will connect a MAX7219 and scroll the text across.


Since these modules use the MAX7219 LED driver chip, we will be able to turn on and off the 64 LEDs of each module, using only 3 pins on our UNO.

### Component Required:

- (1) x LONTEN Uno R3
- (1) x Max7219 module
- (5) x F-M wires (Female to Male DuPont wires)

### Component Introduction

#### MAX7219 LED Dot Matrix Module

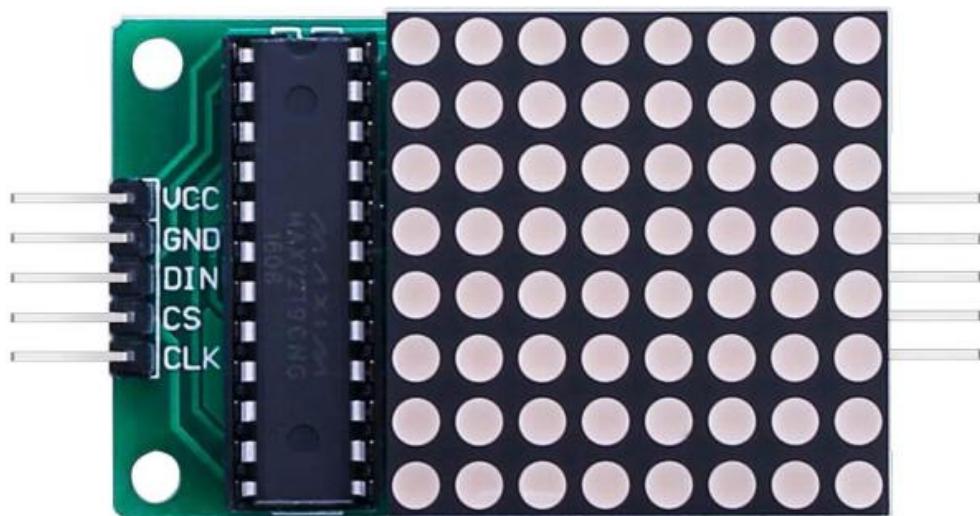



---

Our project is in fact an Arduino with Serially Interfaced MAX7219 Operates an 8X8 LED Matrix .The MAX7219 IC is a serial input/output common-cathode display driver that interfaces microprocessors to a 7-segment numeric LED displays of up to 8 digits, bar-graph displays, or 64 individual LEDs. For convenience, here an  $8 \times 8$  LED matrix,integrated with a MAX7219 IC setup, available as a pre-wired module is used.

Typical specification of this LED Matrix Module is shown below:

Operating Voltage: DC 4.7V – 5.3V

Typical Voltage: 5V


Operating Current: 320mA

Max Operating Current: 2A

## **Connection**


### **Schematic**

# LROBRUYA

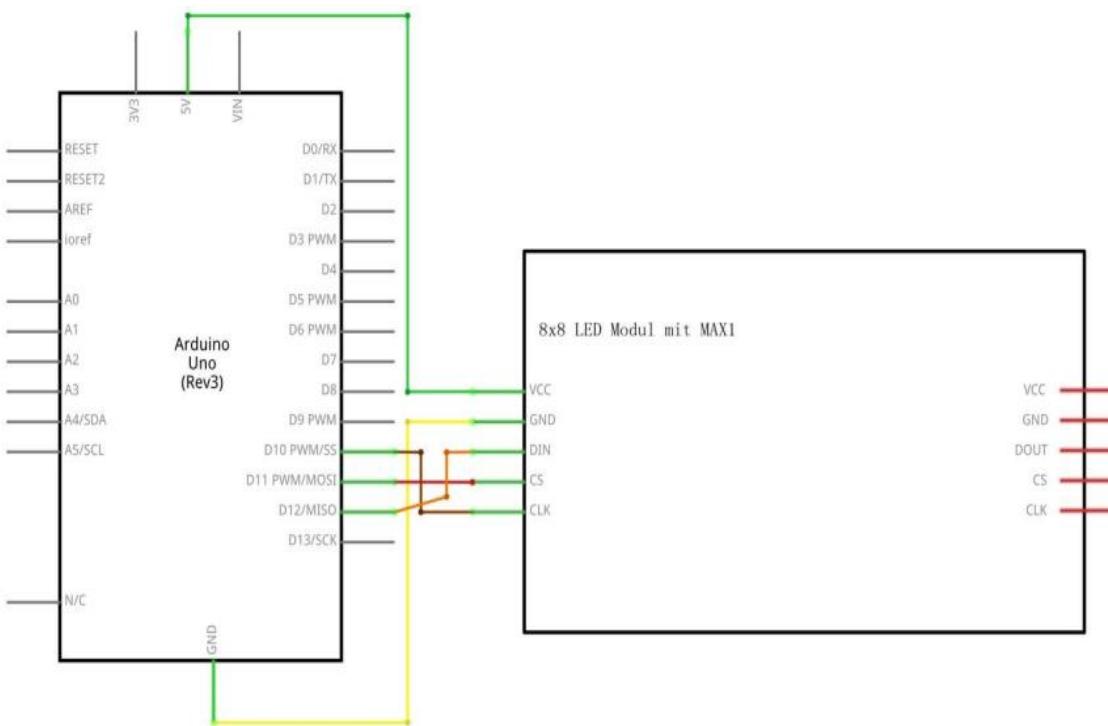

## Circuit Connection

# LROBRUYA

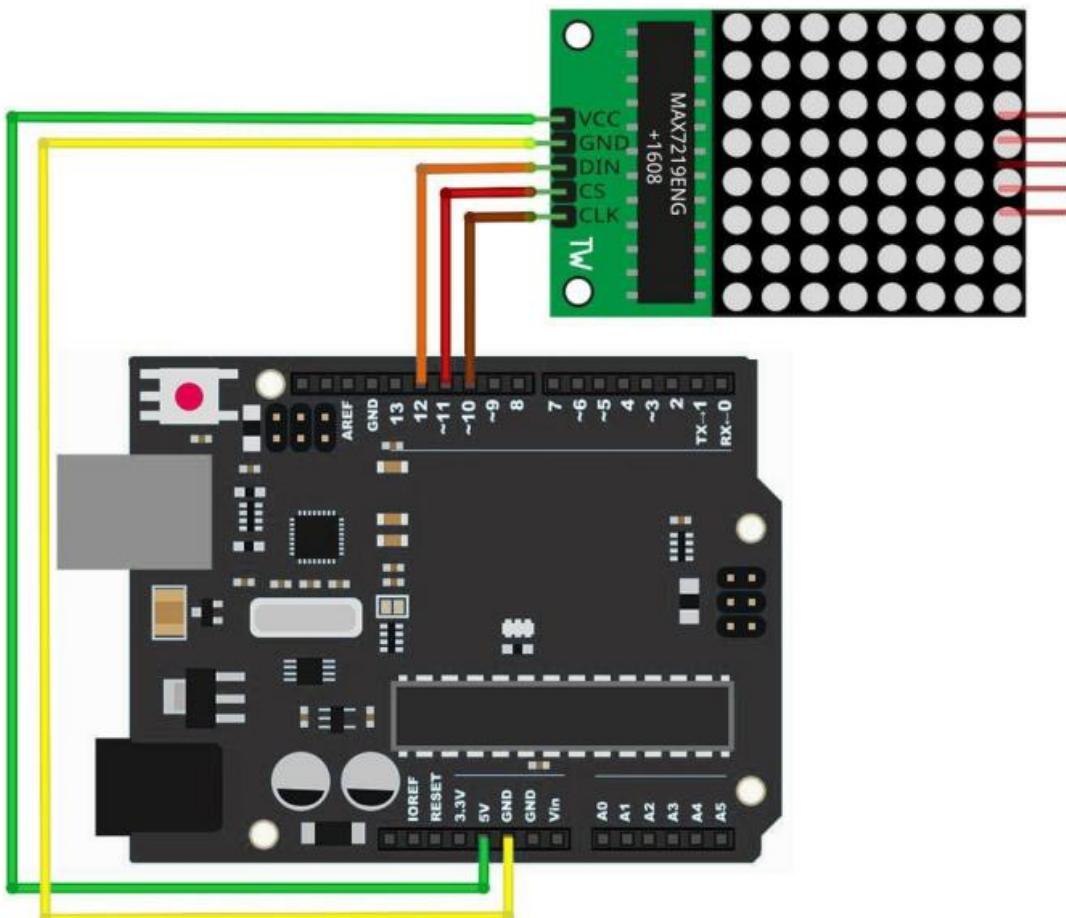


VCC and Ground are connected to the Arduino.

Pin 12 is connected to DIN, Pin 11 is connected to CS and Pin 10 is connected to CLK.

## Example picture

# LROBRYA

---

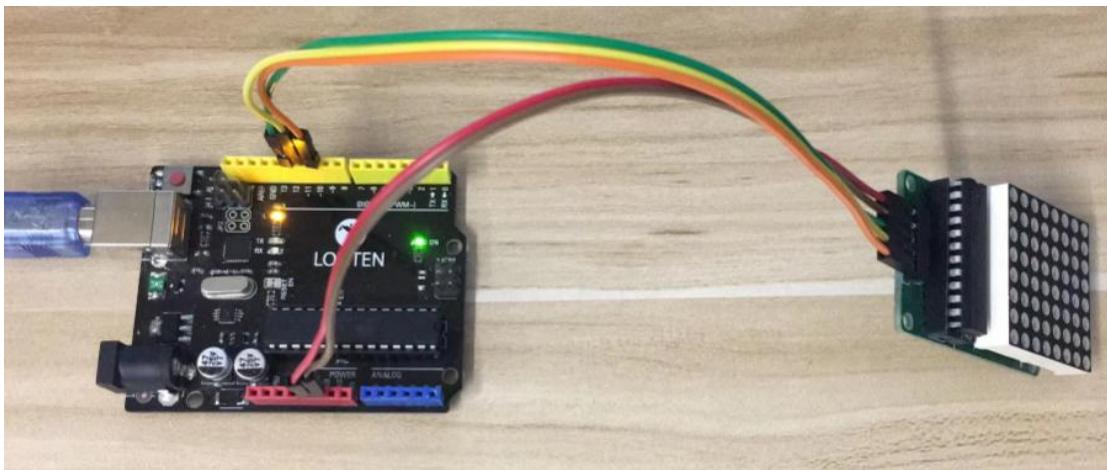

## Code

Our Sketch will make use of the “Maxmatrix” Library to communicate with the MAX7219 modules.

[After wiring, please open the program in the code folder- Lesson 22 MAX7219 LED Dot Matrix Module and click UPLOAD to upload the program.](#)

[Before you can run this, make sure that you have installed the <LedControl> library or re-install it, if necessary. Otherwise, your code won't work.](#)

## Lesson 23 RC522 RFID Module

### Overview

In this lesson, you will learn to how to apply the RC522 RFID Reader Module on UNO R3. This module uses the Serial Peripheral Interface

# LROBRYA

---

(SPI) bus to communicate with controllers such as Arduino, Raspberry Pi, beagle board, etc.

## **Component Required:**


(1) x LONTEN Uno R3

(1) x RC522 RFID module

(7) x F-M wires (Female to Male DuPont wires)

## **Component Introduction**

### **RC522**

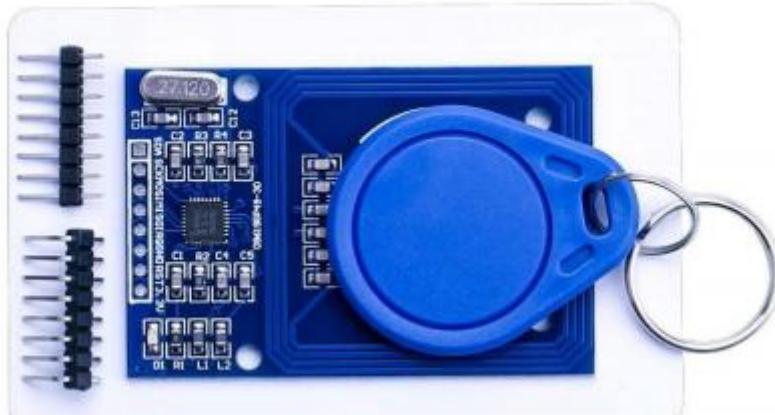

The MFRC522 is a highly integrated reader/writer for contactless communication at 13.56 MHz. The MFRC522 reader supports ISO 14443A / MIFARE® mode.

The MFRC522's internal transmitter part is able to drive a reader/writer antenna designed to communicate with ISO/IEC 14443A/MIFARE® cards and transponders without additional active circuitry. The receiver part provides a robust and efficient implementation of a demodulation



---

and decoding circuitry for signals from ISO/IEC 14443A/MIFARE® compatible cards and transponders. The digital part handles the complete ISO/IEC 14443A framing and error detection (Parity & CRC). The MFRC522 supports MIFARE®Classic (e.g. MIFARE® Standard) products. The MFRC522 supports contactless communication using MIFARE® higher transfer speeds up to 848 kbit/s in both directions.


Various host interfaces are implemented:

- SPI interface
- Serial UART (similar to RS232 with voltage levels according pad voltage supply)
- I2C interface.


The figure below shows a typical circuit diagram, using a complementary antenna connection to the MFRC522.

**Connection  
Schematic**

# LROBRYA

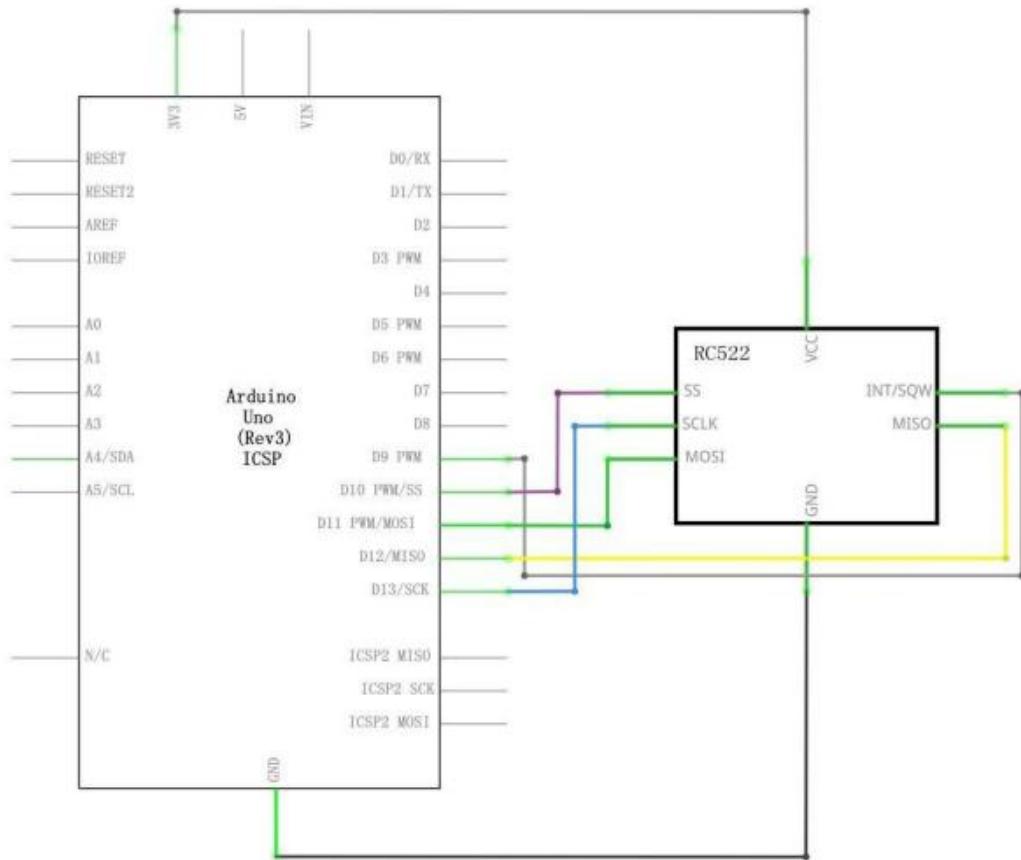


## Circuit Connection

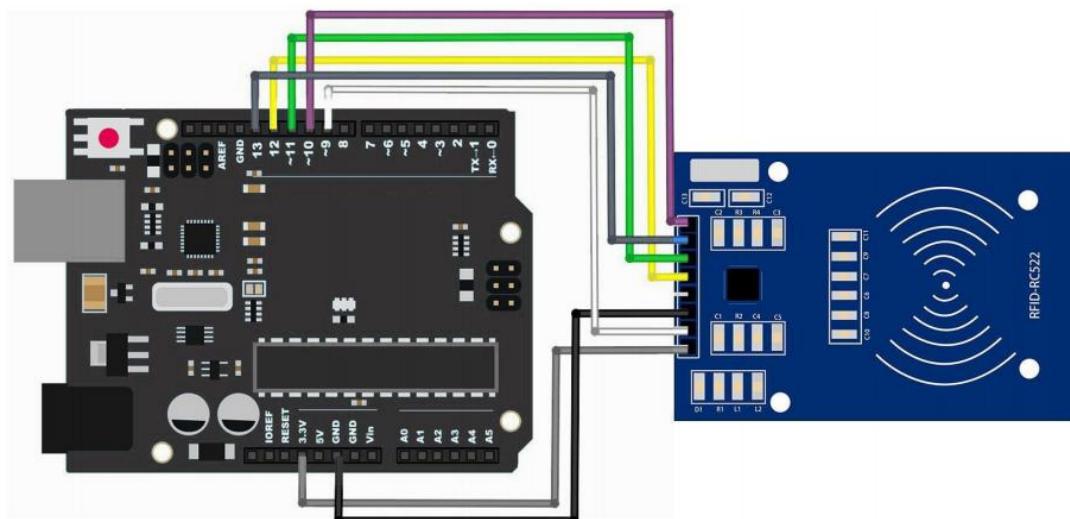

## Example picture

# LROBRUYA

---

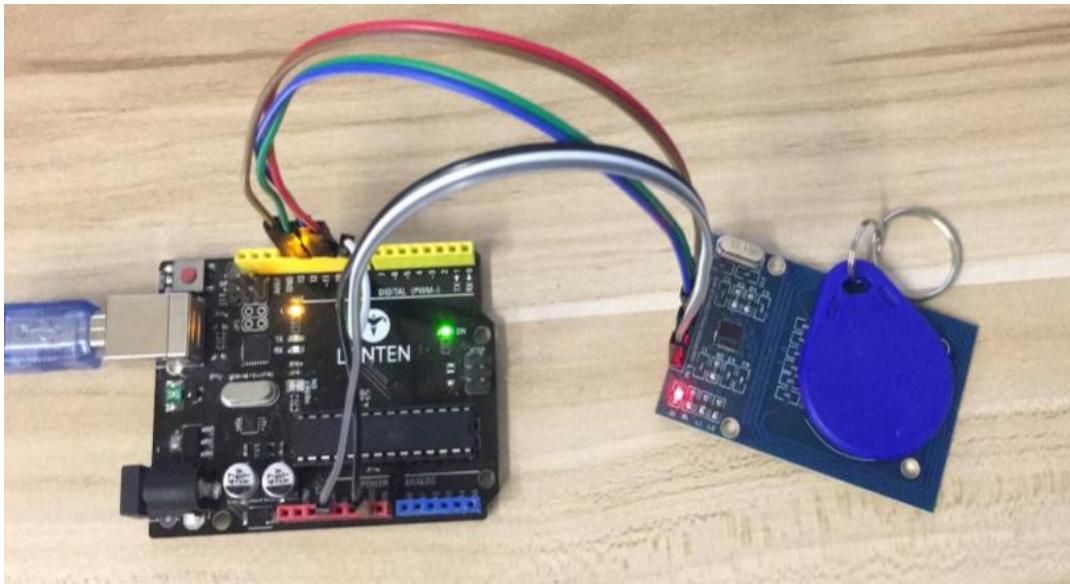

## Code

After wiring, please open the program in the code folder- Lesson 23

RC522 RFID Module and press UPLOAD to upload the program.

Before you can run this, make sure that you have installed the < rfid > library or re-install it, if necessary. Otherwise, your code won't work.

```
#define RST_PIN 9 // Configurable, see typical pin layout above
```

```
#define SS_PIN 10 // Configurable, see typical pin layout above
```

The locations of SPI pins vary with different chips, and you have to make a minor modification of the function.

Open the monitor then you can see the module can read the time as below:

Enter information here, ending with #

# LROBRUYA

The screenshot shows a terminal window titled "COM6 (Arduino Uno)". The text output is as follows:

```
LONTE#  
Write personal data on a MIFARE PICC  
Card UID: F3 1B 57 09 PICC type: MIFARE 1KB  
Type Family name, ending with #  
PCD_Authenticate() success:  
MIFARE_Write() success:  
MIFARE_Write() success:  
Type First name, ending with #
```

The input field contains "LONTE#". A red arrow points to the "#".

At the bottom of the window, there are several control buttons: "Autoscroll" (checked), "Newline", "9600 baud", and "Clear output".

# LROBRUYA

The screenshot shows a terminal window titled "COM6 (Arduino Uno)". The text output is as follows:

```
Read personal data on a MIFARE PICC:  
**Card Detected:**  
Card UID: F3 1B 57 09  
Card SAK: 08  
PICC type: MIFARE 1KB  
Name:  
LONTEN ←  
**End Reading**
```

At the bottom of the terminal window, there are several configuration buttons: "Autoscroll" (checked), "Newline", "9600 baud", and "Clear output". A red arrow points to the word "LONTEN" in the Name field.

## Lesson 24 Real Time Clock Module

### Overview

In this lesson, you will learn how to use the DS3231, clock module that displays the year, month, day, hour, minute, second and week. Support is via a backup battery trickle charger, which can be used unless being connected to UNO with only three data cables.

### Component Required:

- (1) x LONTEN Uno R3
- (1) x DS3231 RTC module

# LROBRYA


(4) x F-M wires (Female to Male DuPont wires)

## Component Introduction
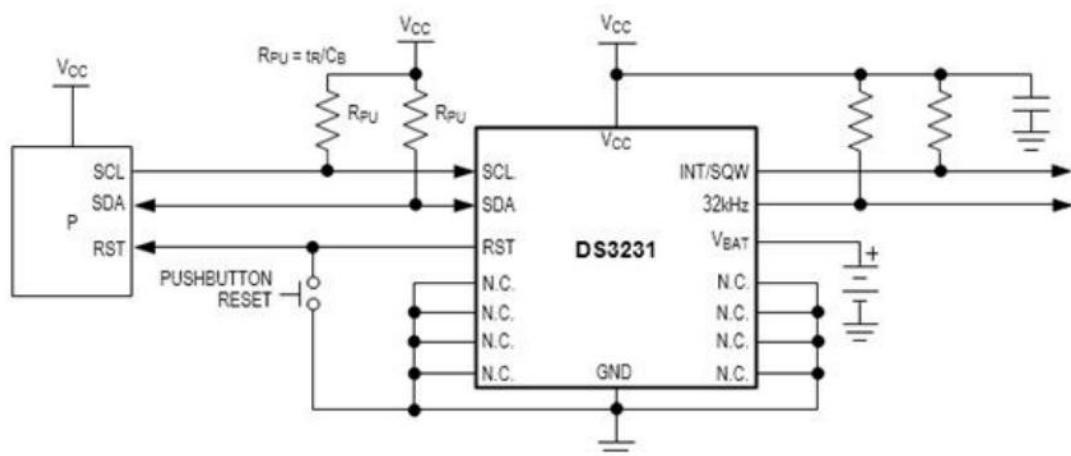
### DS3231




The DS3231 is a simple time-keeping chip. It has an integrated battery, so the clock can continue keeping time even when unplugged.




**Connection  
Schematic**

# LROBRUYA

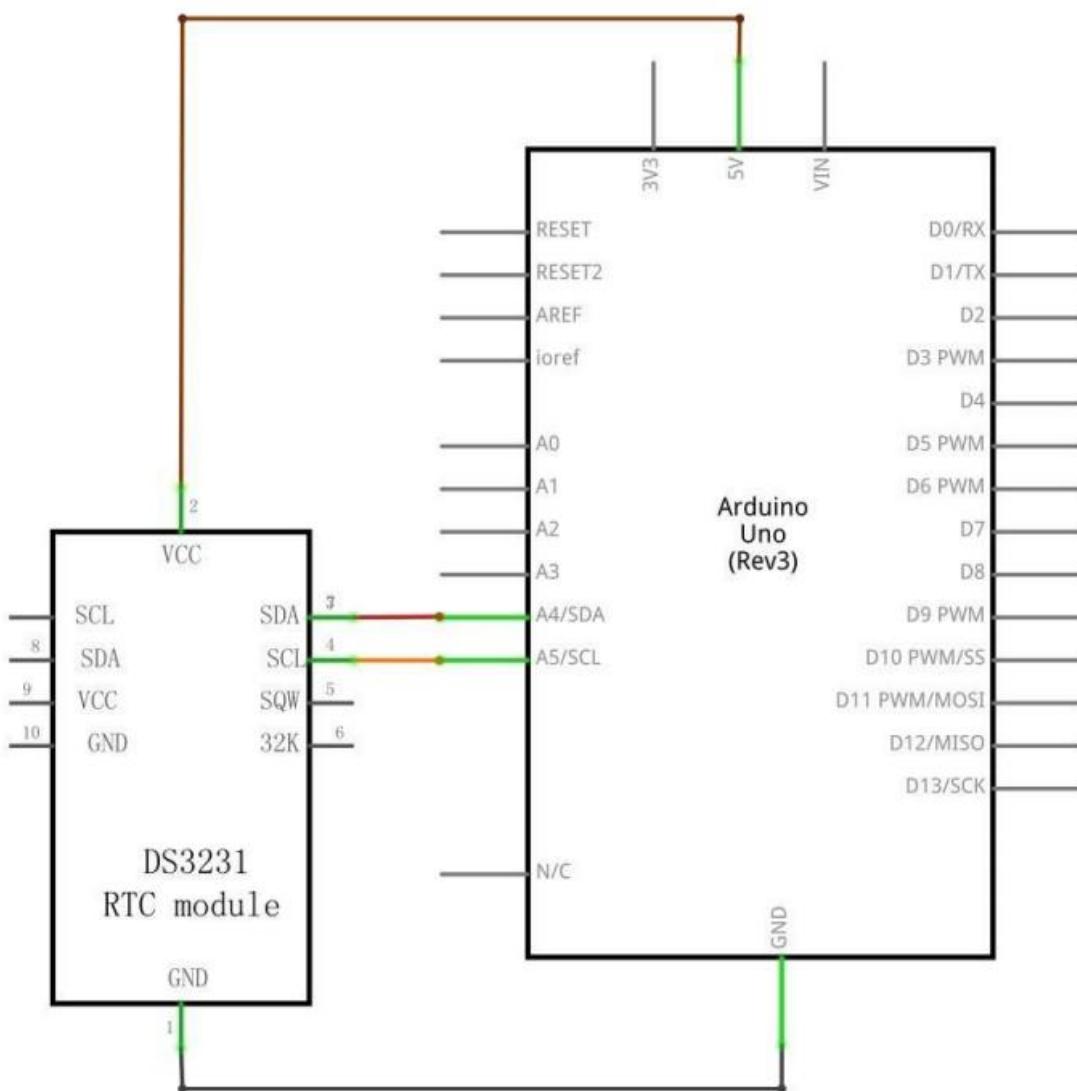

## Circuit Connection

# LROBRUYA

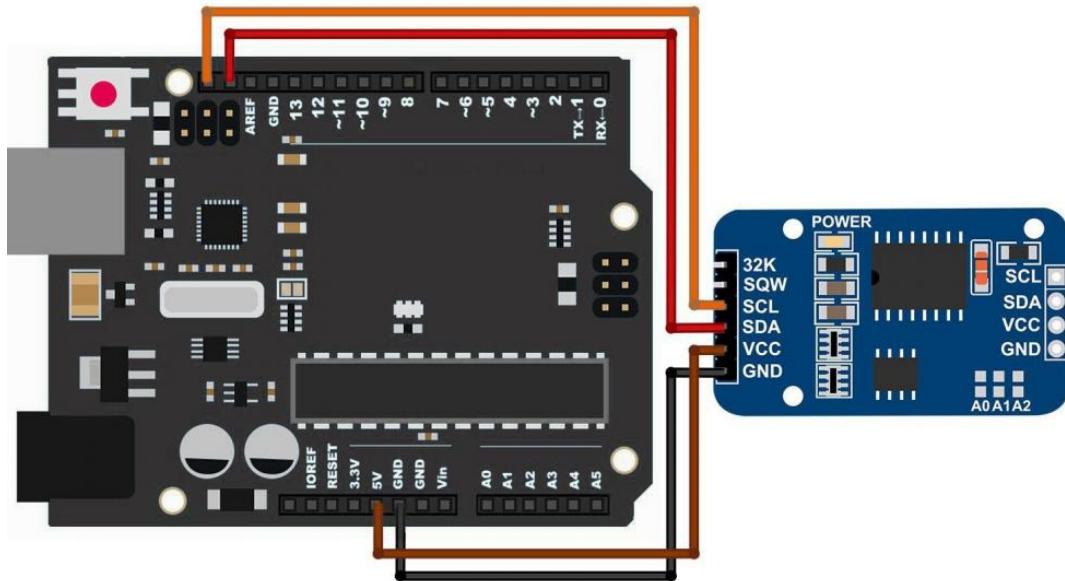


Set up according to the following image.

Ignore the 32K and SQW pins; you will not need them. Plug the SCL pin into your UNO R3 board SCL port, and the SDA pin into the SDA port.

The VCC pin plugs into the 5V port, and the GND plugs into the GND port.

## Example picture

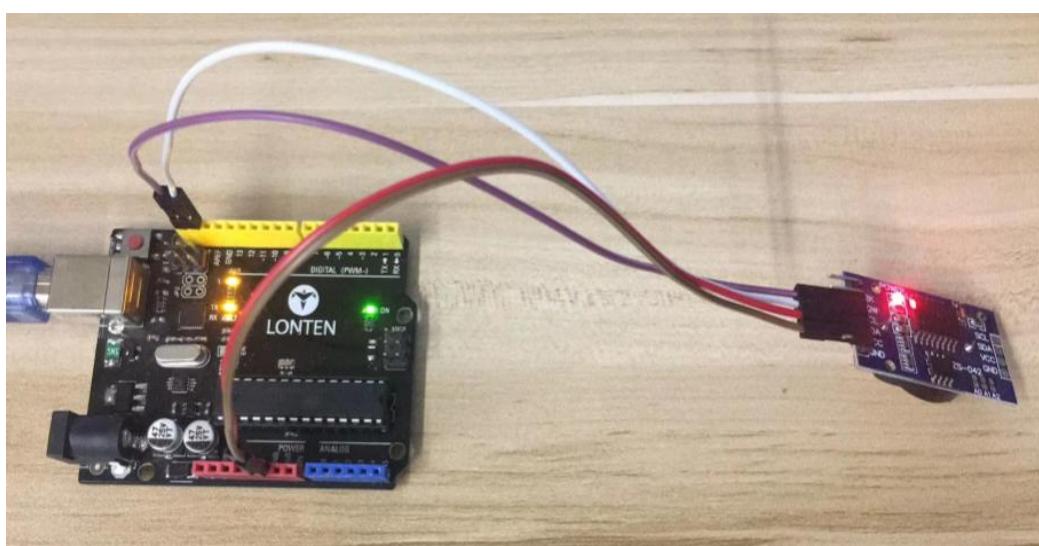



## Code

After wiring, please open program in the code folder- Lesson 24 Real Time Clock Module and click UPLOAD to upload the program.

Before you can run this, make sure that you have installed the <DS3231> library or re-install it, if necessary. Otherwise, your code won't work.

Open the monitor then you can see the module can read the time as below:

The screenshot shows the Arduino Serial Monitor window titled "COM6 (Arduino Uno)". The window displays the following text output from the DS3231 module:

```
Toda          1689695155
Today is:      18-7-2023 16:45:56
Unixtime:      1689695156
xtime:         1689695155
Today is:      18-7-2023 16:45:56
Unixtime:      1689695156
xtime:         1689695155
Today is:      18-7-2023 16:45:56
Unixtime:      1689695156
Initialize DS3231
Today is:      18-7-2023 16:45:29
Unixtime:      1689695129
Today is:      18-7-2023 16:45:30
Unixtime:      1689695130
```

At the bottom of the monitor window, there are three buttons: "Autoscroll" (checked), "Newline", and "9600 baud".



---

## Lesson 25 The Serial Monitor


### Overview

In this lesson, you will build on Lesson 16, adding the facility to control the LEDs from your computer using the Arduino Serial Monitor. The serial monitor is the 'tether' between the computer and your UNO. It lets you send and receive text messages, handy for debugging and also controlling the UNO from a keyboard! For example, you will be able to send commands from your computer to turn on LEDs. In this lesson, you will use exactly the same parts and a similar breadboard layout as Lesson 16. So, if you have not already done so, follow Lesson 16 now.

### Steps taken

After you have uploaded this sketch onto your UNO, click on the right-most button on the toolbar in the Arduino IDE. The button is circled below.

# LROBRUYA

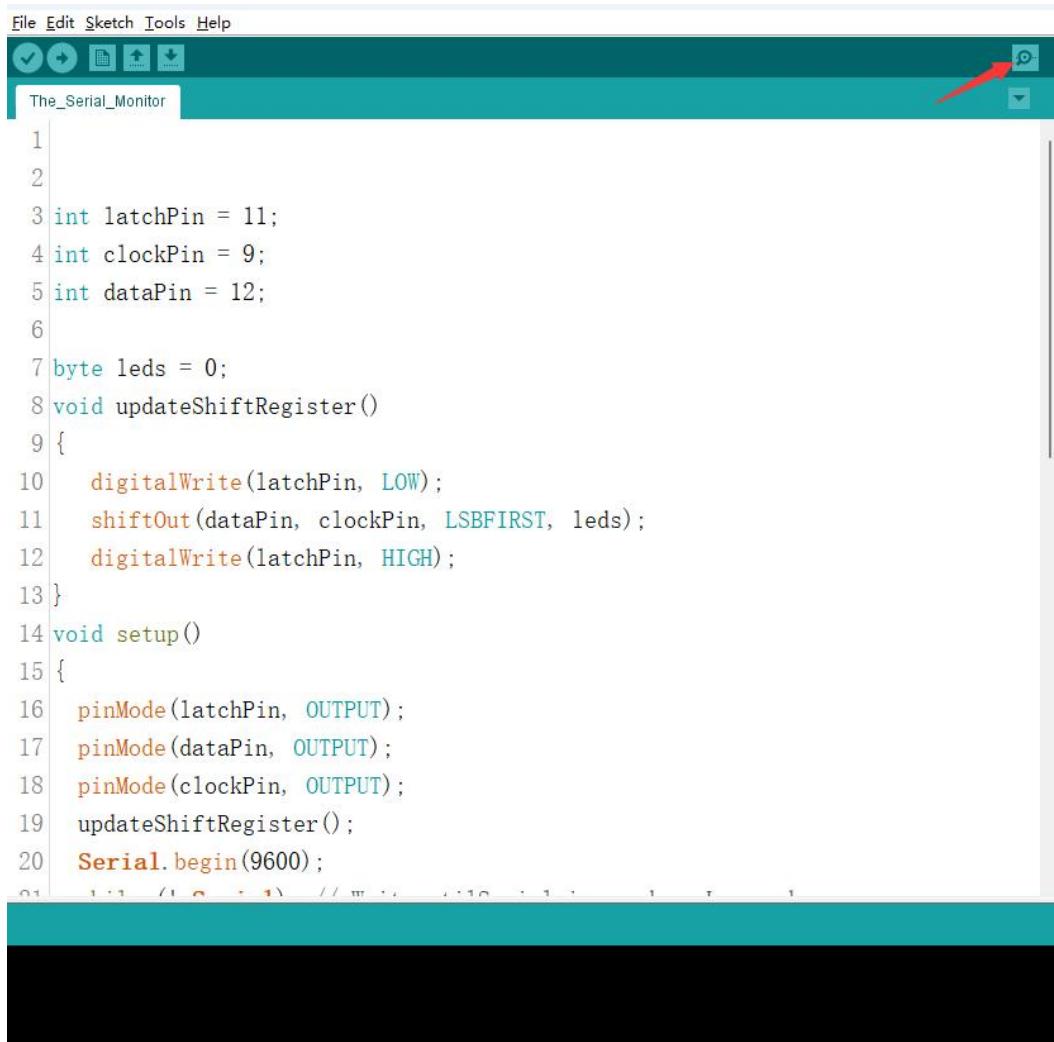


The screenshot shows the Arduino IDE interface. The top menu bar includes File, Edit, Sketch, Tools, and Help. Below the menu is a toolbar with various icons. The main area is titled "The\_Serial\_Monitor". A red arrow points to the "Serial Monitor" button (a magnifying glass icon) in the toolbar. The code in the editor is:

```
1
2
3 int latchPin = 11;
4 int clockPin = 9;
5 int dataPin = 12;
6
7 byte leds = 0;
8 void updateShiftRegister()
9 {
10    digitalWrite(latchPin, LOW);
11    shiftOut(dataPin, clockPin, LSBFIRST, leds);
12    digitalWrite(latchPin, HIGH);
13 }
14 void setup()
15 {
16    pinMode(latchPin, OUTPUT);
17    pinMode(dataPin, OUTPUT);
18    pinMode(clockPin, OUTPUT);
19    updateShiftRegister();
20    Serial.begin(9600);
```

The following window will open.

Click the Serial Monitor button to turn on the serial monitor.

# LROBRYA

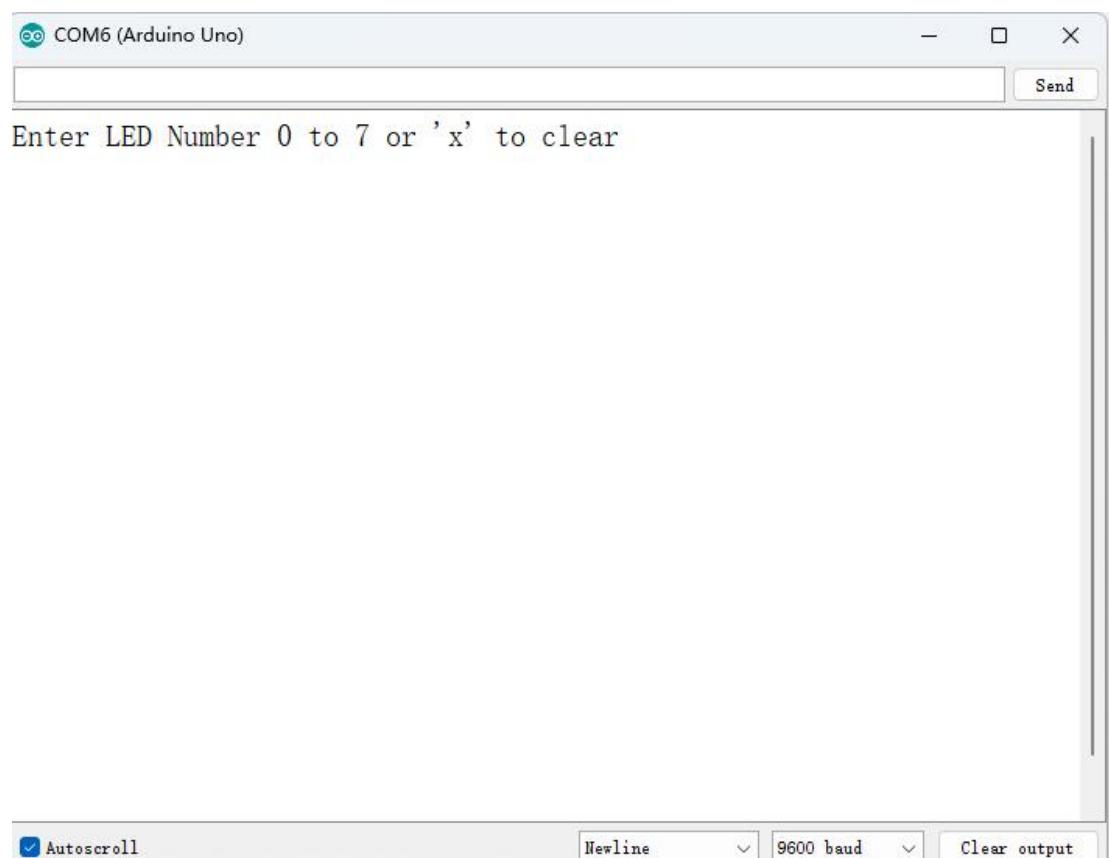


This window is called the Serial Monitor and it is part of the Arduino IDE software. Its job is to allow you to both send messages from your computer to an UNO board (over USB) and also to receive messages from the UNO. The message “Enter LED Number 0 to 7 or 'x' to clear” has been sent by the Arduino. It is telling us what commands we can send to the Arduino: either send the 'x' (to turn all the LEDs off) or the number of the LED you want to turn on (where 0 is the bottom LED, 1 is the next one up, all the way to 7 for the top LED).

Try typing the following commands into the top area of the Serial Monitor that is level with the 'Send' button. Press 'Send', after typing each
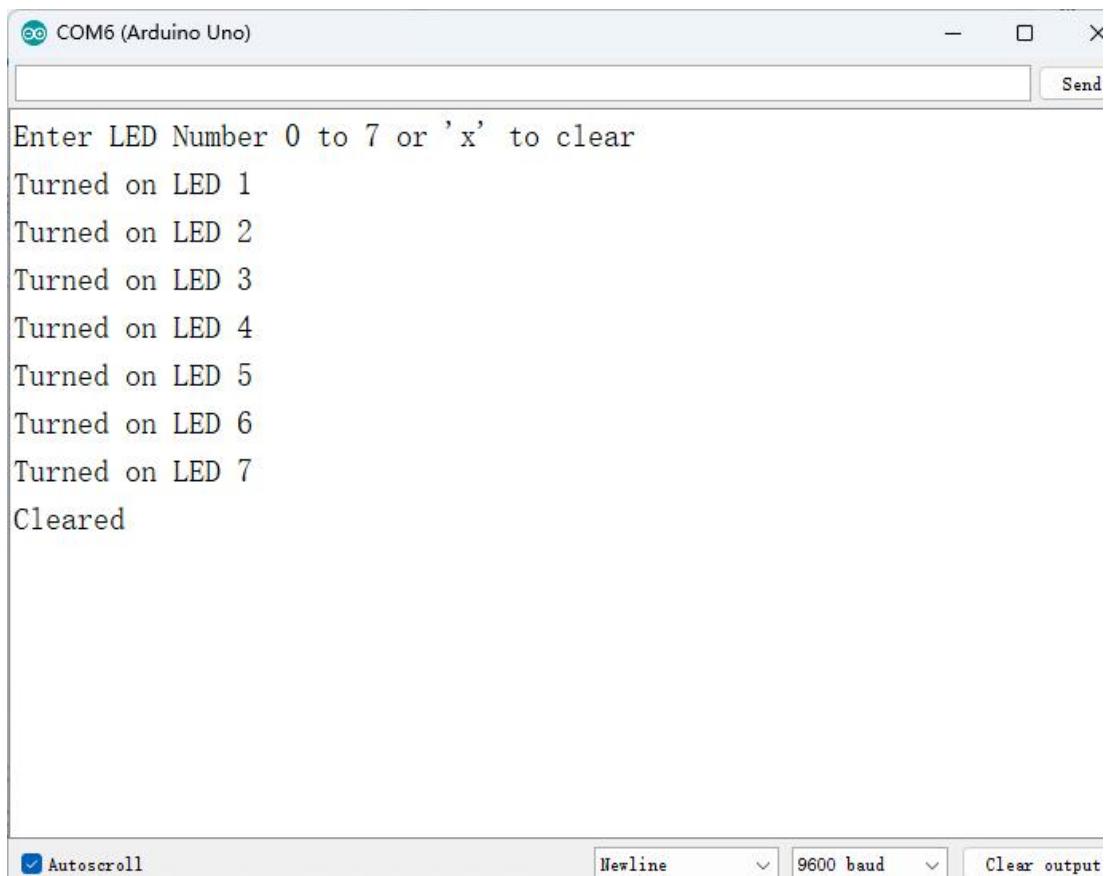
# LROBRUYA

---

of these characters: x 0 3 5 Typing x will have no effect if the LEDs are already all off, but as you enter each number, the corresponding LED should light and you will get a confirmation message from the UNO board. The Serial Monitor will appear as shown below.



The screenshot shows the Arduino Serial Monitor window titled "COM6 (Arduino Uno)". The window has a "Send" button in the top right corner. The text area displays the following messages:  
Enter LED Number 0 to 7 or 'x' to clear  
Turned on LED 1  
Turned on LED 2  
Turned on LED 3  
Turned on LED 4  
Turned on LED 5  
Turned on LED 6  
Turned on LED 7  
Cleared

At the bottom of the window, there are buttons for "Autoscroll", "Newline", "9600 baud", and "Clear output".

Type x again and press ‘Send’ to turn off all LEDs.

## Code

After wiring, please open program in the code folder- Lesson 25 The Serial Monitor and click UPLOAD to upload the program.



---

As you might expect, the sketch is based on the sketch used in Lesson 18. So, we will just cover the new bits here. You will find it useful to refer to the full sketch in your Arduino IDE.

In the 'setup' function, there are three new lines at the end:

```
void setup()
{
    pinMode(latchPin, OUTPUT);
    pinMode(dataPin, OUTPUT);
    pinMode(clockPin, OUTPUT);
    updateShiftRegister();
    Serial.begin(9600);
    while (! Serial); // Wait until Serial is ready - Leonardo
    Serial.println("Enter LED Number 0 to 7 or 'x' to clear");
}
```

Firstly, we have the command 'Serial.begin(9600)'. This starts serial communication, so that the UNO can send out commands through the USB connection. The value 9600 is called the 'baud rate' of the connection. This is how fast the data is to be sent.

You can change this to a higher value, but you will also have to change the Arduino Serial monitor to the same value. We will discuss this later;



---

for now, leave it at 9600. The line beginning with 'while' ensures that there is something at the other end of the USB connection for the Arduino to talk to before it starts sending messages. Otherwise, the message might be sent, but not displayed. This line is actually only necessary if you are using an Arduino Leonardo because the Arduino UNO automatically resets the Arduino board when you open the Serial Monitor, whereas this does not happen with the Leonardo.

The last of the new lines in 'setup' sends out the message that we see at the top of the Serial Monitor.

The 'loop' function is where all the action happens:

```
void loop()
{
if (Serial.available())
{
char ch = Serial.read(); if
(ch >= '0' && ch <= '7')
{
int led = ch - '0';
bitSet(leds, led);
updateShiftRegister();
```



```
Serial.print("Turned on LED ");

Serial.println(led);

}

if (ch == 'x')

{

leds = 0;

updateShiftRegister();

Serial.println("Cleared");

}

}

}
```

Everything that happens inside the loop is contained within an 'if' statement. So unless the call to the built-in Arduino function 'Serial.available()' is 'true' then nothing else will happen.

Serial.available() will return 'true' if data has been send to the UNO and is there ready to be processed. Incoming messages are held in what is called a buffer and Serial.available() returns true if that buffer is Not empty.

If a message has been received, then it is on to the next line of code:

```
char ch = Serial.read();
```



---

This reads the next character from the buffer, and removes it from the buffer. It also assigns it to the variable 'ch'. The variable 'ch' is of type 'char' which stands for 'character' and as the name suggests, holds a single character.

If you have followed the instructions in the prompt at the top of the Serial Monitor, then this character will either be a single digit number between 0 and 7 or the letter 'x'.

The 'if' statement on the next line checks to see if it is a single digit by seeing if 'ch' is greater than or equal to the character '0' and less than or equal to the character '7'. It looks a little strange comparing characters in this way, but is perfectly acceptable.

Each character is represented by a unique number, called its ASCII value. This means that when we compare characters using `<=` and `>=` it is actually the ASCII values that were being compared.

If the test passes, then we come to the next line:

```
int led = ch - '0';
```

Now we are performing arithmetic on characters! We are subtracting the digit '0' from whatever digit was entered. So, if you typed '0' then '0' – '0' will equal 0. If you typed '7' then '7' – '0' will equal the number 7 because it is actually the ASCII values that are being used in the subtraction.



Since that we know the number of the LED that we want to turn on, we just need to set that bit in the variable 'leds' and update the shift register.

```
bitSet(leds, led);  
updateShiftRegister();
```

The next two lines write back a confirmation message to the Serial Monitor.

```
Serial.print("Turned on LED ");  
Serial.println(led);
```

The first line uses `Serial.print` rather than `Serial.println`. The difference between the two is that `Serial.print` does not start a new line after printing whatever is in its parameter.

We use this in the first line, because we are printing the message in two parts. Firstly the general bit: 'Turned on LED ' and then the number of the LED. The number of the LED is held in an 'int' variable rather than being a text string. `Serial.print` can take either a text string enclosed in double-quotes, or an 'int' or for that matter pretty much any type of variable.

After the 'if' statement that handles the case, when a single digit has been handled, there is a second 'if' statement that checks to see if 'ch' is the letter 'x'.



```
if (ch == 'x')  
{  
    leds = 0;  
    updateShiftRegister();  
    Serial.println("Cleared");  
}
```

If it is, then it clears all the LEDs and sends a confirmation message.


## Lesson 26 LCD1602 I2C Module

### Overview

In this lesson, you will learn how to wire up and use an alphanumeric LCD display.

The display has an LED backlight and can display two rows with up to 16 characters on each row. You can see the rectangles for each character on the display and the pixels that make up each character. The display is just white on blue and is intended for showing text.

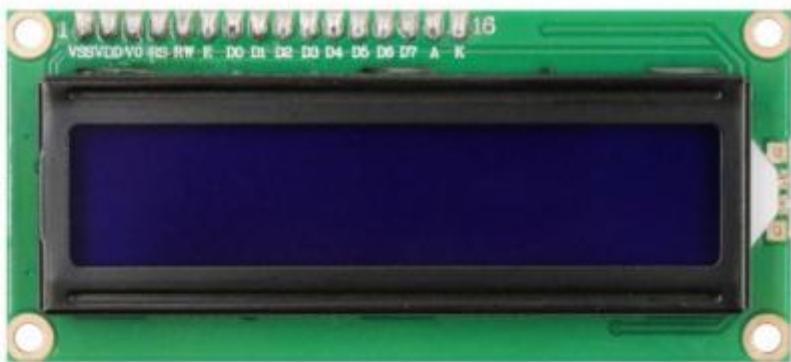In this lesson, we will run the Arduino example program for the LCD I2C library, but in the next lesson, we will get our display to show the temperature, using sensors.



## **Component Required:**


- (1) x LONTEN Uno R3
- (1) x LCD1602 I2C module
- (1) x Potentiometer (10k)
- (1) x 830 tie-points Breadboard
- (16) x M-M wires (Male to Male jumper wires)

## **Component Introduction:**

This is great LCD display compatible with arduino. With limited pin resources, your project will quickly run out of resources using normal LCDs. With this I2C interface LCD module, you only need 2 lines (I2C) to display the information. If you already have I2C devices in your project, this LCD module actually cost no more resources at all. The address can be set 0x27.


## **Connection Schematic**

# LROBRUYA

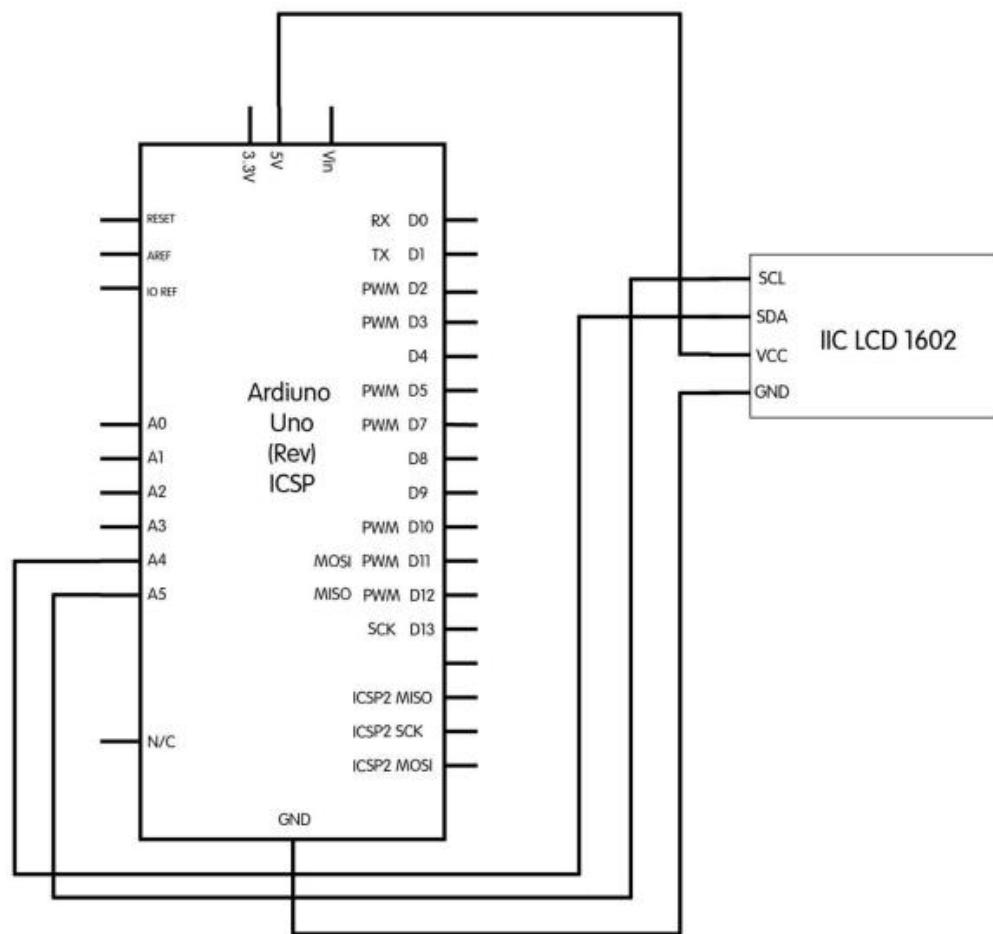

## Circuit Connection


# LROBRYA

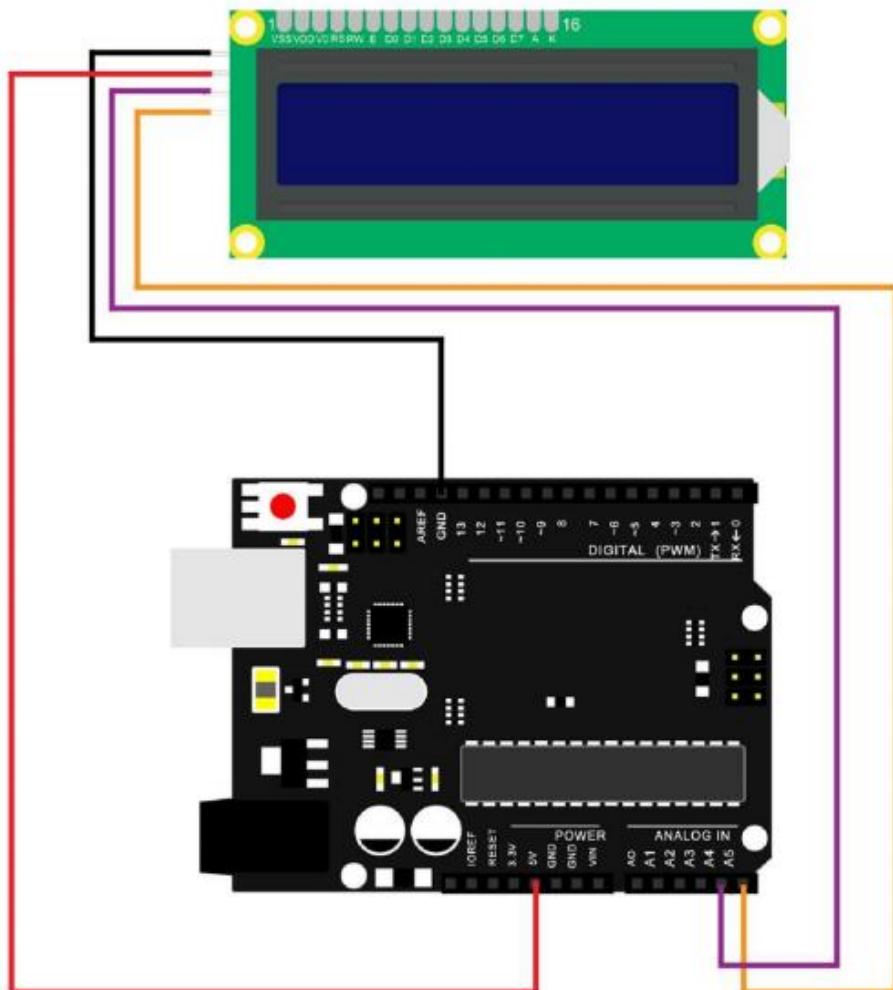

Example picture

# LROBRYA

---

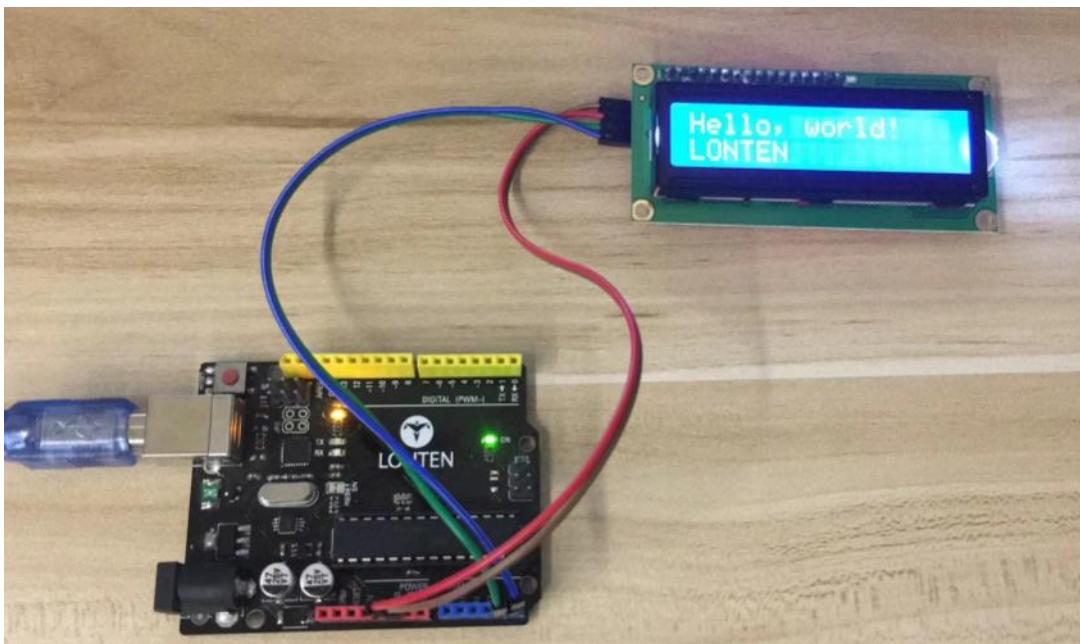

## Code

After wiring, please open the program in the code folder- Lesson 26 LCD Display and click UPLOAD to upload the program.

Before you can run this, make sure that you have installed the <LiquidCrystal\_I2C> library or re-install it, if necessary. Otherwise, your code won't work.

Upload the code to your Arduino board and you should see the message “Hello, world! LONTEN” displayed.

The first thing of note in the sketch is the line:

```
#include <LiquidCrystal_I2C.h>
```

This tells Arduino that we wish to use the LiquidCrystal\_I2C library.

Next set the LCD address to 0x27 for a 16 chars and 2 line display



LiquidCrystal\_I2C lcd(0x27,16,2);

After uploading this code, make sure the backlight is lit up, and adjust the potentiometer all the way around until you see the text message.

In the 'setup' function, we have four commands:

```
lcd.setCursor(0,0);
lcd.print("Hello, world!");
lcd.setCursor(0,1);
lcd.print("LONTEN");
```

The `lcd.setCursor(0,0)` tells the Begin displaying the next line of code in the first row and first column.

The `lcd.setCursor(0,1)` tells the Begin displaying the next line of code in the second row and first column.

```
lcd.print("Hello, world!");
lcd.print("LONTEN");
```

Tell screen display

“ Hello, world! LONTEN”

## Lesson 27 Thermometer

### Overview

In this lesson, you will use an LCD display to show the temperature.



## **Component Required:**

- (1) x LONTEN Uno R3
- (1) x LCD1602 I2C Module
- (1) x 10k ohm resistor
- (1) x Thermistor
- (1) x Potentiometer
- (1) x 830 tie-points Breadboard
- (18) x M-M wires (Male to Male jumper wires)

## **Component Introduction**

### **Thermistor**

A thermistor is a thermal resistor - a resistor that changes its resistance with temperature. Technically, all resistors are thermistors - their resistance changes slightly with temperature - but the change is usually very small and difficult to measure. Thermistors are made so that the resistance changes drastically with temperature so that it can be 100 ohms or more of change per degree!


There are two kinds of thermistors, NTC (negative temperature coefficient) and PTC (positive temperature coefficient). In general, you will see NTC sensors used for temperature measurement. PTC's are often used as resettable fuses - an increase in temperature increases the

# LROBRYA

resistance which means that as more current passes thru them, they heat up and 'choke back' the current, quite handy for protecting circuits!


## Connection

### Schematic

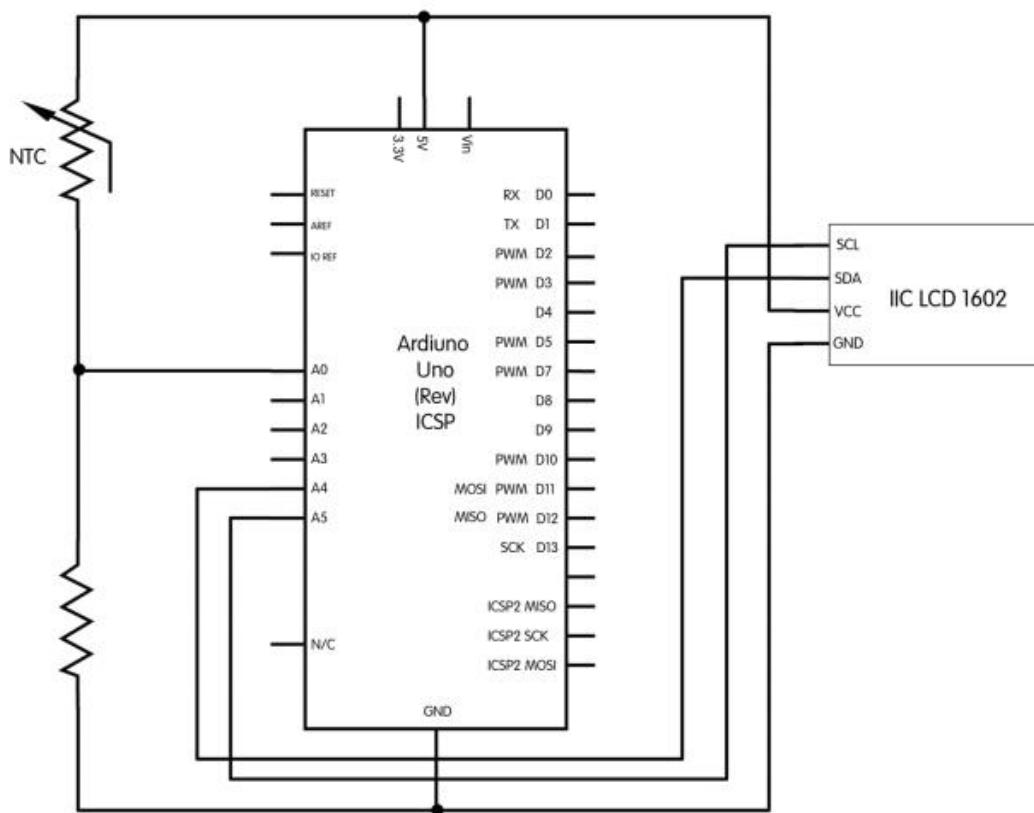

## Circuit Connection

# LROBRYA

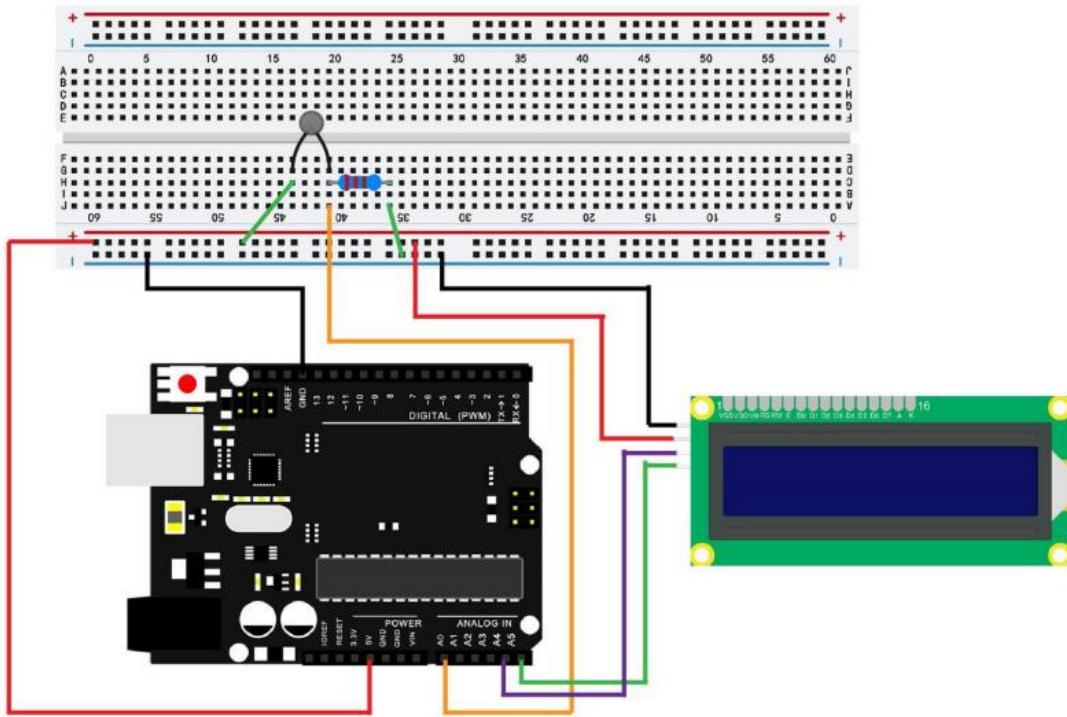

The breadboard layout is based on the layout from Lesson 25, so it will simplify things if you still have this on the breadboard.


There are a few jumper wires near the pot that have been moved slightly on this layout.

The 10 kΩ resistor and thermistor are all new additions to the board.

## Example picture

# LROBRYA

---

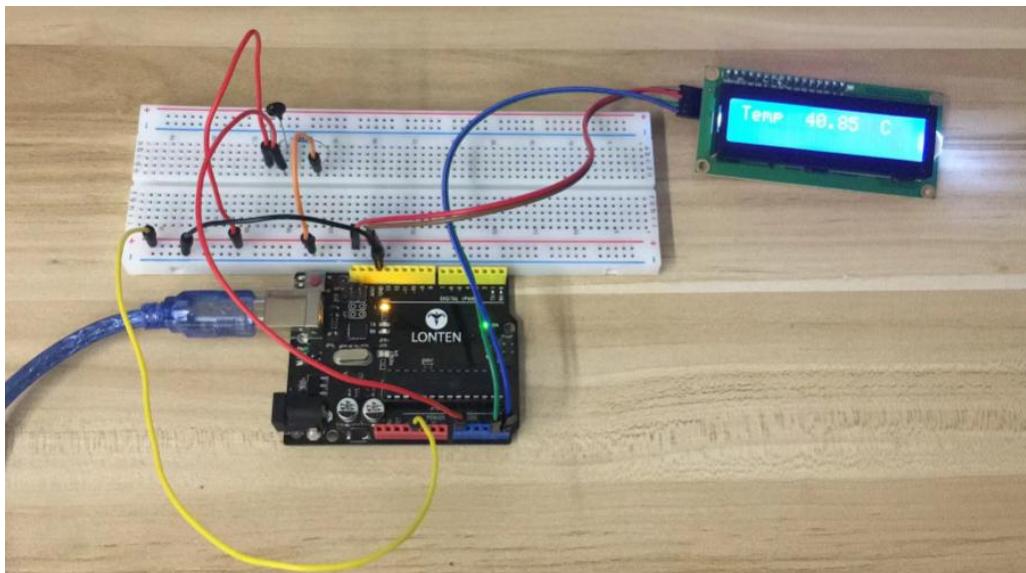

## Code

After wiring, please open the program in the code folder- Lesson 27 Thermometer and click UPLOAD to upload the program.

Before you can run this, make sure that you have installed the <LiquidCrystal\_I2C> library or re-install it, if necessary. Otherwise, your code won't work.

The sketch for this is based on that of lesson 25. Load it up onto your Arduino and you should find that warming the temperature sensor by putting your finger on it will increase the temperature reading.

`LiquidCrystal_I2C lcd(0x27,16,2);`

set the LCD address to 0x27 for a 16 chars and 2 line display

This makes things easier if you decide to change which pins you use.



---

In the 'loop' function there are now two interesting things going on.

Firstly we have to convert the analog from the temperature sensor into an actual temperature, and secondly we have to work out how to display them.

First of all, let's look at calculating the temperature.

```
int tempReading = analogRead(tempPin);

double tempK = log(10000.0 * ((1024.0 / tempReading - 1)));

tempK = 1 / (0.001129148 + (0.000234125 + (0.0000000876741 * tempK

*

tempK )) * tempK );

float tempC = tempK - 273.15;

float tempF = (tempC * 9.0)/ 5.0 + 32.0;
```

Displaying changing readings on an LCD display can be tricky. The main problem is that the reading may not always be the same number of digits.

So, if the temperature changed from 101.50 to 99.00 then the extra digit from the old reading is in danger of being left on the display.

To avoid this, write the whole line of the LCD each time around the loop.

```
lcd.setCursor(0, 0);

lcd.print("Temp C ");

lcd.setCursor(6, 0);
```



---

```
lcd.print(tempF);
```

The rather strange comment serves to remind you of the 16 columns of the display. You can then print a string of that length with spaces where the actual reading will go.

To fill in the blanks, set the cursor position for where the reading should appear and then print it.

## Lesson 28 DC Motors

### Overview

In this lesson, you will learn how to control a small DC motor using an UNO R3 and a transistor.

### Component Required:

- (1)x LONTEN Uno R3
- (1) x 830 tie-points breadboard
- (1) x L293D IC
- (1) x Fan blade and 3-6v motor
- (5) x M-M wires (Male to Male jumper wires)
- (1) x Power Supply Module
- (1) x 9V1A adapter

### Component Introduction

## Breadboard Power Supply

The small DC motor is likely to use more power than an UNO R3 board digital output can handle directly. If we tried to connect the motor straight to an UNO R3 board pin, there is a good chance that it could damage the UNO R3 board. So we use a power supply module provides power supply.



## Product Specifications:

Locking On/Off Switch

LED Power Indicator

Input voltage: 6.5-9v (DC) via 5.5mm x 2.1mm plug

Output voltage: 3.3V/5v

Maximum output current: 700 mA

# LROBRYA


Independent control rail output. 0v, 3.3v, 5v to breadboard

Output header pins for convenient external use

Size: 2.1 in x 1.4 in

USB device connector onboard to power external device


## Setting up output voltage:

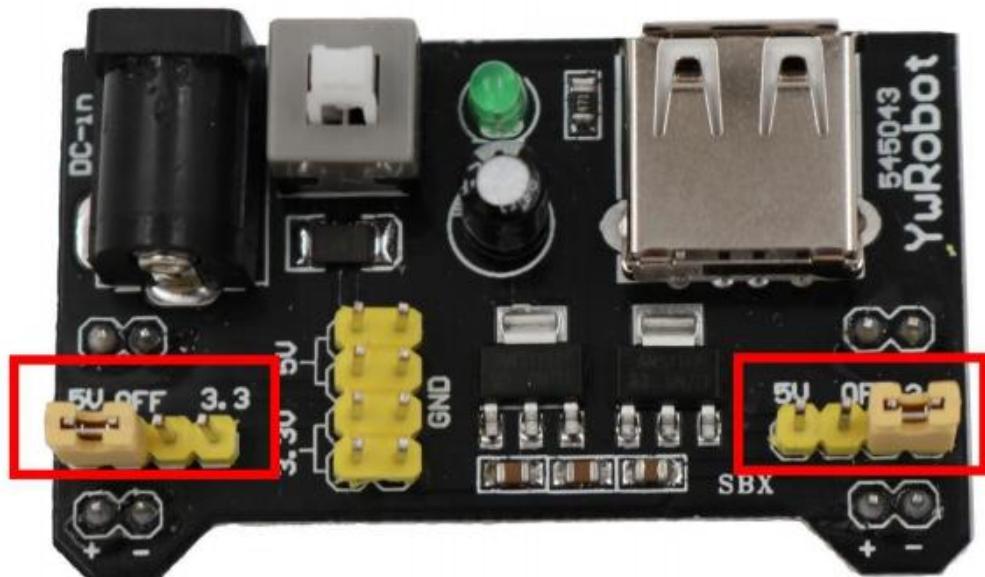

The left and right voltage output can be configured independently. To select the output voltage, move jumper to the corresponding pins. Note: power indicator LED and the breadboard power rails will not power on if both jumpers are in the “OFF” position.

# LROBROUYA

---

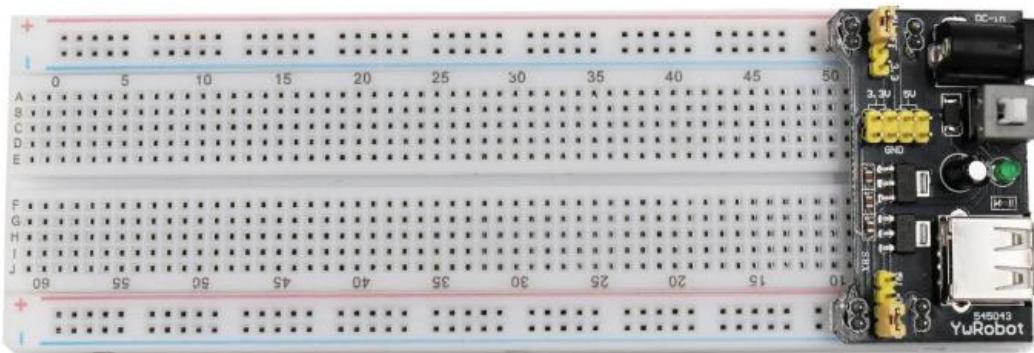

## Important note:

Make sure that you align the module correctly on the breadboard. The negative pin(-) on module lines up with the blue line(-) on breadboard and that the positive pin(+) lines up with the red line(+). Failure to do so could result in you accidentally reversing the power to your project

## L293D

This is a very useful chip. It can actually control two motors independently. We are just using half the chip in this lesson, most of the pins on the right hand side of the chip are for controlling a second motor.



# LROBRYA

## Product Specifications:

- Featuring Unitrode L293 and L293D Products Now From Texas Instruments
- Wide Supply-Voltage Range: 4.5 V to 36 V
- Separate Input-Logic Supply
- Internal ESD Protection
- Thermal Shutdown
- High-Noise-Immunity Inputs
- Functionally Similar to SGS L293 and SGS L293D
- Output Current 1 A Per Channel (600 mA for L293D)
- Peak Output Current 2 A Per Channel (1.2 A for L293D)
- Output Clamp Diodes for Inductive Transient Suppression (L293D)



## Description/ordering information

The L293 and L293D are quadruple high-current half-H drivers. The L293 is designed to provide bidirectional drive currents of up to 1 A at voltages from 4.5 V to 36 V. The L293D is designed to provide




---

bidirectional drive currents of up to 600-mA at voltages from 4.5 V to 36 V. Both devices are designed to drive inductive loads such as relays, solenoids, dc and bipolar stepping motors, as well as other high-current/high-voltage loads in positive-supply applications. All inputs are TTL compatible. Each output is a complete totem-pole drive circuit, with a Darlington transistor sink and a pseudo-Darlington source. Drivers are enabled in pairs, with drivers 1 and 2 enabled by 1,2EN and drivers 3 and 4 enabled by 3,4EN. When an enable input is high, the associated drivers are enabled, and their outputs are active and in phase with their inputs. When the enable input is low, those drivers are disabled, and their outputs are off and in the high-impedance state. With the proper data inputs, each pair of drivers forms a full-H (or bridge) reversible drive suitable for solenoid or motor applications.

## **Block diagram**

# LROBRYA

---

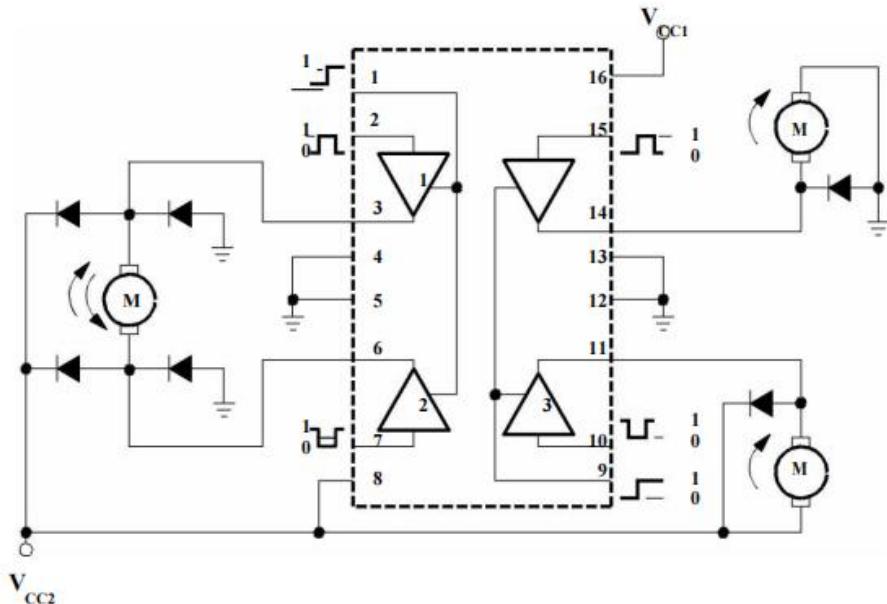

I got fed up with indecipherable pinout diagrams within datasheets, so have designed my own that I think gives more pertinent information. There are 3 wires connected to the Arduino, 2 wires connected to the motor, and 1 wire connected to a battery.

## L293D

M1 PWM	1	16	Battery +ve
M1 direction 0/1	2	15	M2 direction 0/1
M1 +ve	3	14	M2 +ve
GND	4	13	GND
GND	5	12	GND
M1 -ve	6	11	M2 -ve
M1 direction 1/0	7	10	M2 direction 1/0
Battery +ve	8	9	M2 PWM

Motor 1

Motor 2



---

To use this pinout:

The left hand side deals with the first motor, the right hand side deals with a second motor. Yes, you can run it with only one motor connected.

## **Arduino Connections**

M1 PWM - connect this to a PWM pin on the Arduino. They're label led on the Uno, pin 5 is an example. Output any integer between 0 and 255, where 0 will be off, 128 is half speed and 255 is max speed.

M1 direction 0/1 and M1 direction 1/0 - Connect these two to two digital Arduino pins.


Output one pin as HIGH and the other pin as LOW, and the motor will spin in one direction.

Reverse the outputs to LOW and HIGH, and the motor will spin in the other direction.


## **Connection**

### **Schematic**

# LROBRYA

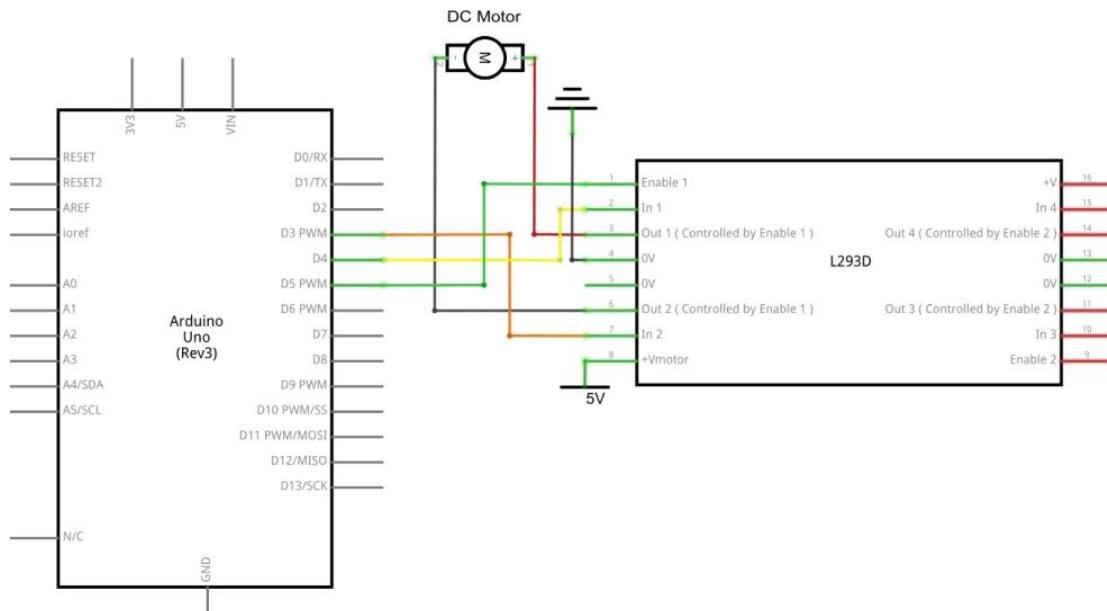

## Circuit Connection

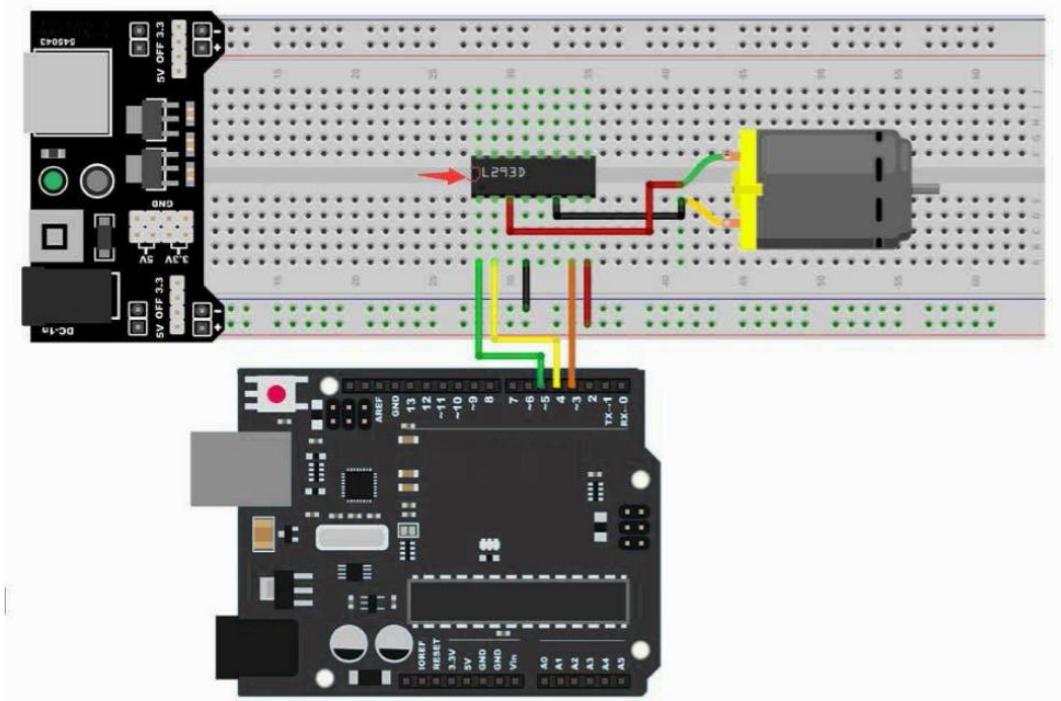


# LROBRYA

---

The code below does not use a separate power supply (ie a battery), it uses instead the 5v power from the Arduino. Note that this would be risky without the L293D controlling it.

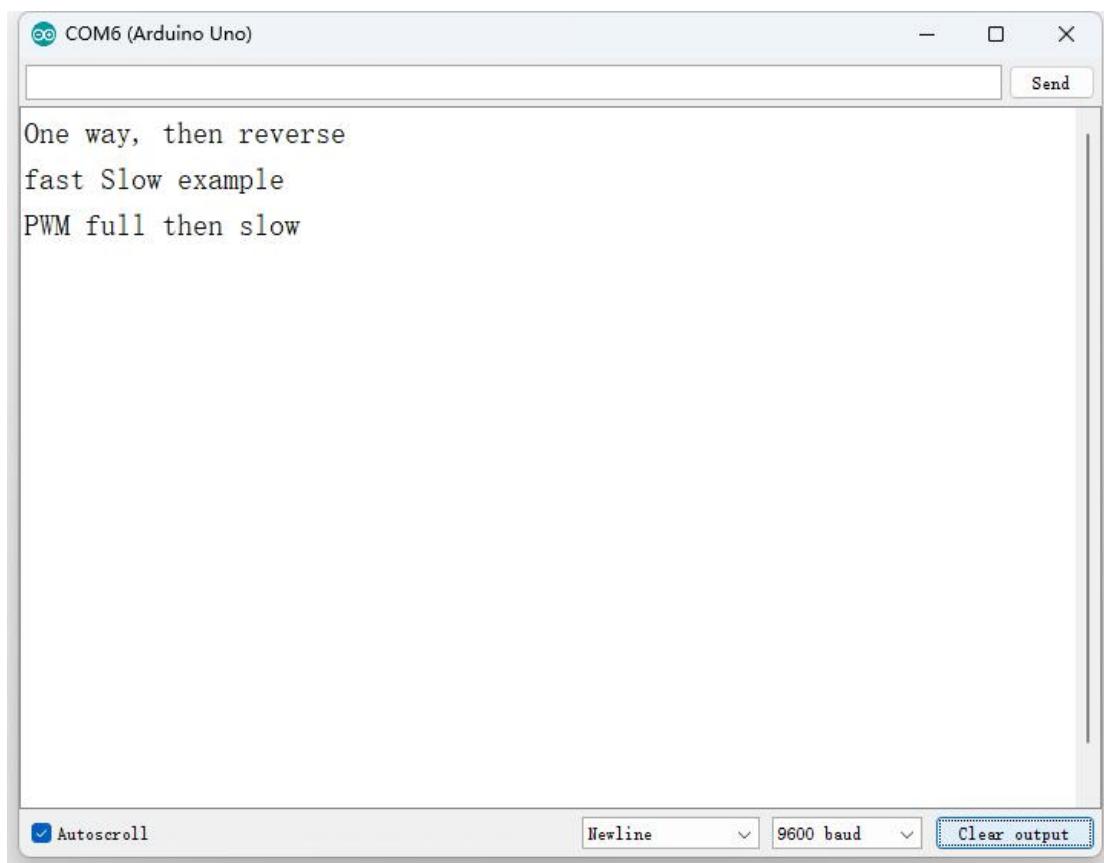You should never connect a motor directly to the Arduino, because when you switch a motor off you get an electrical feedback. With a small motor, this will damage your Arduino, and with a large motor, you can watch an interesting flame and sparks effect.



A screenshot of the Arduino Serial Monitor window titled "COM6 (Arduino Uno)". The window shows the following text output:


```
One way, then reverse
fast Slow example
PWM full then slow
```

At the bottom of the window, there are several controls: "Autoscroll" (checked), "Newline", "9600 baud", and "Clear output".

# LROBRYA

---

## Example picture

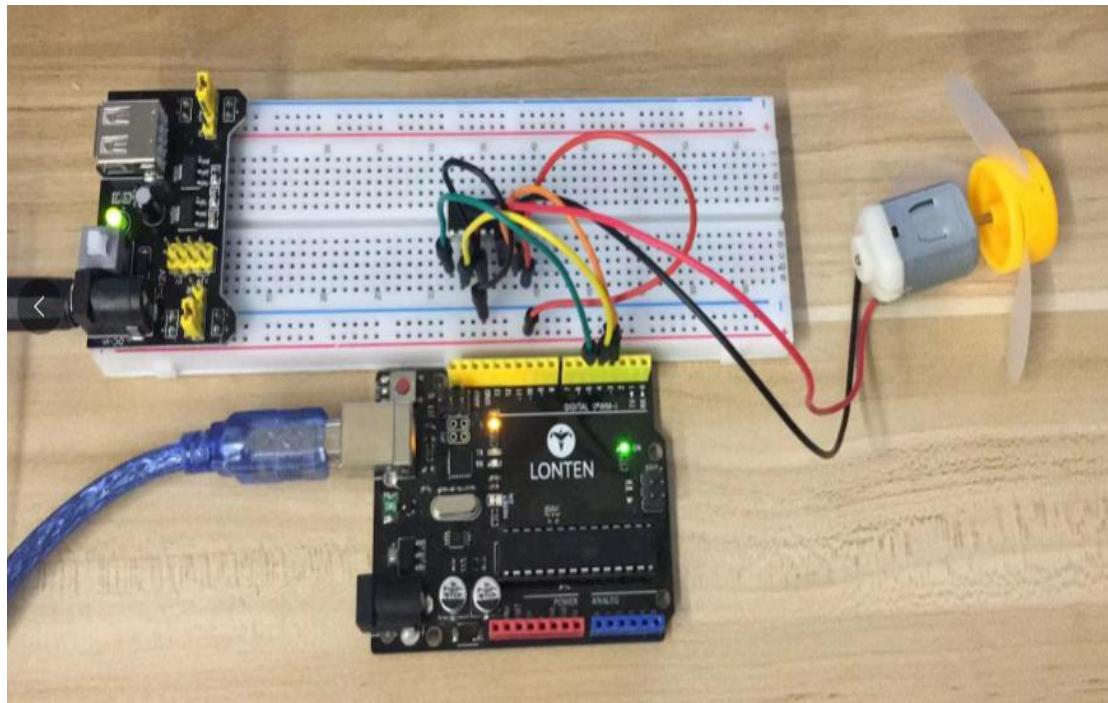

## Code

After wiring, please open the program in the code folder- Lesson 28 DC Motors and click UPLOAD to upload the program.

After program loading, turn on all the power switches. The motor will slightly rotate clockwise and anticlockwise for 5 times. Then, it will continue to dramatically rotate clockwise. After a short pause, it will dramatically rotate anticlockwise. Then the controller board will send PWM signal to drive the motor, the motor will slowly reduce its maximum RPM to the minimum and increase to the maximum again. Finally, it comes to a stop for 10s until the next cycle begins.



---

## Lesson 29 Relay

### Overview

In this lesson, you will learn how to use a relay.

### Component Required:

- (1) x LONTEN Uno R3
- (1) x 830 tie-points breadboard
- (1) x Fan blade and 3-6v dc motor
- (1) x L293D IC
- (1) x 5v Relay
- (1) x Power Supply Module
- (1) x 9V1A Adapter
- (8) x M-M wires (Male to Male jumper wires)

### Component Introduction

#### Relay:





---

A relay is an electrically operated switch. Many relays use an electromagnet to mechanically operate a switch, but other operating principles are also used as in solid-state relays. Relays are used where it is necessary to control a circuit by a low-power signal (with complete electrical isolation between control and controlled circuits), or where several circuits must be controlled by one signal. The first relays were used in long-distance telegraph circuits as amplifiers. They repeated the signal coming in from one circuit and re-transmitted it on another circuit. Relays were used extensively in telephone exchanges and early computers to perform logical operations.

A type of relay that can handle the high power required to directly control an electric motor or other loads is called a contactor. Solid-state relays control power circuits with no moving parts, instead using a semiconductor device to perform the switching.

Relays with calibrated operating characteristics and sometimes multiple operating coils are used to protect electrical circuits from overload or faults. In modern electric power systems, these functions are performed by digital instruments called "protective relays".


Below is the schematic of how to drive relay with Arduino.

# LROBRYA

---

You may be confused about how to insert the relay into the bread board.

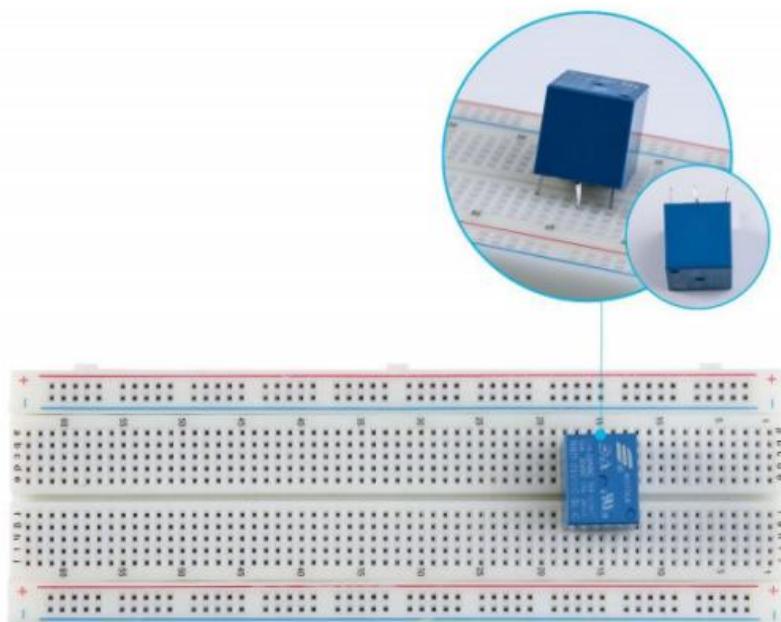
As the picture below shows, you will have to bend one of the pins of the relay slightly then you can insert it into the bread board.




## Connection

### Schematic

# LROBRUYA

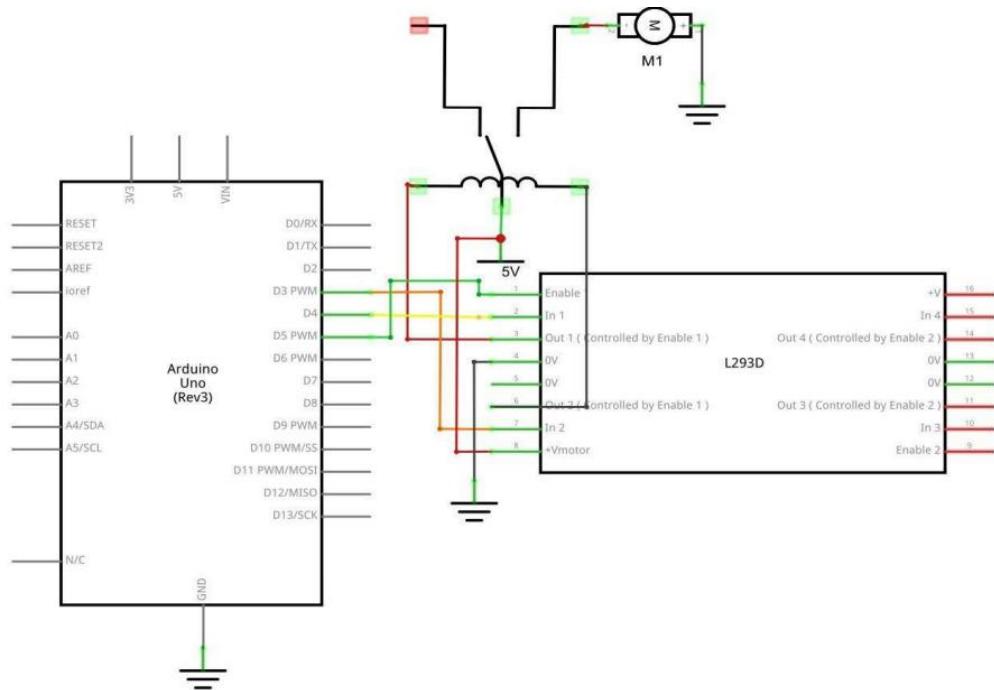


## Circuit Connection

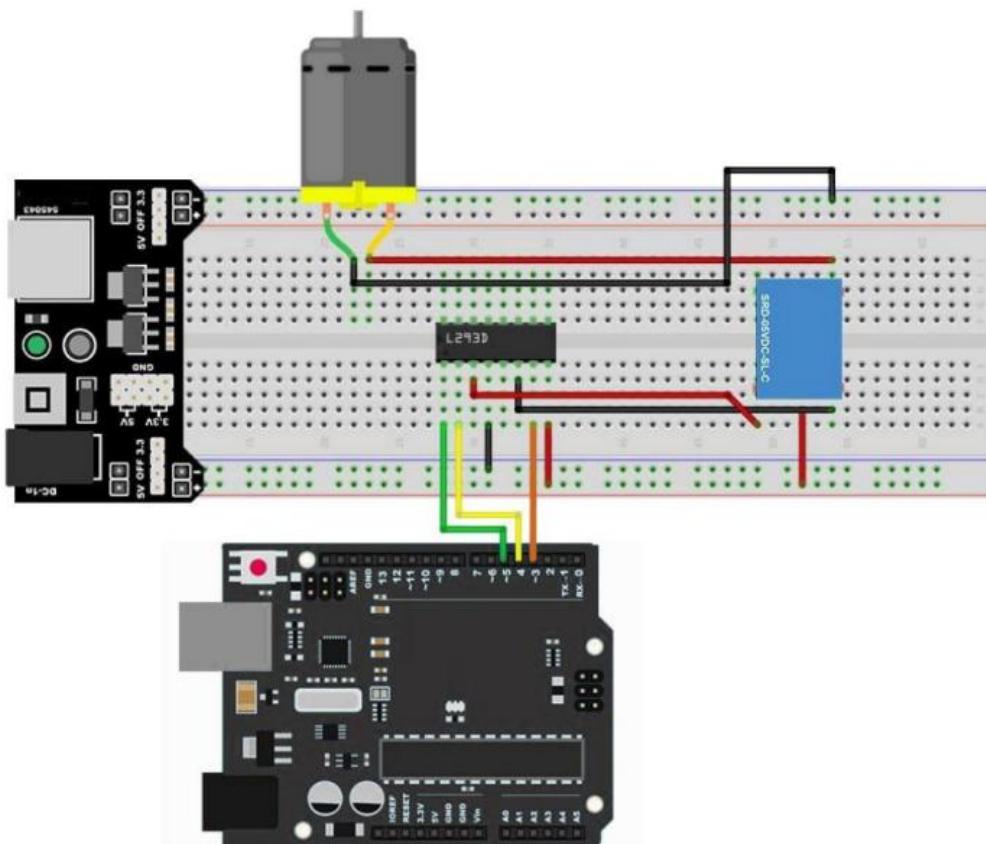

# LROBRYA

---

## Example picture

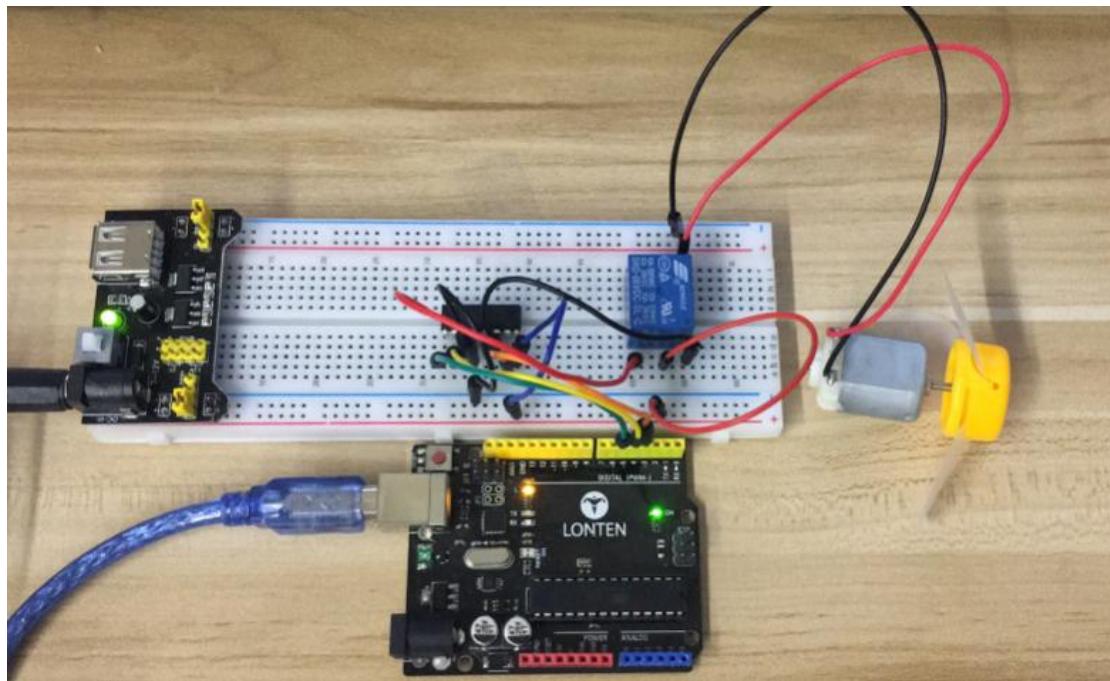

## Code

After wiring, please open the program in the code folder- Lesson 29

Relay and click UPLOAD to upload the program.

After program loading, turn on all the power switches. The relay will pick up with a ringing sound. Then, the motor will rotate. After a period of time, the relay will be released, and the motor stops.

## Lesson 30 Stepper Motor

## Overview

In this lesson, you will learn a fun and easy way to drive a stepper motor.

# LROBRYA

---

The stepper we are using comes with its own driver board making it easy to connect to our UNO.

## **Component Required:**

- (1) x LONTEN Uno R3
- (1) x 830 tie-points breadboard
- (1) x ULN2003 stepper motor driver module
- (1) x Stepper motor
- (1) x 9V1A Adapter
- (1) x Power supply module
- (6) x F-M wires (Female to Male DuPont wires)
- (1) x M-M wire (Male to Male jumper wire)

## **Component Introduction**

### **Stepper Motor**



A stepper motor is an electromechanical device which converts electrical pulses into discrete mechanical movements. The shaft or spindle of a stepper motor rotates in discrete step increments when electrical



---

command pulses are applied to it in the proper sequence. The motors rotation has several direct relationships to these applied input pulses. The sequence of the applied pulses is directly related to the direction of motor shafts rotation. The speed of the motor shafts rotation is directly related to the frequency of the input pulses and the length of rotation is directly related to the number of input pulses applied. One of the most significant advantages of a stepper motor is its ability to be accurately controlled in an open loop system. Open loop control means no feedback information about position is needed. This type of control eliminates the need for expensive sensing and feedback devices such as optical encoders. Your position is known simply by keeping track of the input step pulses.

## **Stepper motor 28BYJ-48 Parameters**

Model: 28BYJ-48

Rated voltage: 5VDC

Number of Phase: 4

Speed Variation Ratio: 1/64

Stride Angle:  $5.625^\circ$  /64

Frequency: 100Hz

DC resistance:  $50\Omega \pm 7\%$ ( $25^\circ\text{C}$ )

# LROBRYA

---

Idle In-traction Frequency: > 600Hz

Idle Out-traction Frequency: > 1000Hz

In-traction Torque >34.3mN.m(120Hz)

Self-positioning Torque >34.3mN.m

Friction torque: 600-1200 gf.cm

Pull in torque: 300 gf.cm

Insulated resistance >10MΩ(500V)

Insulated electricity power: 600VAC/1mA/1s


Insulation grade: A

Rise in Temperature <40K(120Hz)

Noise <35dB(120Hz,No load,10cm)

## Interfacing circuits


### WIRING DIAGRAM

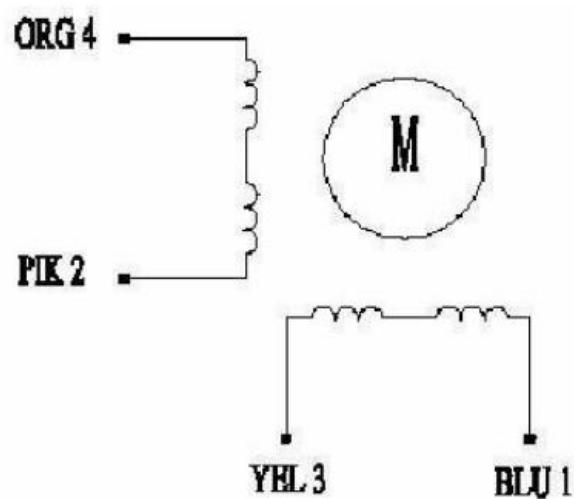

# LROBRYA

The bipolar stepper motor usually has four wires coming out of it. Unlike unipolar steppers, bipolar steppers have no common center connection. They have two independent sets of coils instead. You can distinguish them from unipolar steppers by measuring the resistance between the wires. You should find two pairs of wires with equal resistance. If you've got the leads of your meter connected to two wires that are not connected (i.e. not attached to the same coil), you should see infinite resistance (or no continuity).

## ULN2003 Driver Board

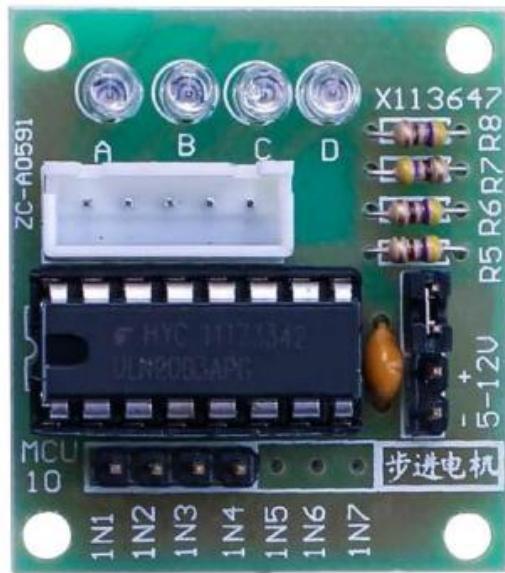

## Product Description

- o Size: 42mmx30mm
- o Use ULN2003 driver chip, 500mA

# LROBRYA

---

- o A. B. C. D LED indicating the four phase stepper motor working condition.
- o White jack is the four phase stepper motor standard jack.
- o Power pins are separated
- o We kept the rest pins of the ULN2003 chip for your further prototyping.


The simplest way of interfacing a unipolar stepper to Arduino is to use a breakout for ULN2003A transistor array chip. The ULN2003A contains seven Darlington transistor drivers and is somewhat like having seven TIP120 transistors all in one package. The ULN2003A can pass up to 500 mA per channel and has an internal voltage drop of about 1V when on. It also contains internal clamp diodes to dissipate voltage spikes when driving inductive loads. To control the stepper, apply voltage to each of the coils in a specific sequence.

The sequence would go like this:

Lead Wire Color	---> CW Direction (1-2 Phase)							
	1	2	3	4	5	6	7	8
4 ORG	-	-						-
3 YEL		-	-	-				
2 PIK				-	-	-		
1 BLU						-	-	-

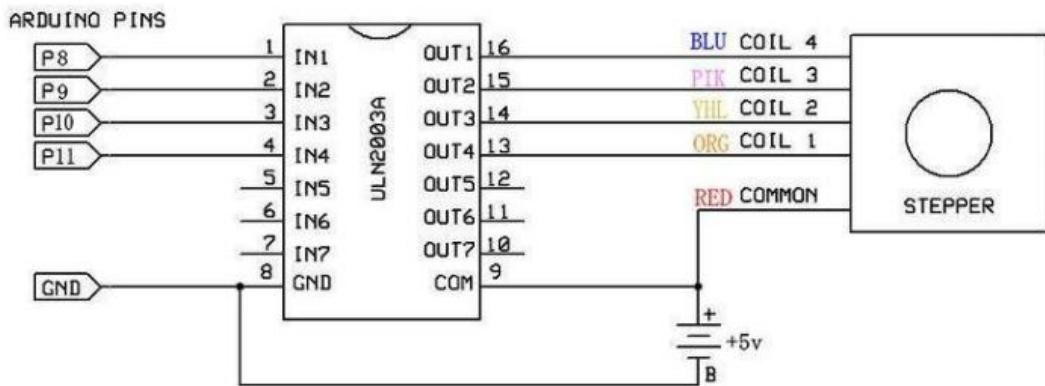
# LROBRYA

Here are schematics showing how to interface a unipolar stepper motor to four controller pins using a ULN2003A, and showing how to interface using four com.



## Connection


### Schematic

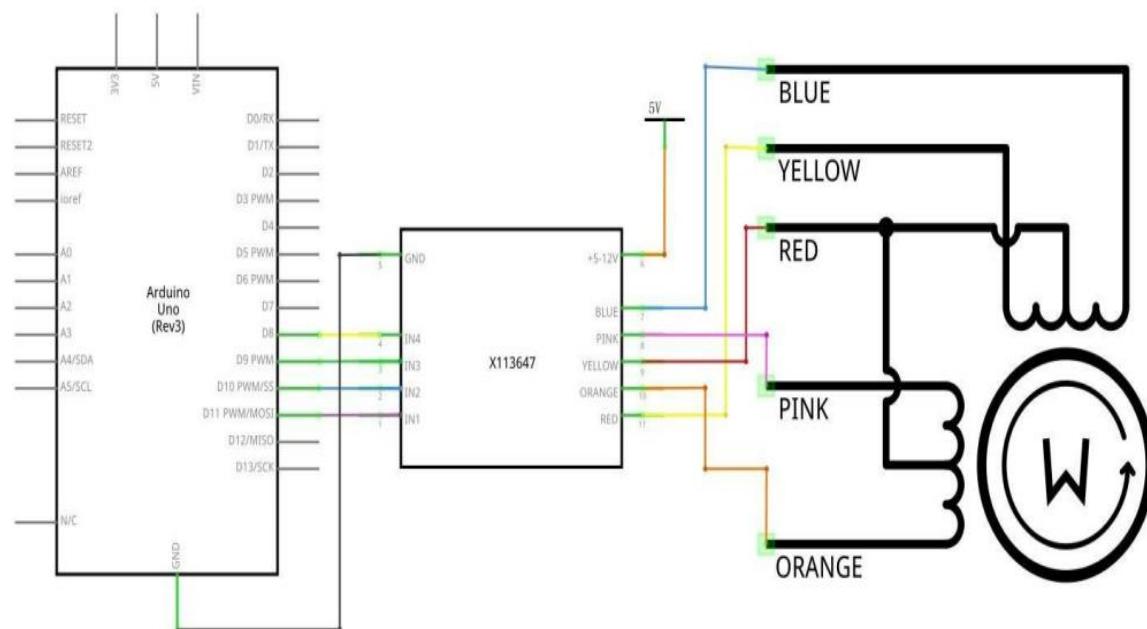

# LROBRYA

---

## Circuit Connection

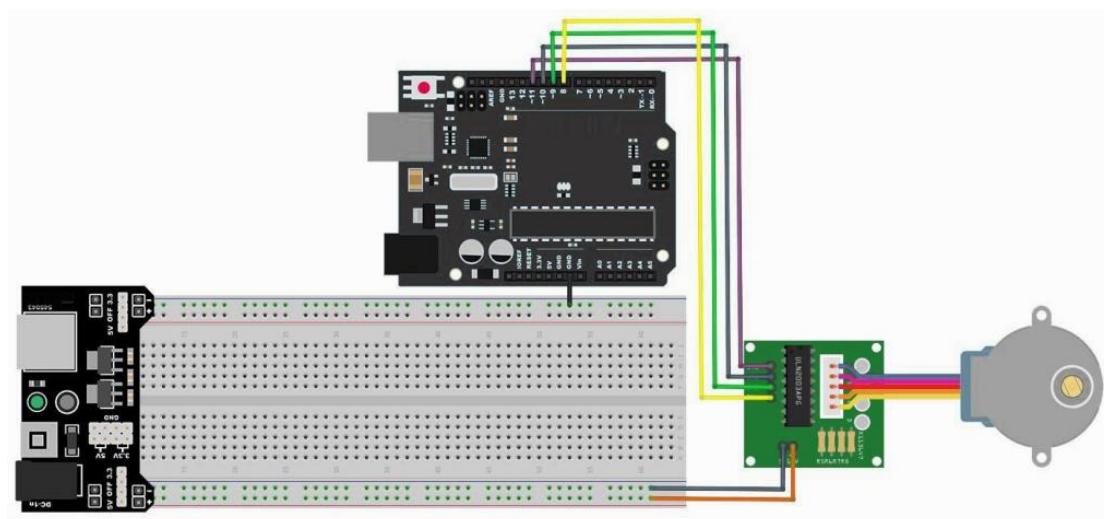

We are using 4 pins to control the Stepper.


Pin 8-11 are controlling the Stepper motor.

We connect the Ground from to UNO to the Stepper motor.

## Example picture

# LROBRYA

---

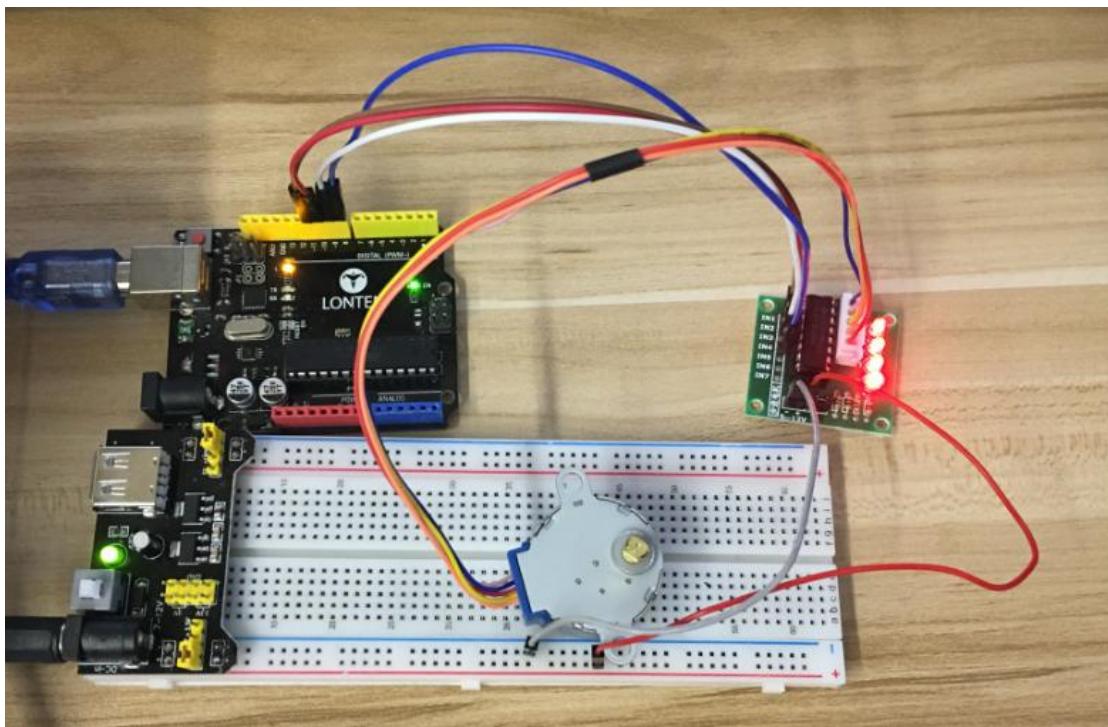

## Code

After wiring, please open the program in the code folder- Lesson 30

Stepper Motor and click UPLOAD to upload the program.

Before you can run this, make sure that you have installed the < Stepper > library or re-install it, if necessary. Otherwise, your code won't work.

## Lesson 31 Controlling Stepper Motor With Remote

## Overview

In this lesson, you will learn a fun and easy way to control a stepper motor from a distance using an IR remote control.



---

The stepper we are using comes with its own driver board making it easy to connect to our UNO.

Since we don't want to drive the motor directly from the UNO, we will be using an inexpensive little breadboard power supply that plugs right into our breadboard and power it with a 9V 1Amp power supply.

The IR sensor is connected to the UNO directly since it uses almost no power.


### **Component Required:**

- (1) x LONTEN Uno R3
- (1) x 830 tie-points breadboard
- (1) x IR receiver module
- (1) x IR remote
- (1) x ULN2003 stepper motor driver module
- (1) x Stepper motor
- (1) x Power supply module
- (1) x 9V1A Adapter
- (9) x F-M wires (Female to Male DuPont wires)
- (1) x M-M wire (Male to Male jumper wire)


### **Connection**

#### **Schematic**

# LROBRYUA

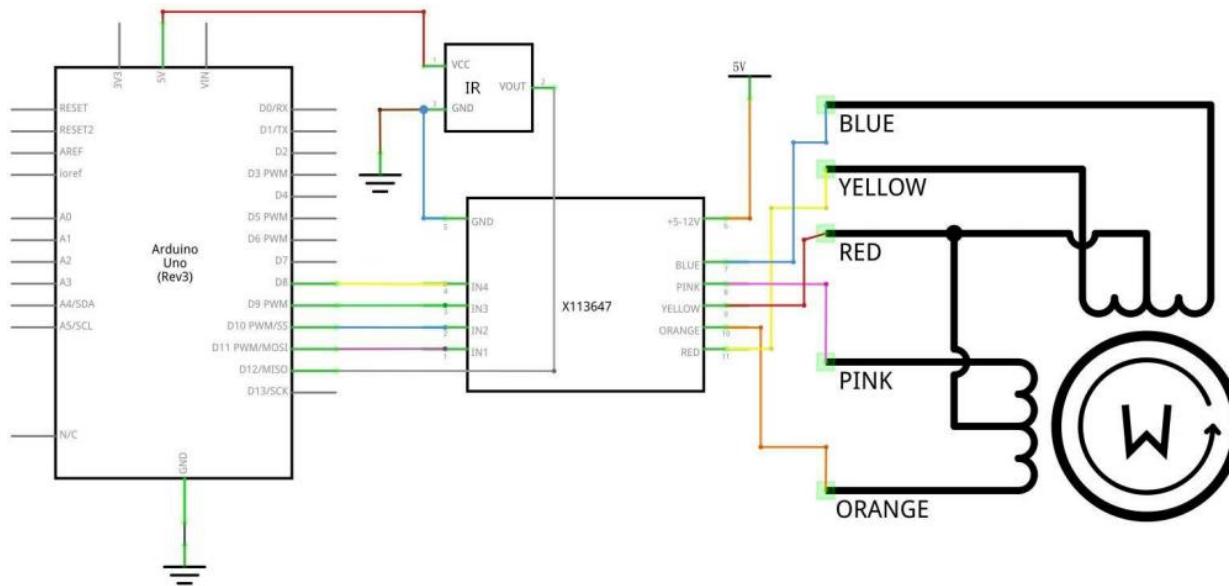

## Circuit Connection

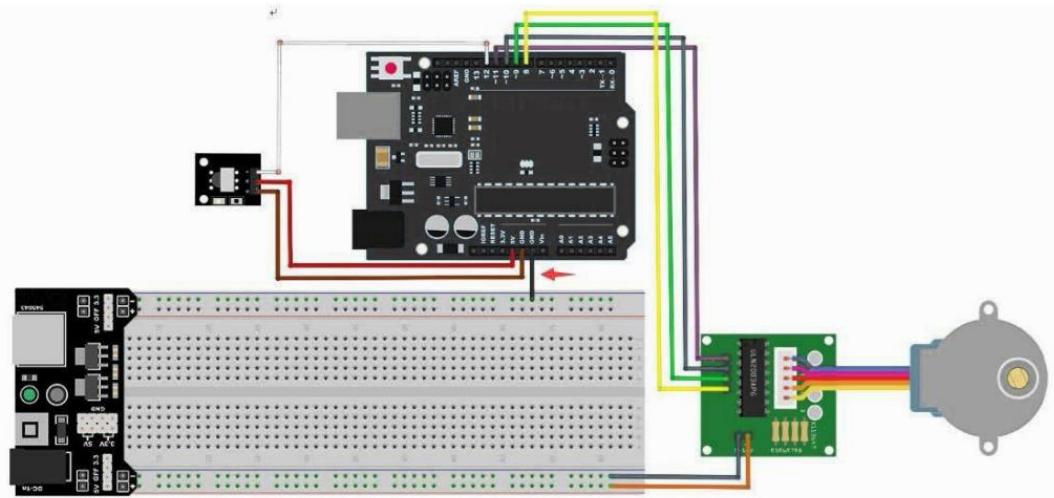

We are using 4 pins to control the Stepper and 1 pin for the IR sensor.


Pins 8-11 are controlling the Stepper motor and pin 12 is receiving the IR information.

# LROBRYA

---

We connect the 5V and Ground from the UNO to the sensor. As a precaution, use a breadboard power supply to power the stepper motor since it can use more power and we don't want to damage the power supply of the UNO.

## Example picture

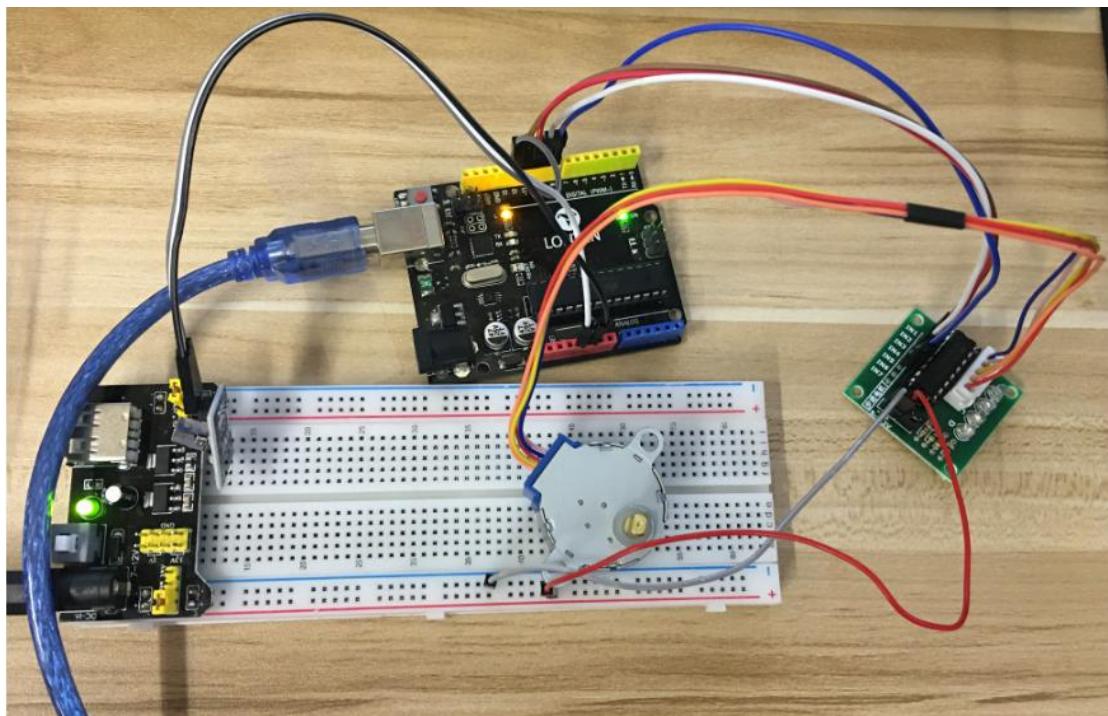

## Code

After wiring, please open program in the code folder- Lesson 31

Controlling Stepper Motor With Remote and click UPLOAD to upload the program.



---

Before you can run this, make sure that you have installed the <IRremote><Stepper>library or re-install it, if necessary. Otherwise, your code won't work.

The code only recognize 2 values from the IR Remote control: "UP" and "DOWN". When "UP" is pressed on the remote the motor will make a full rotation clockwise. "DOWN" will make a full rotation

## **Lesson 32 Controlling Stepper Motor With Rotary Encoder**

### **Overview**

In this lesson, you will learn how to control stepper motors using a rotary encoder. We will use the inexpensive and popular stepper motor that comes with its own control board: the 28BYJ-48 stepper motor with the ULN2003 board.

The 28BYJ-48 motor is not very fast or very strong, but it's great for beginners to start experimenting with controlling a stepper motor with an Arduino.

We will write some code to have the motor move in the direction that we turn the rotary encoder, and will also keep track of how many steps we have taken, so that we can have the motor move back to the starting position by pressing down on the rotary encoder switch.



---

## Component Required:

- (1)x LONTEN Uno R3
- (1) x 830 tie-points breadboard
- (1) x Rotary Encoder Module
- (1) x ULN2003 stepper motor driver module
- (1) x Stepper motor
- (1) x Power supply module
- (1) x 9V1A Adapter
- (9) x F-M wires (Female to Male DuPont wires)
- (1) x M-M wire (Male to Male jumper wire)

## Component Introduction

### Rotary encoder

A rotary encoder, also called a shaft encoder, is an electro-mechanical device that converts the angular position or motion of a shaft or axle to an analog or digital code.


There are two main types: absolute and incremental (relative). The output of absolute encoders indicates the current position of the shaft, making them angle transducers.

# LROBRYA

---

The output of incremental encoders provides information about the motion of the shaft, which is typically further processed elsewhere into information such as speed, distance and position.

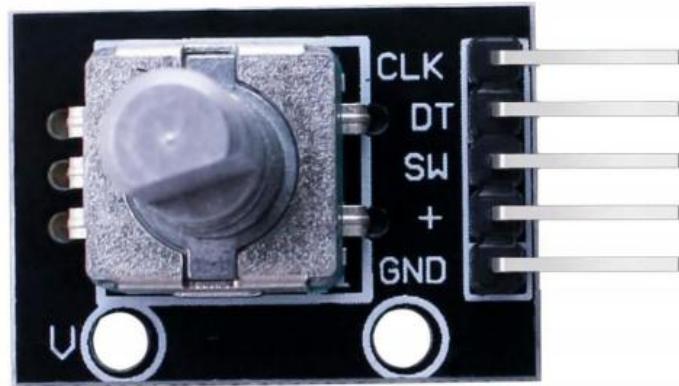
Rotary encoders are used in many applications that require precise shaft unlimited rotation—including industrial controls, robotics, special purpose photographic lenses, [1] computer input devices (such as optical mechanical mice and trackballs), controlled stress rheometers, and rotating radar platforms.




## Connection

### Schematic

# LROBRUYA

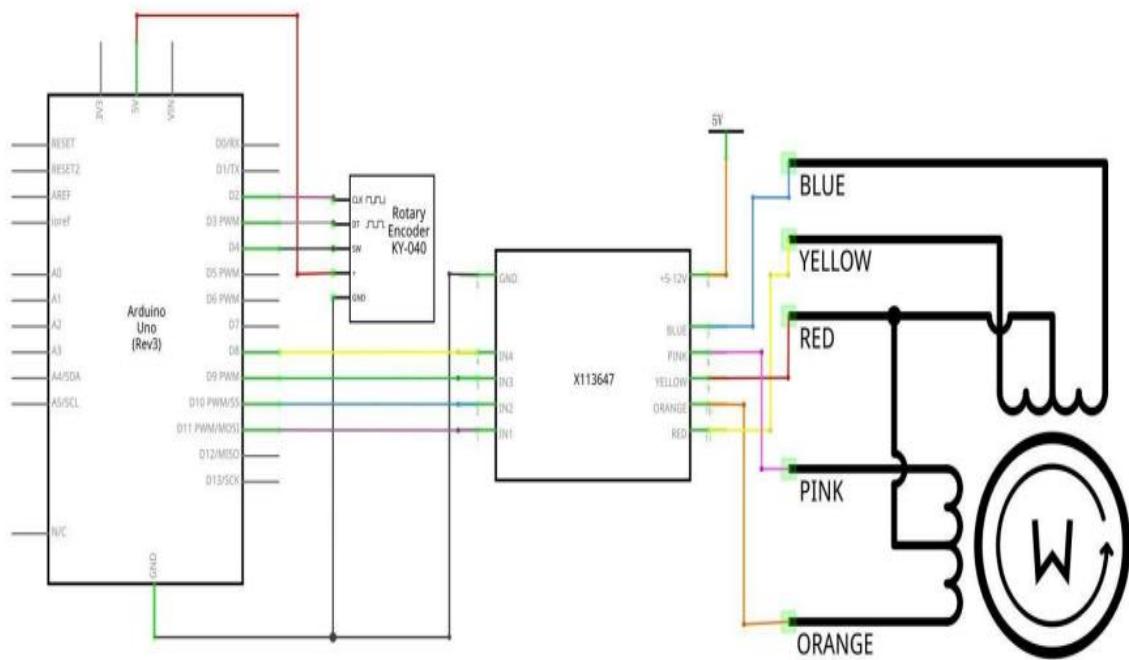

## Circuit Connection

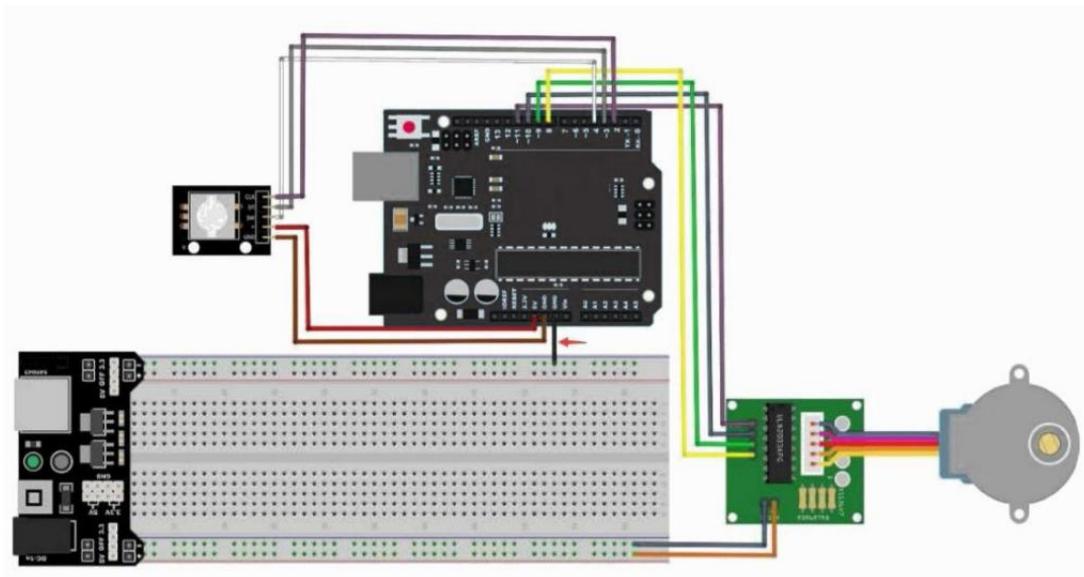

# LROBRYA


---

We are using 4 pins to control the Stepper and 3 pins for the rotary encoder module. Pins 8-11 are controlling the Stepper motor and pins 2-4 are receiving information from the rotary encoder.

We connect the 5V and Ground from to UNO to the rotary encoder and as a precaution, use a breadboard power supply to power the stepper motor since it can use more power than the UNO can provide.

We also connect the UNO Ground to the breadboard to serve as a reference.

## Example picture

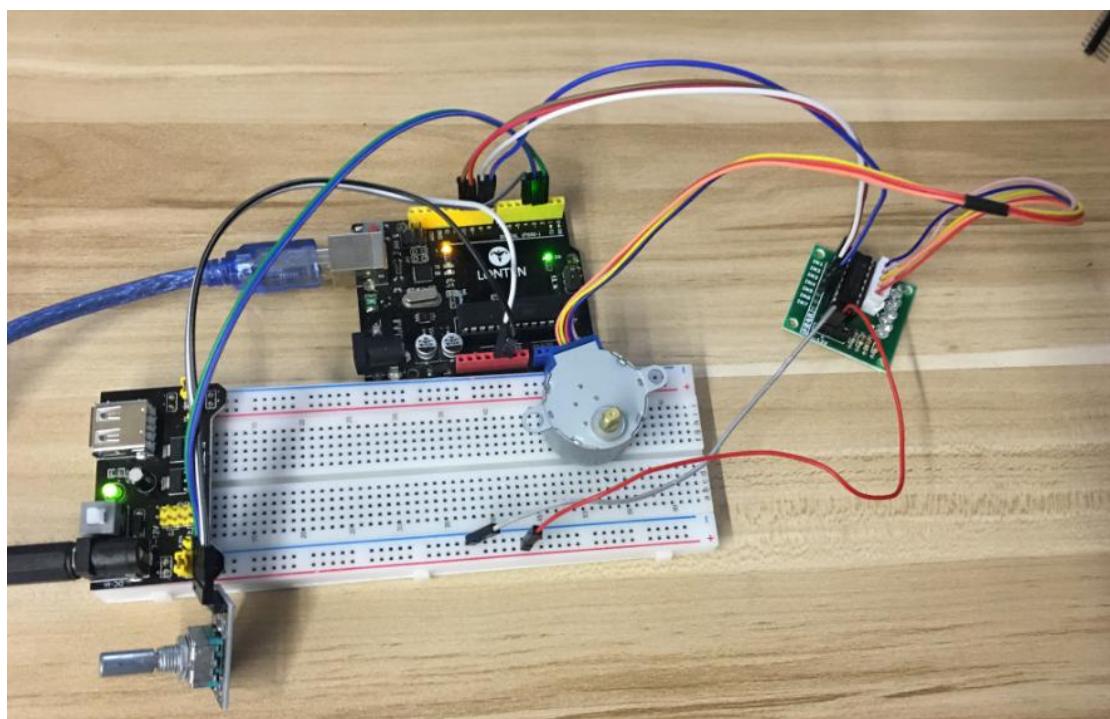



## Code

After wiring, please open the program in the code folder- Lesson 32

Controlling Stepper Motor With Rotary Encoder and click UPLOAD to upload the program.

Before you can run this, make sure that you have installed the < Stepper > library or re-install it, if necessary. Otherwise, your code won't work.

We are using some variables to store the current position, since we want to keep track of the position of the stepper motor so we can make it move back to the starting position.

We also included some error checking code to make sure that the rotary encoder is not missing steps, since that would make our motor position inaccurate.